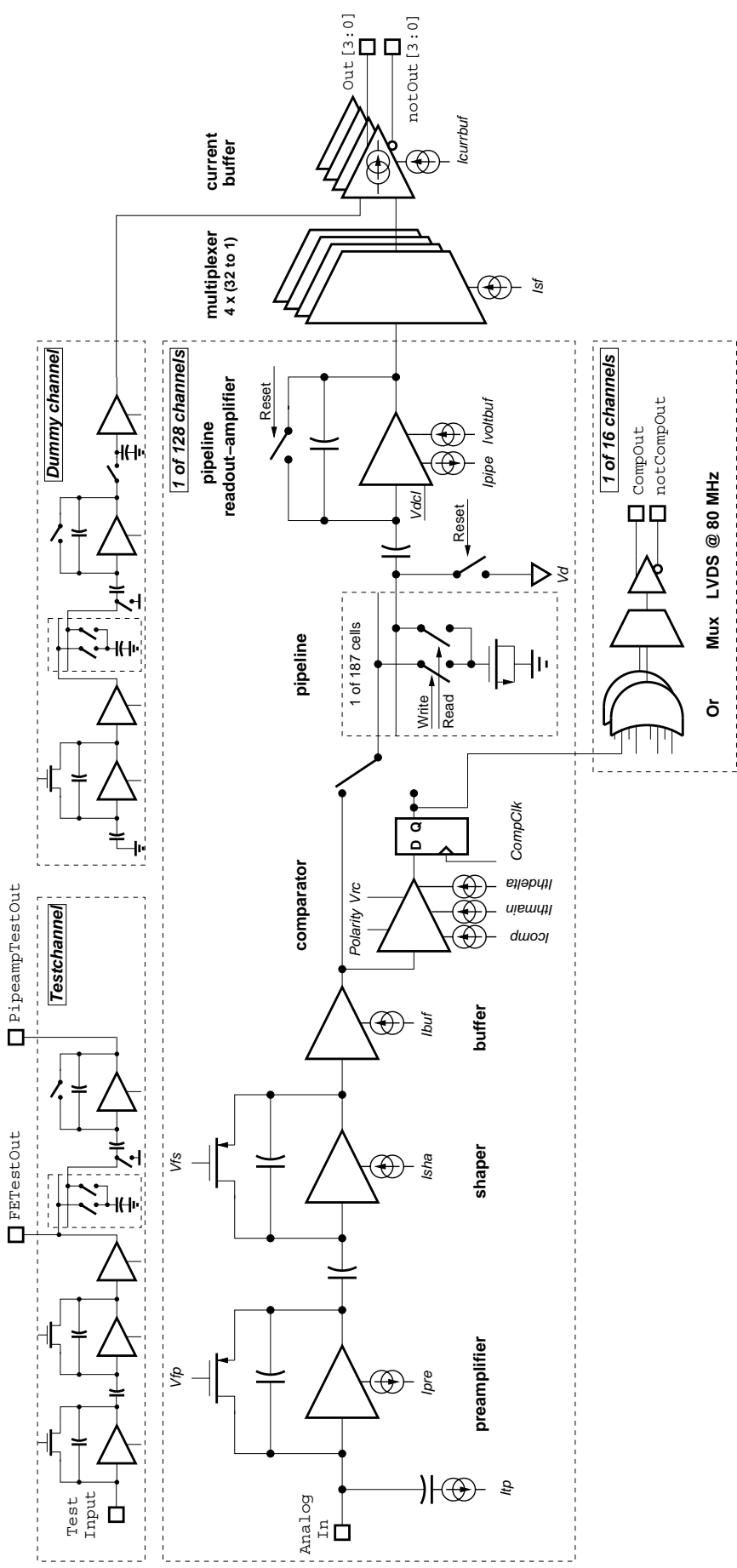


Beetle 1.2 Blockschematic



Testpulse Generator


Vfp
Vfs
Vrc
Ipre
Isha
Ibuf
Icomp
Ithdelta
Ithmain
Itp
Frontend Bias-Generator

Pipeline Control

I2C Interface


Vdcl
Vd
IvoIbuf
Ipipe
Ist
Icurbuf
Backend Bias-Generator

Testpulse

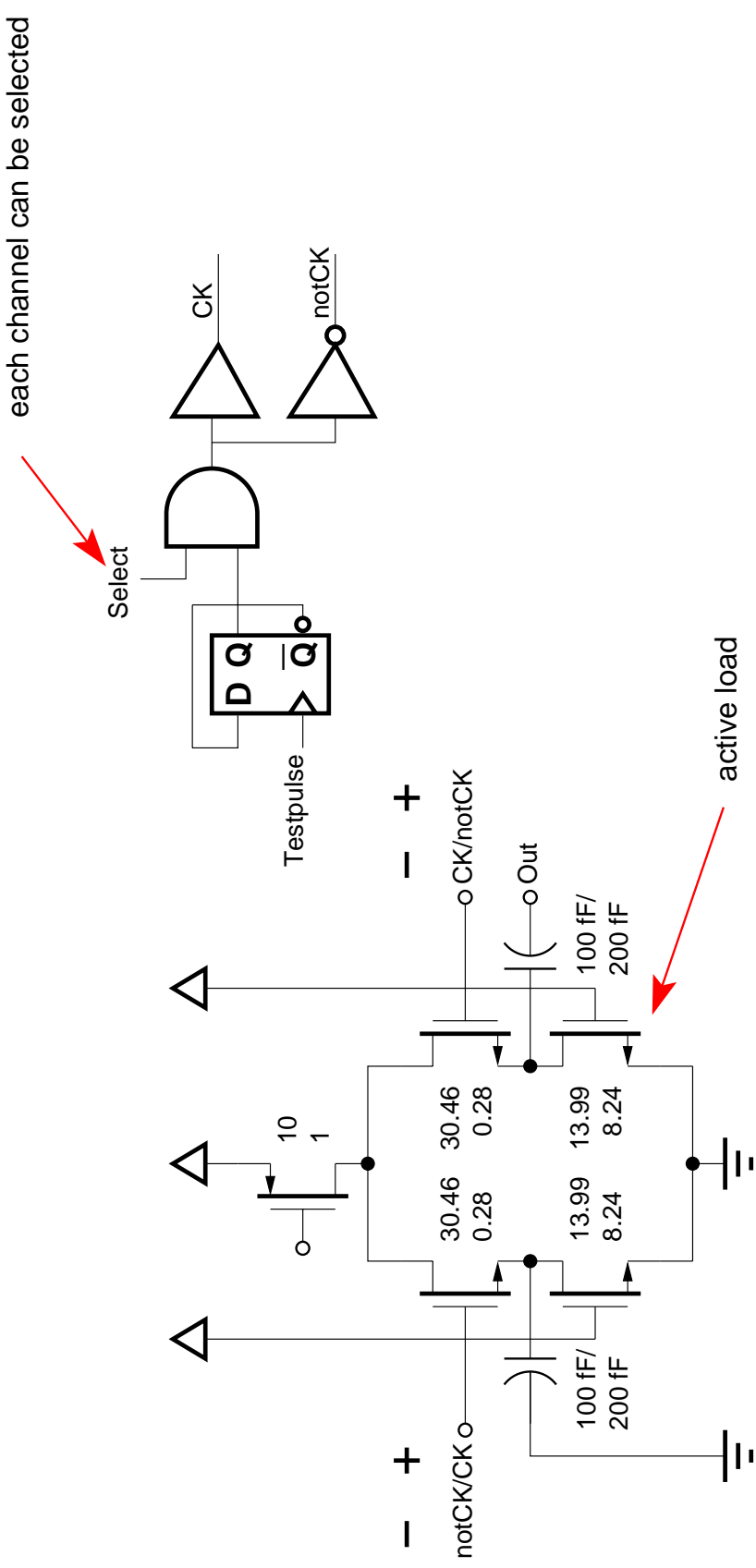


four different testpulse types are generated
 steps correspond to +2, +1, -1, -2 times the input signal amplitude

Frontend

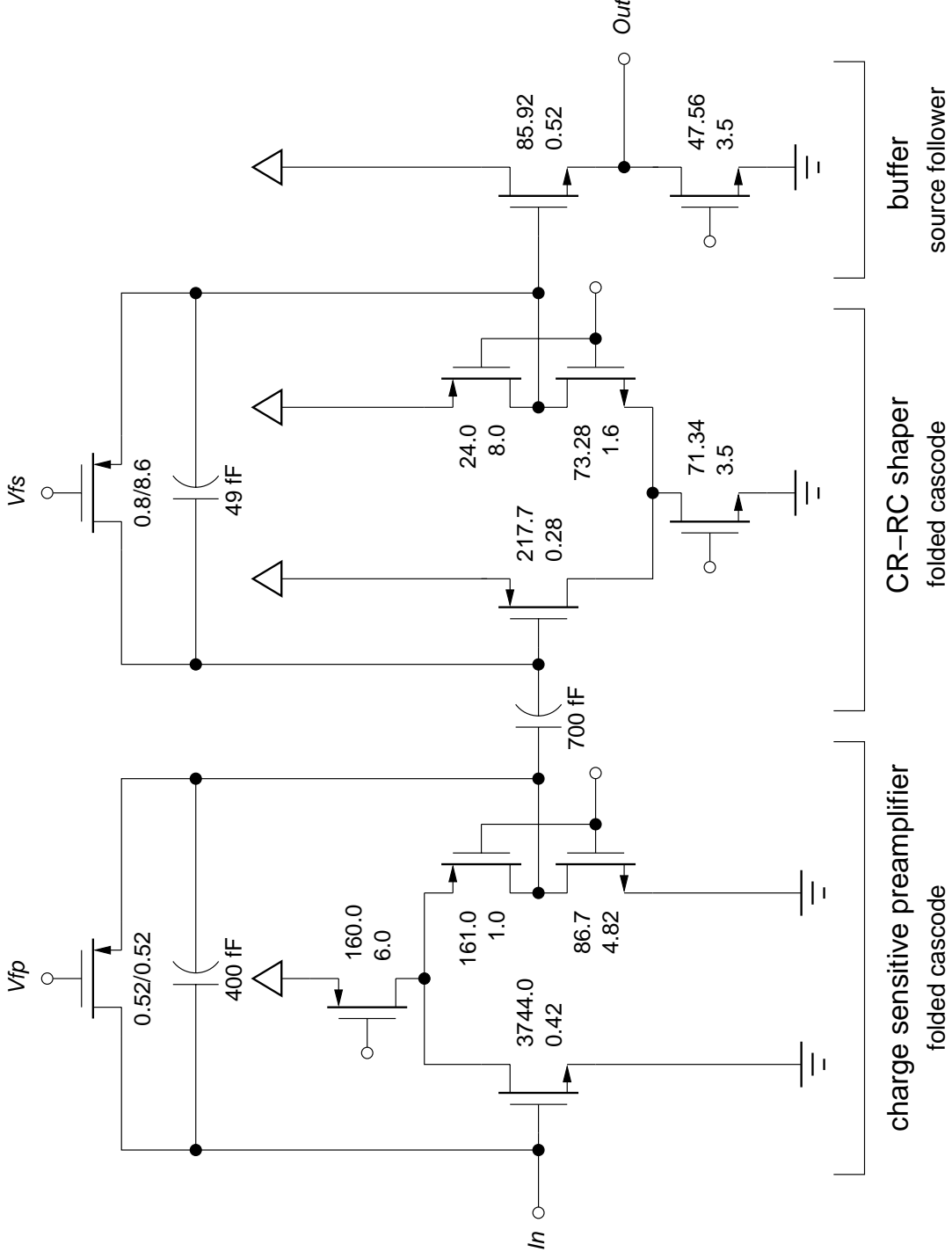




Transient response of FE

 

Simulated primary current pulse of a silicon sensor

P. Sievers

 


Transient response of the front-end

- delta-shaped pulse (dashed line)
- current pulse (solid line)



Pipeline cell

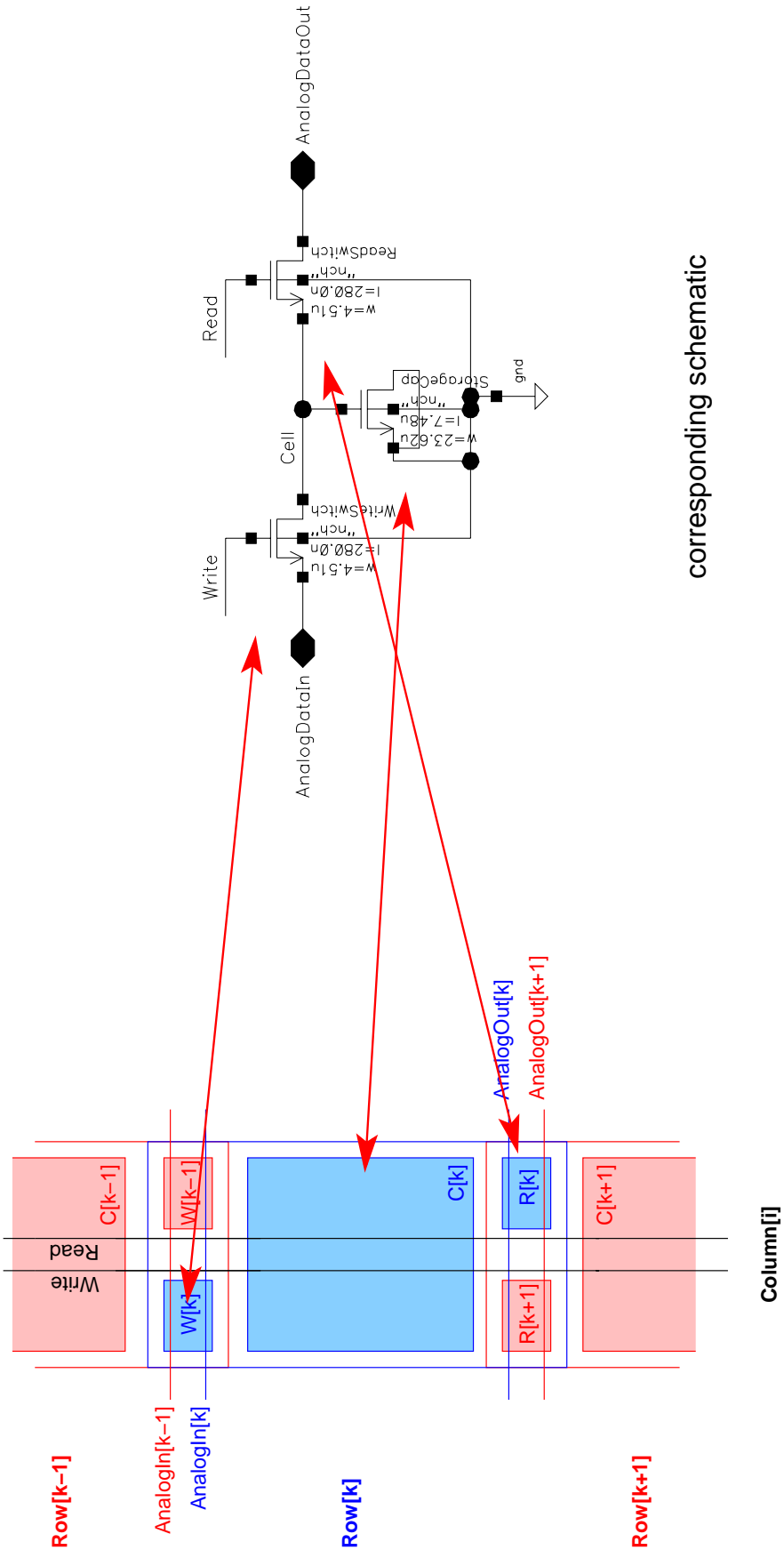

corresponding schematic


Layout of one pipeline storage cell with the adjacent cells in the same column

Pipeline cap. vs Vgate for a nmos, zvt, pmos


Expressions

▽: C zvt
▬: C pmos

△: C cap
■: C nmos

 


Pipeline readout

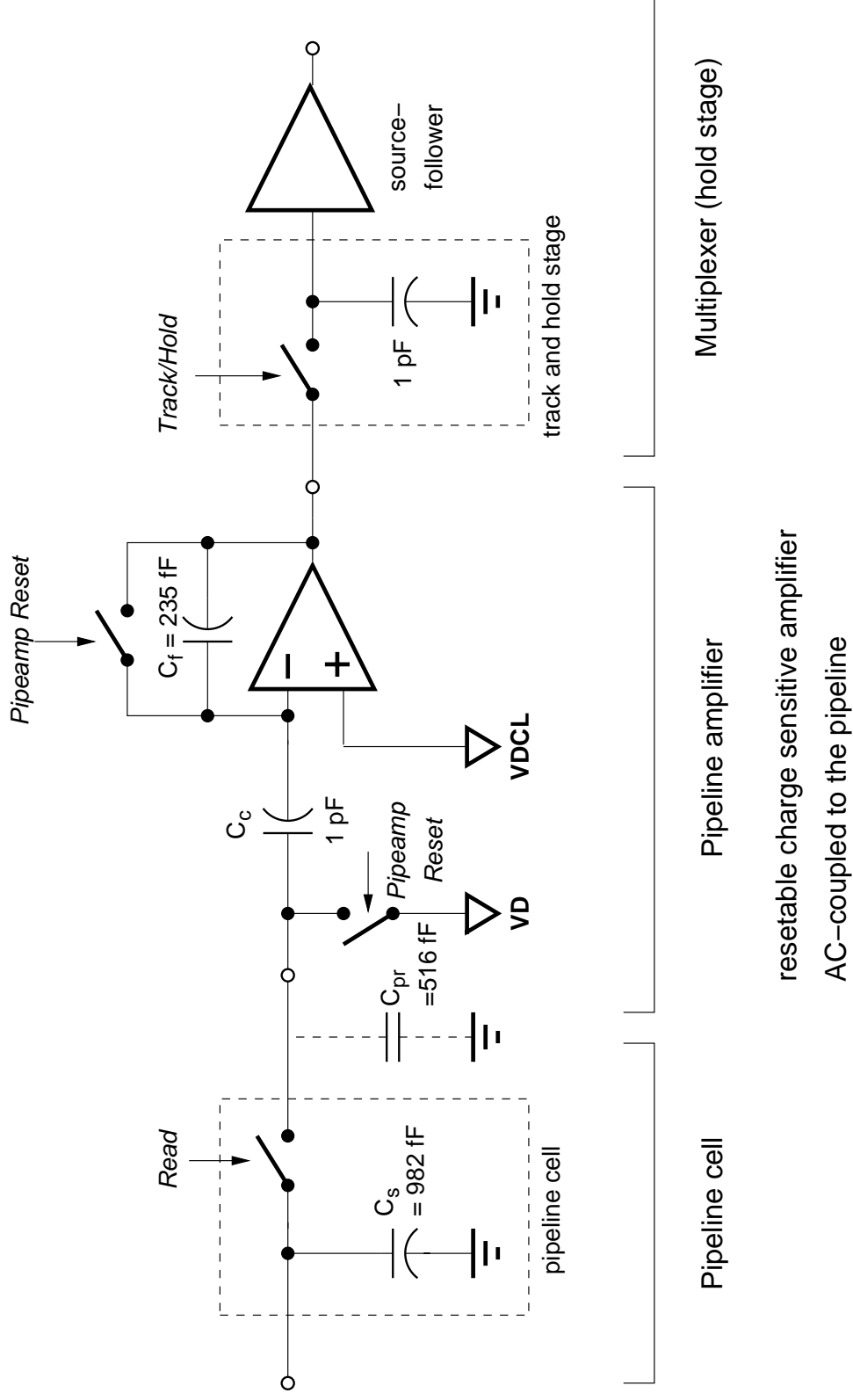


resettable charge sensitive amplifier
AC-coupled to the pipeline

Pipeline amplifier

 

- Pipeamp is reset in between two readouts (to Vd)
- Vdcl bias voltage works as the non-inverting input of the amplifier
- Vdcl node is buffered in each channel

Current output driver

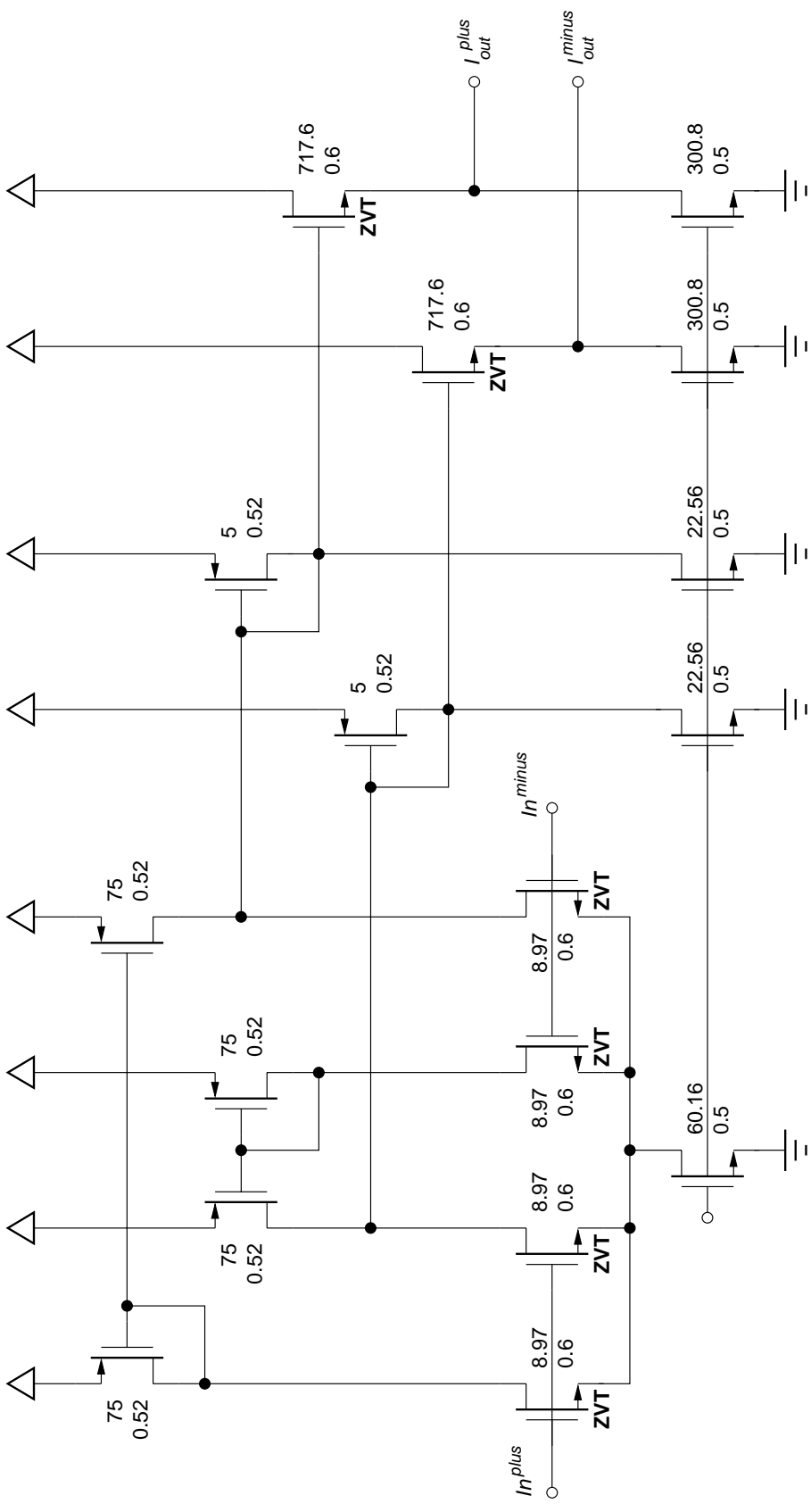


fully differential transconductance amplifier

- In(plus): output of multiplexer source follower
- In(minus): output of the dummy channel

common mode subtraction

Current source

 


- cascode is formed by M1 and M2
- feedback loop (M1, M4 and M3) stabilises the drain-source voltage of M2

Implemented as a regulated cascode configuration


- nominal output 126uA

Current DAC

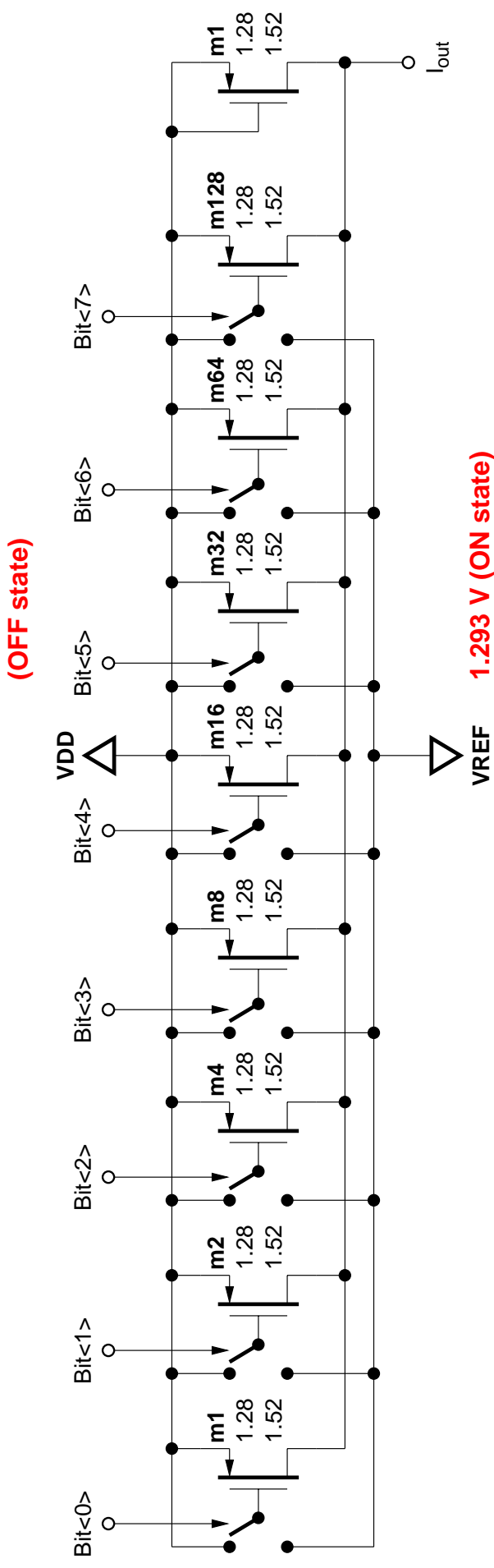

- binary-weighted current sources
- PMOS transistors are arranged in a "common centroid" layout configuration
- homogeneous structure guarantees a good matching
- maximum output current: 2.03 mA


Voltage DAC

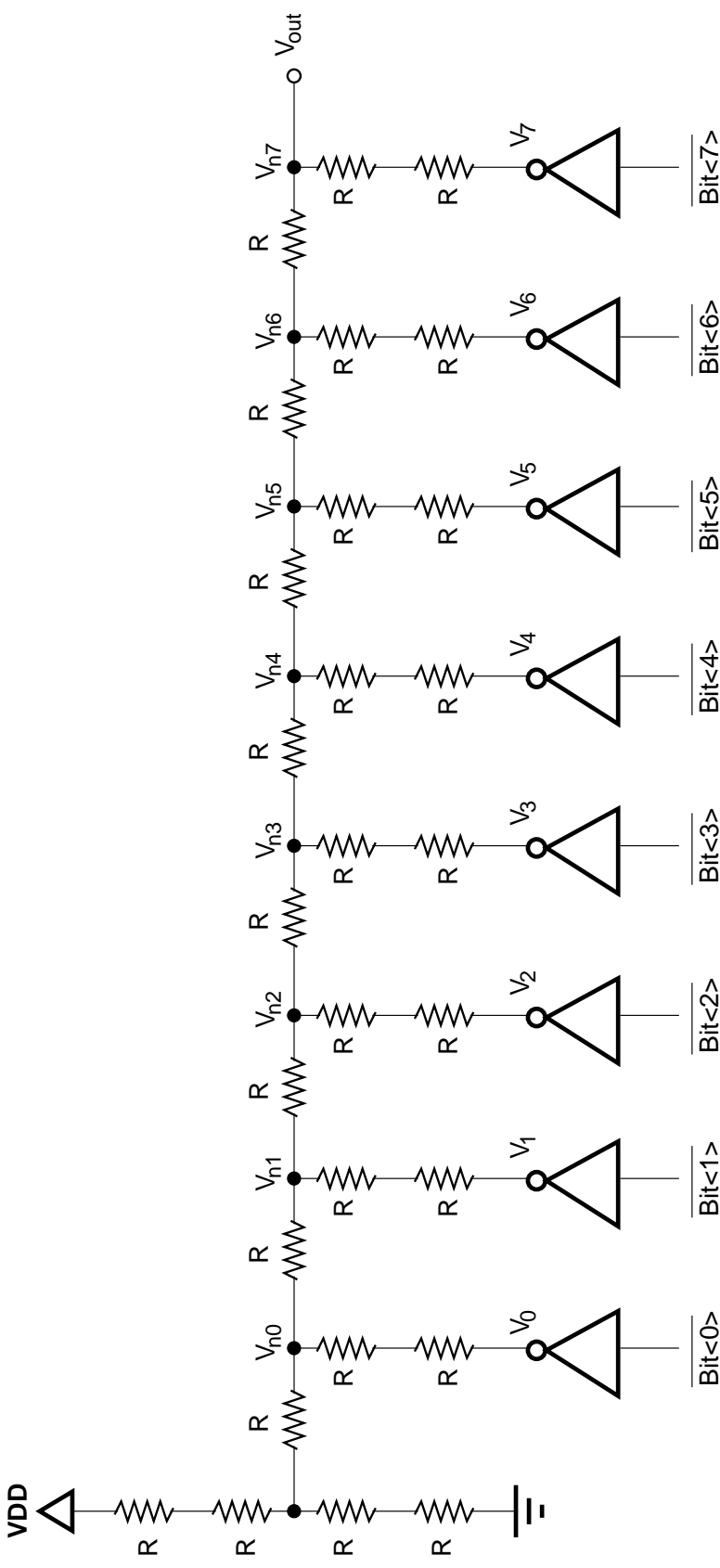


- R-2R ladder configuration
- resistors are made of non-silicided polysilicon

Power routing (Pipeamp)

Power routing

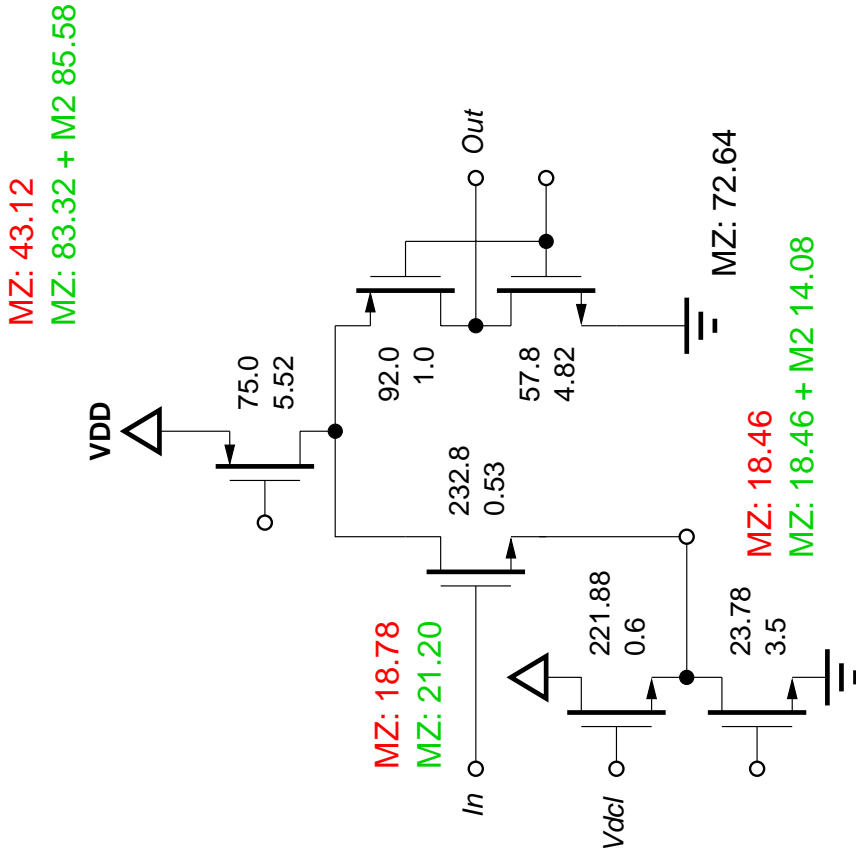


Power routing (Front-end)

 

vdda

gnda

this vdda-pad is on Beetle 1.2 connected to the front-end power

 

Beetle 1.2 readout with:

- pad connected to vdda
- pad not connected to vdda (comparable to Beetle 1.1)