Beetle1.2_MA0 submission

The multi-anode pmt (MApmt) tube is the back up solution for the LHCb RICH detector.

A readout chip is required to be able to collect and store signals from the MApmt in a LHCb specific way.

The Beetle chip from Heidelberg conforms to the LHCb specifications but cannot handle the large signal input from a MApmt.

Modifying the Beetle to be able to accept these signals is possible, but which is the best approach. A MPW will be submitted on the 2nd of December 2002 with a modified Beetle1.2 chip (Beetle1.2_MA0) which has three different front end amplifiers.

Introduction

MApmt specifications

The standard simulation test bed used.

A look at the various front end schematics.

A look at the various front end layouts.

Layout of the Beetle1.2MA0 chip and test points.

Can the Beetle pipe line accept the new dynamic range of the FE amp.

The layout checks that have been done.

Some first order simulations.

Beetle1.2 MA0 submission **Specifications for input pulse from MApmt** Single photon signal 300,000e- @ -800V Pmt capacitance 1.5pF without base Rise/Fall time 2ns baseline width 5ns Gain spread 3 (tube to tube 2, pixel to pixel 2) Signal/pedestal width 40:1 Dynamic range 9 (gain spread x 3 photons) Beetle noise figure $\sim 483e + 45.7e - /pF$ Assuming worse case 10pF load so work with noise ~1000e-Output of amp needs to be 30mV/photon to 270mV/9 photons

30/10/2002

Beetle1.2_MA0 submission

All simulations use the following values unless otherwise stated.

- 300,000e-/photon (delivered by a voltage step across a 3.2pF cap. Rt and Ft =0.1ns, pulse width 10us, Vpeak is -15mV for 300,000e-)
- All simulations done on a three channel segment with parasitic extraction and biased by the bias generator.

10pF load


Vfs=0V, Vfp=0V. This gives best rise time and input rate capabilities.

Vfs=0V, Vfp=405mV for the attenuator amp.

I-shape=78.8uA, I-pre=590.5uA, I-buf=78.8uA. From Beetle bias generators. Standard Beetle1.2 settings.


R=1M//C=1pF on output buffer to give pipeline loading.

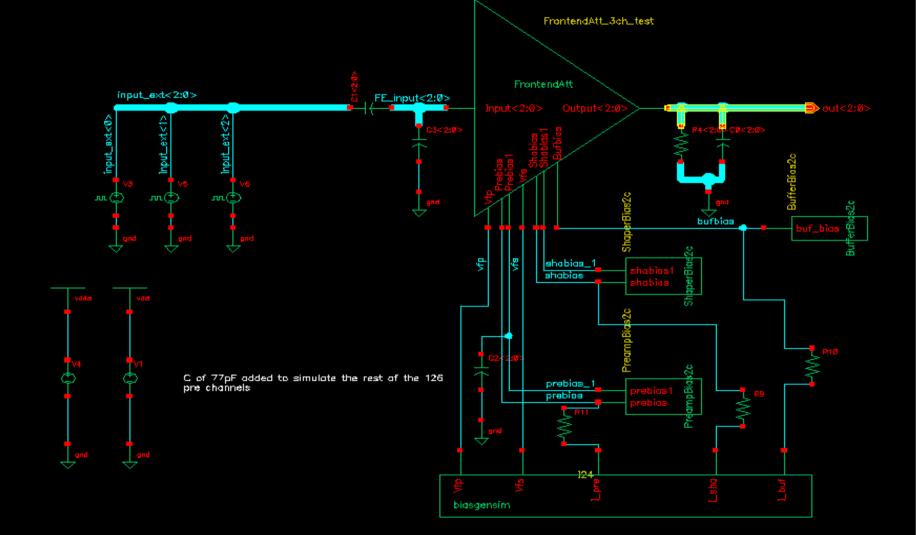A three channel simulation test bed, allows cross talk measurements.




30/10/2002

Standard Beetle1.2 Frontend

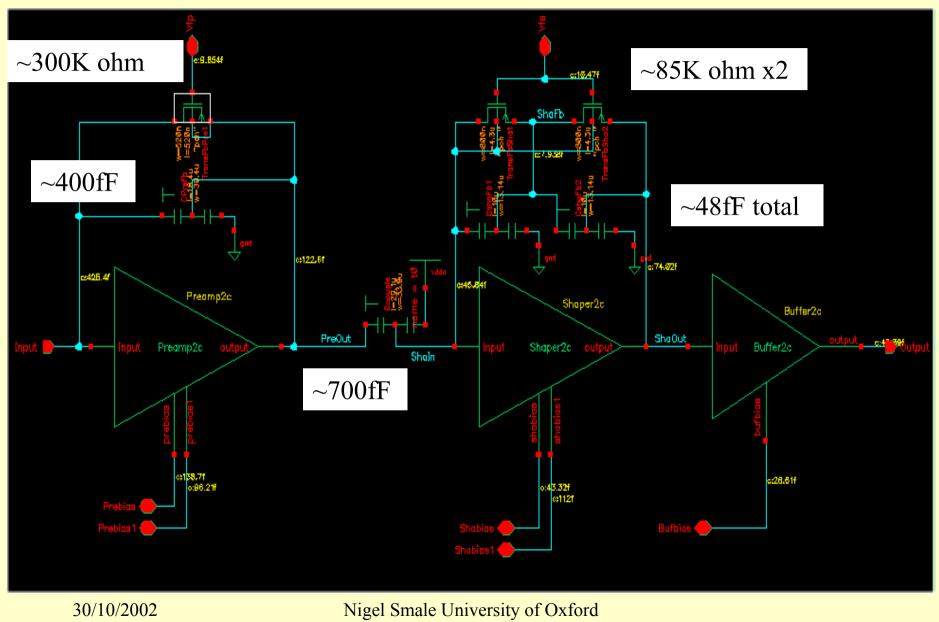


Beetle1.2MA0 FrontendDiv

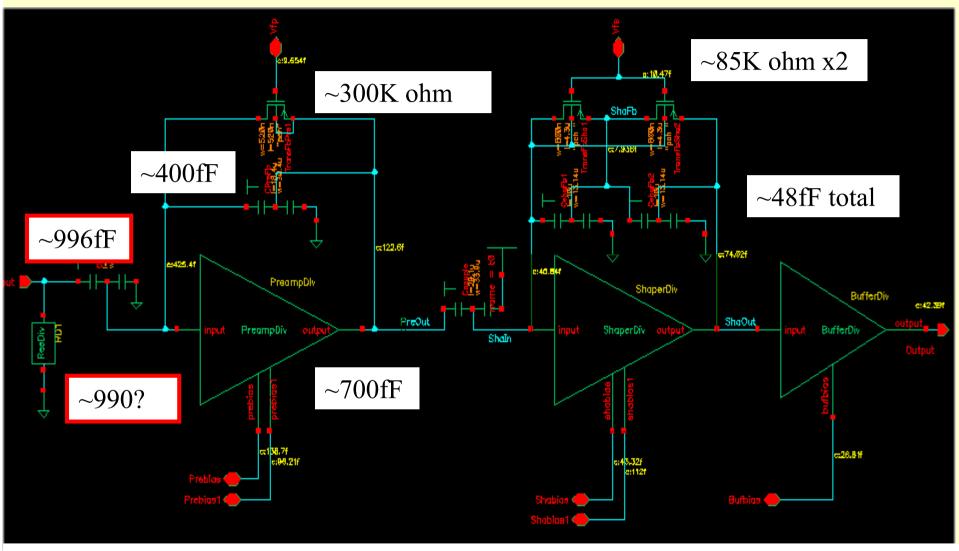

Red box means different to the standard Beetle1.2


30/10/2002

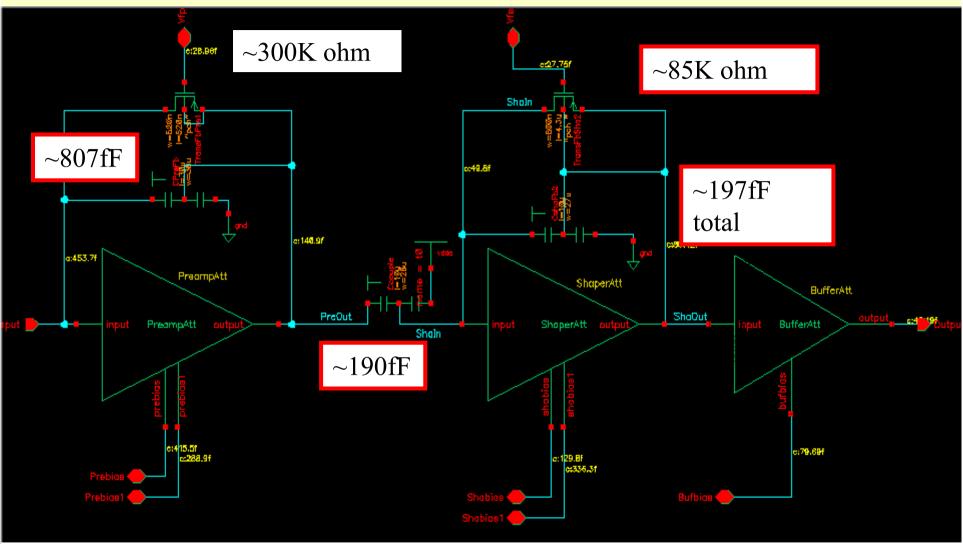


Red box means different to the standard Beetle1.2

30/10/2002


The folded cascode pre-amp

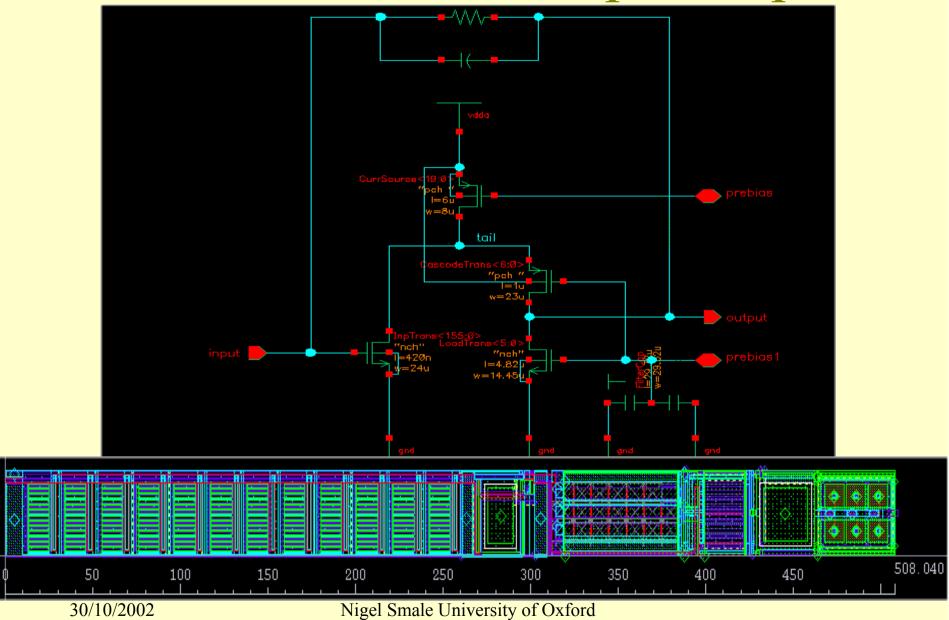




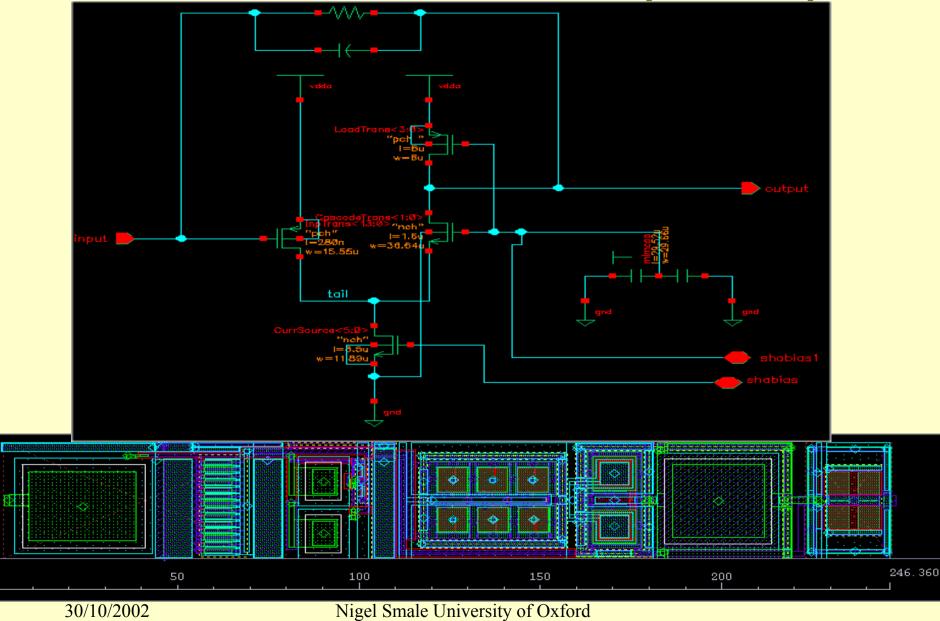


The source follower buffer

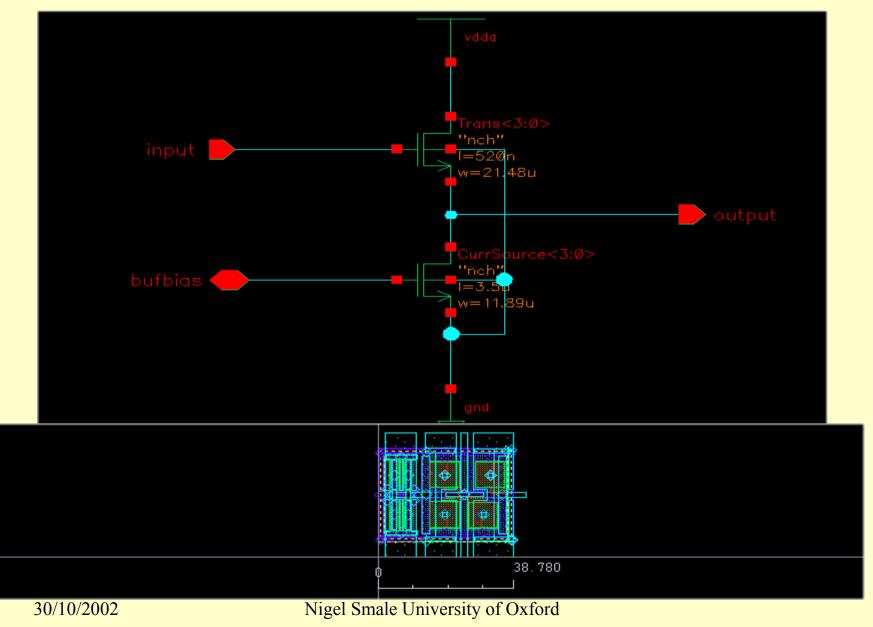

The layout of the three pre-amps

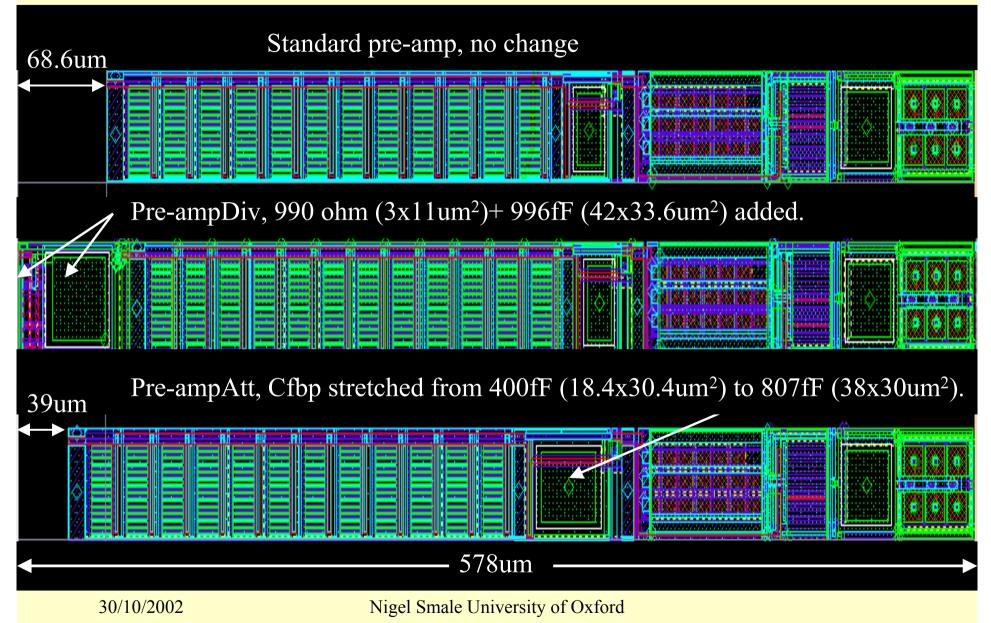


Zoom of the preampDiv RC network

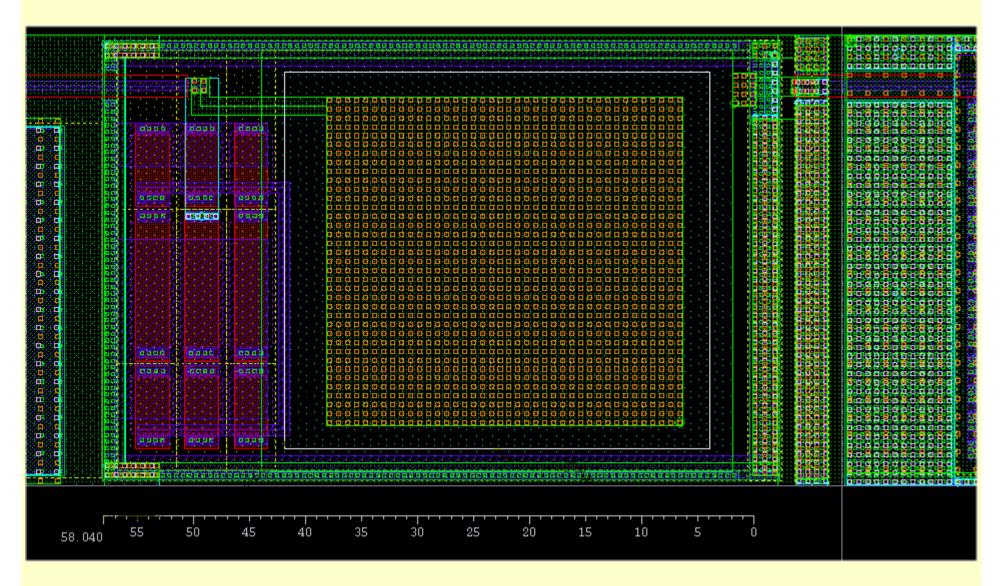

30/10/2002

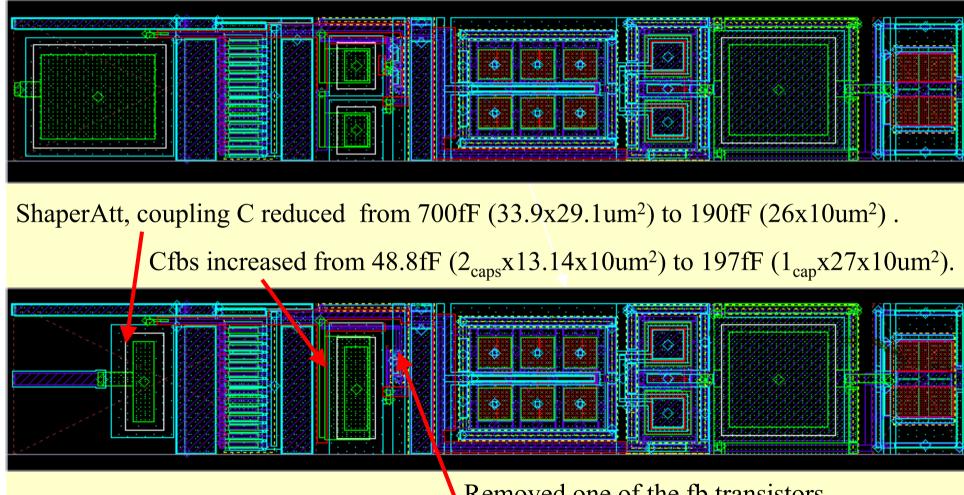
The layout of the three Shaper-amps Shaper & ShaperDiv have no change.



Removed one of the fb transistors

30/10/2002


Zoom of the shapampAtt mods

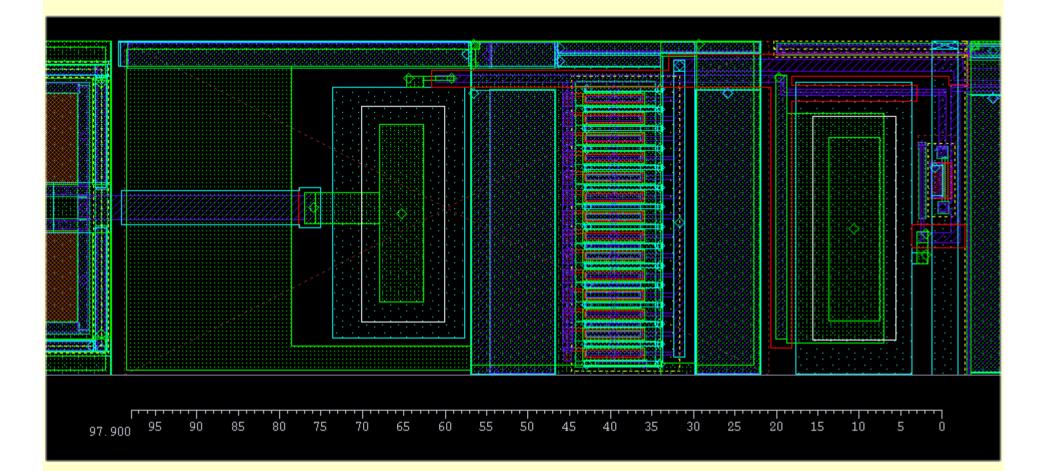


30/10/2002


Beetle1.2 MA0 Layout Scheme

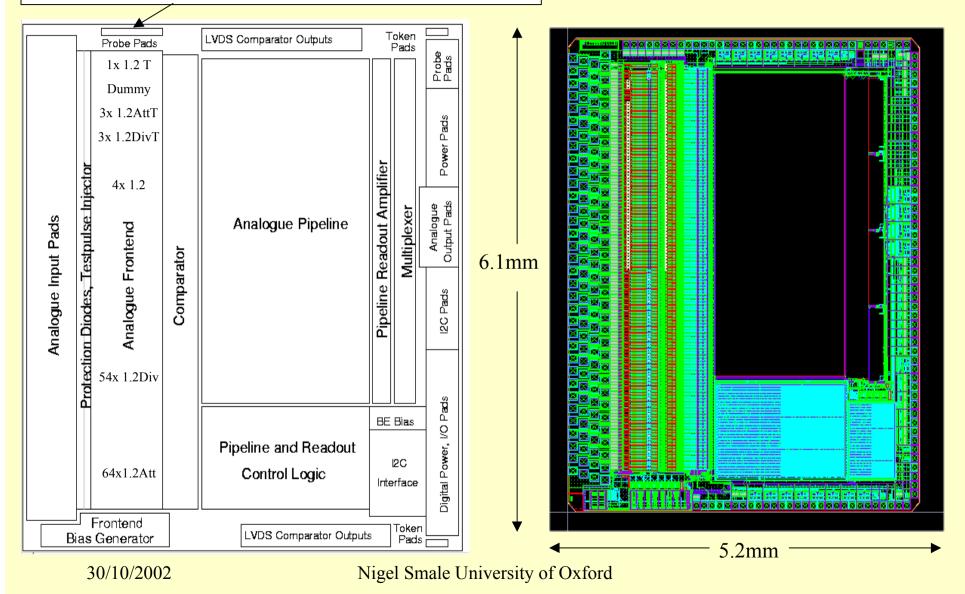Prebias, Prebias1, Shabias, Shabias1, Bufbias, Att_T, Div_t, 1.2_T




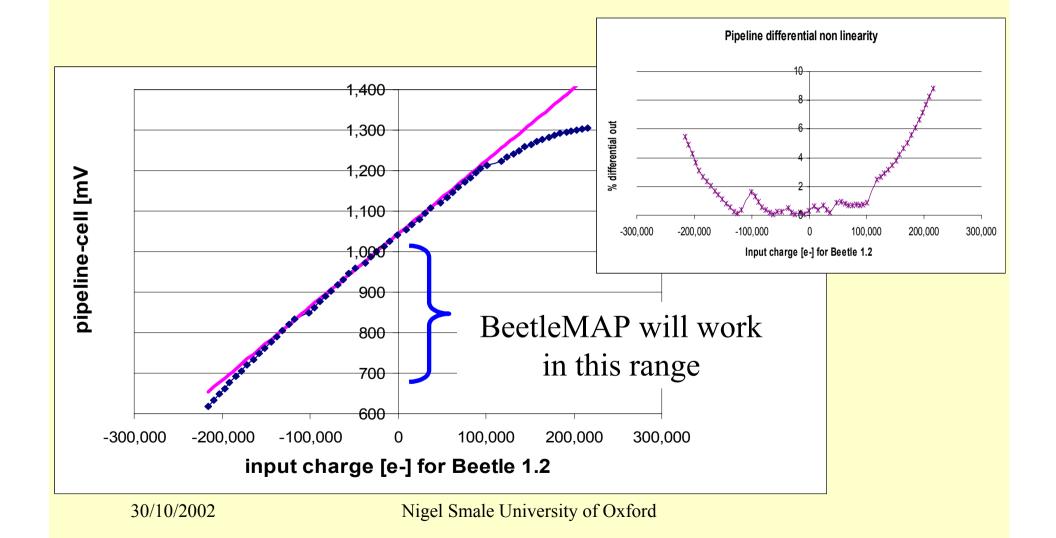
Dynamic input range of the Beetle1.2 pipeline. Plot created by Sven Loechner HD



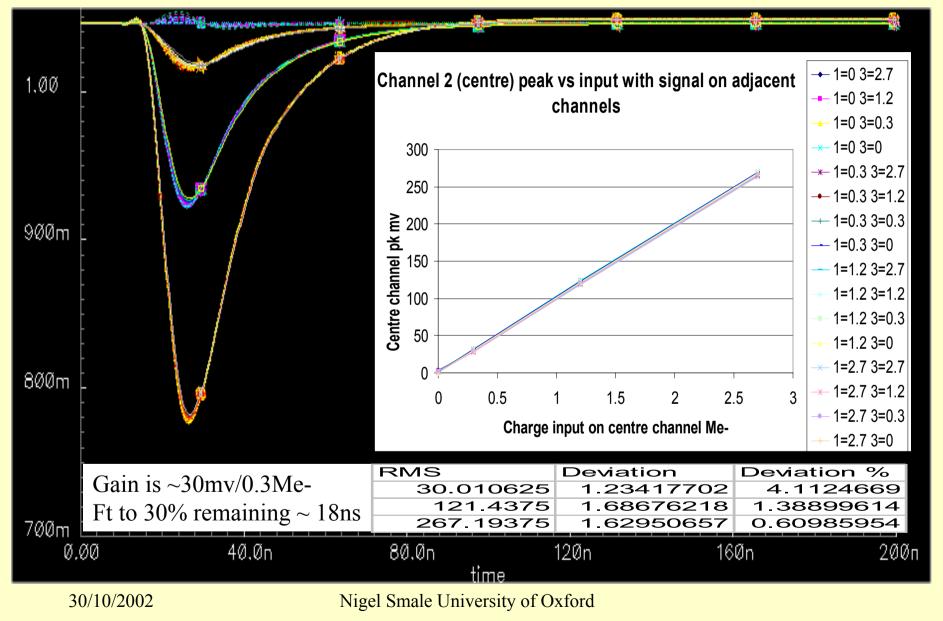


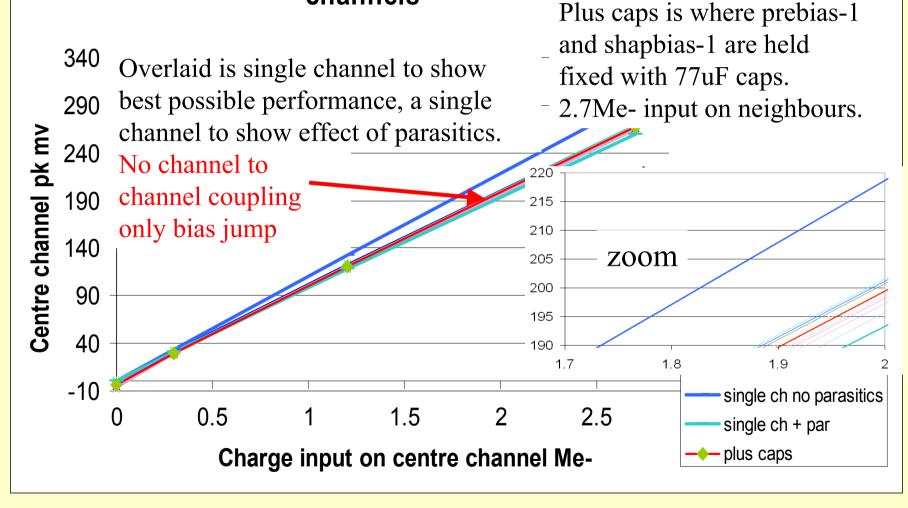Channel 2 (centre) peak vs input with signal on adjac channels




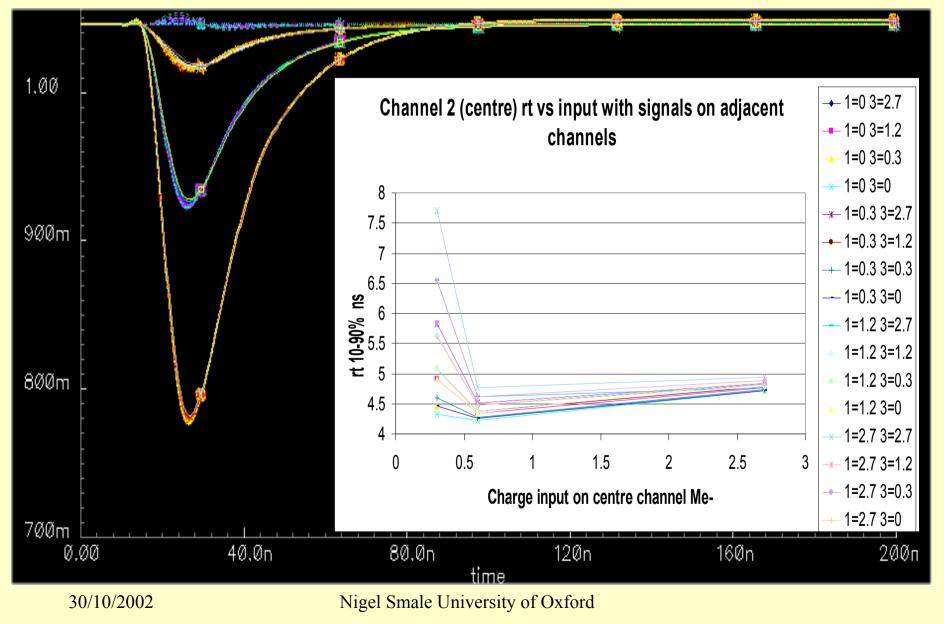


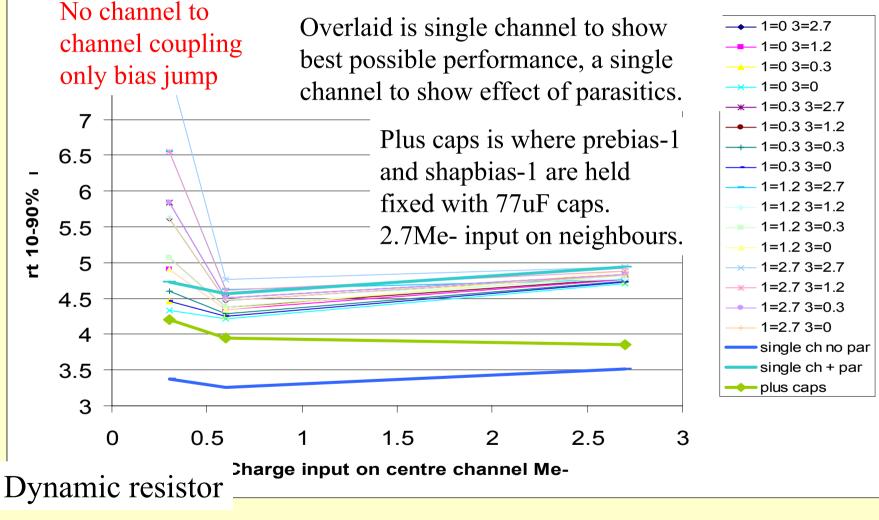
Channel 2 (centre) rt vs input with signals on adjacent channels





30/10/2002

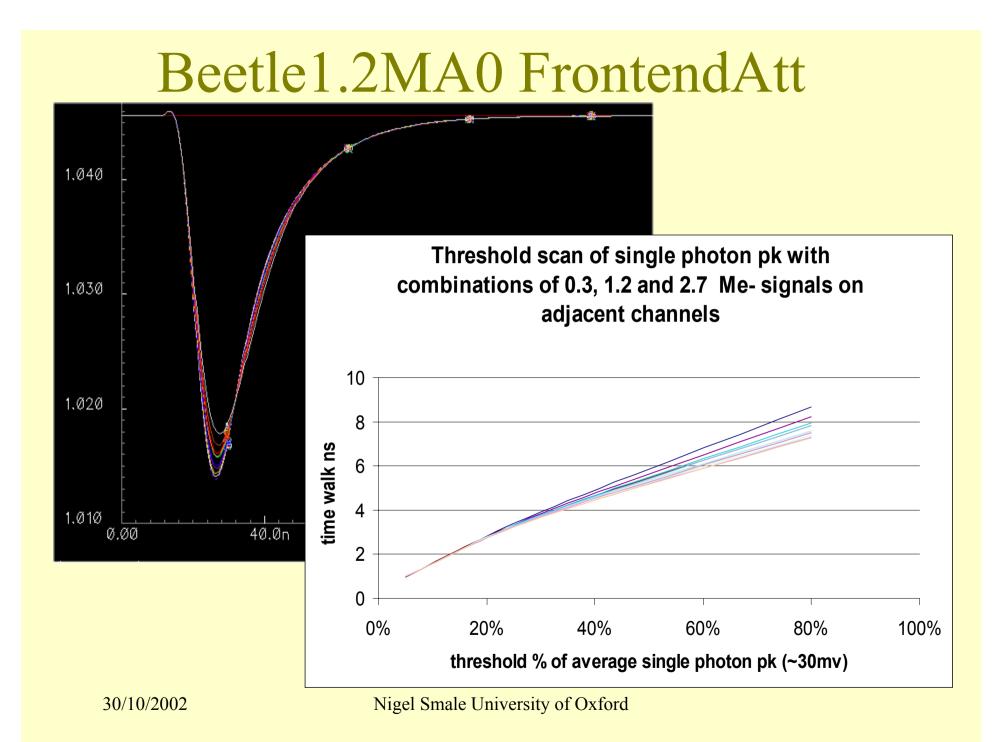


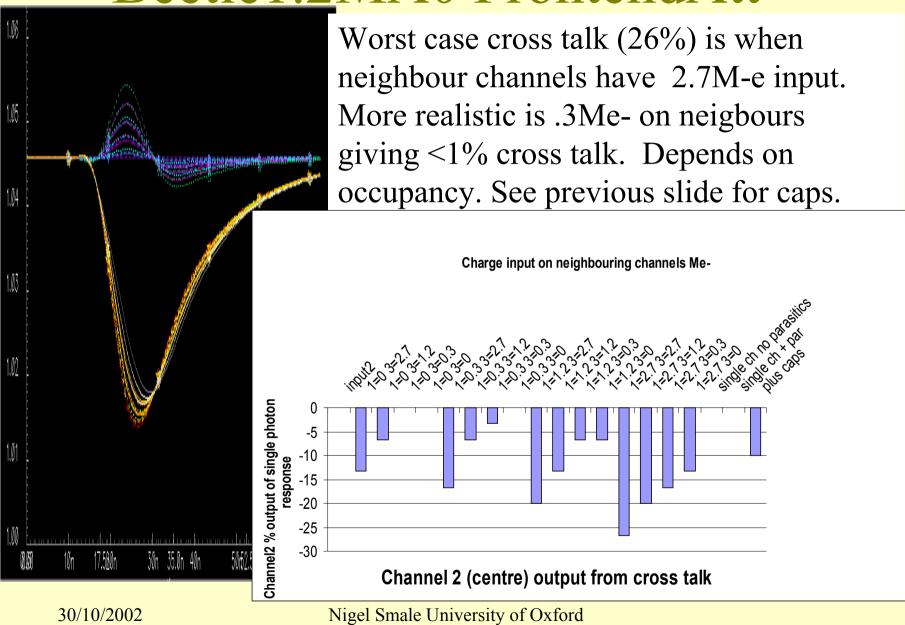

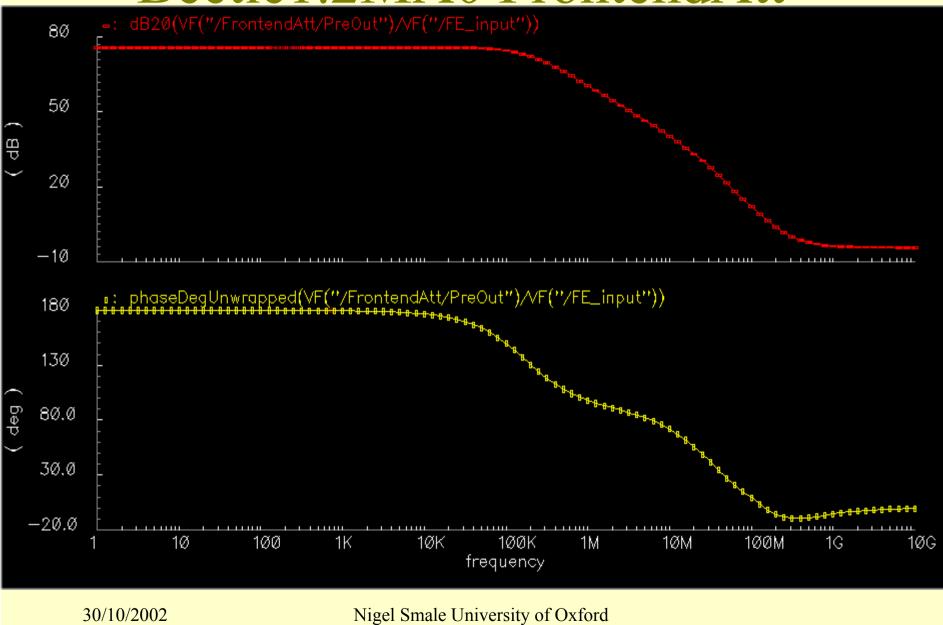

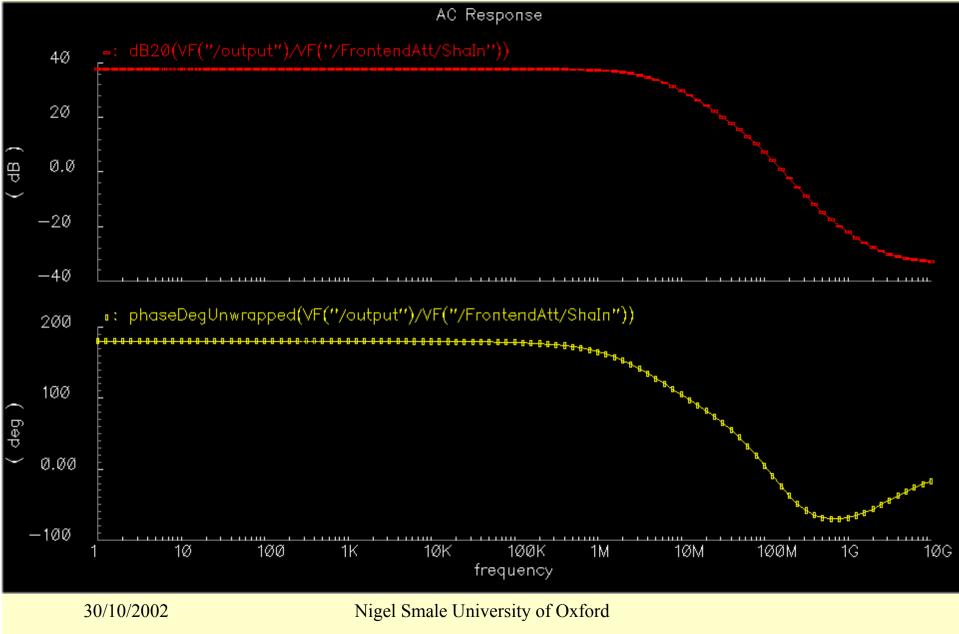


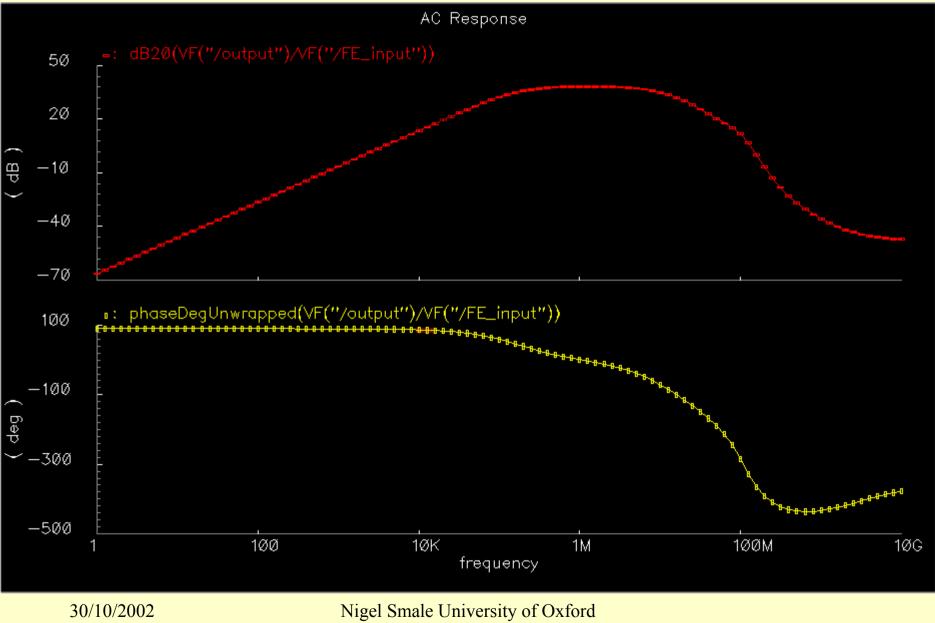

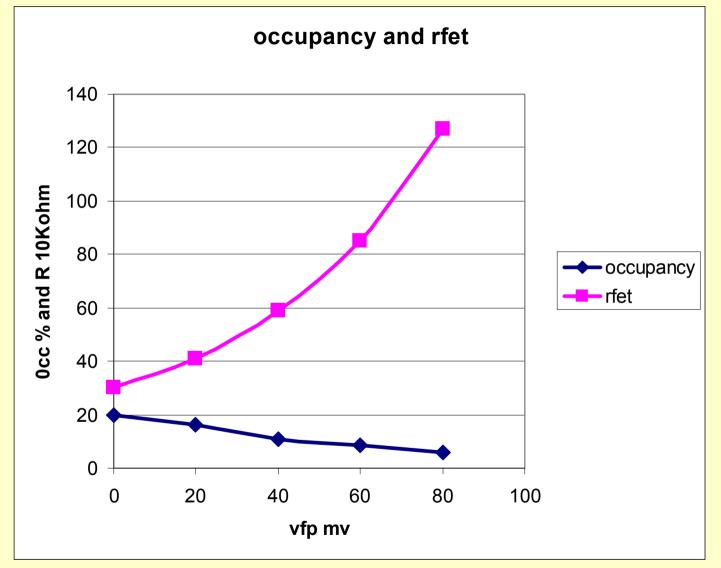



30/10/2002

Prebias-1 problem

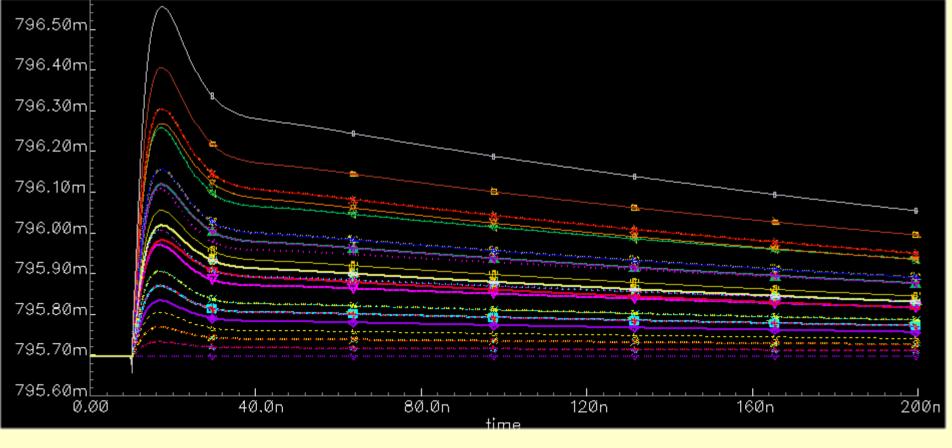


30/10/2002

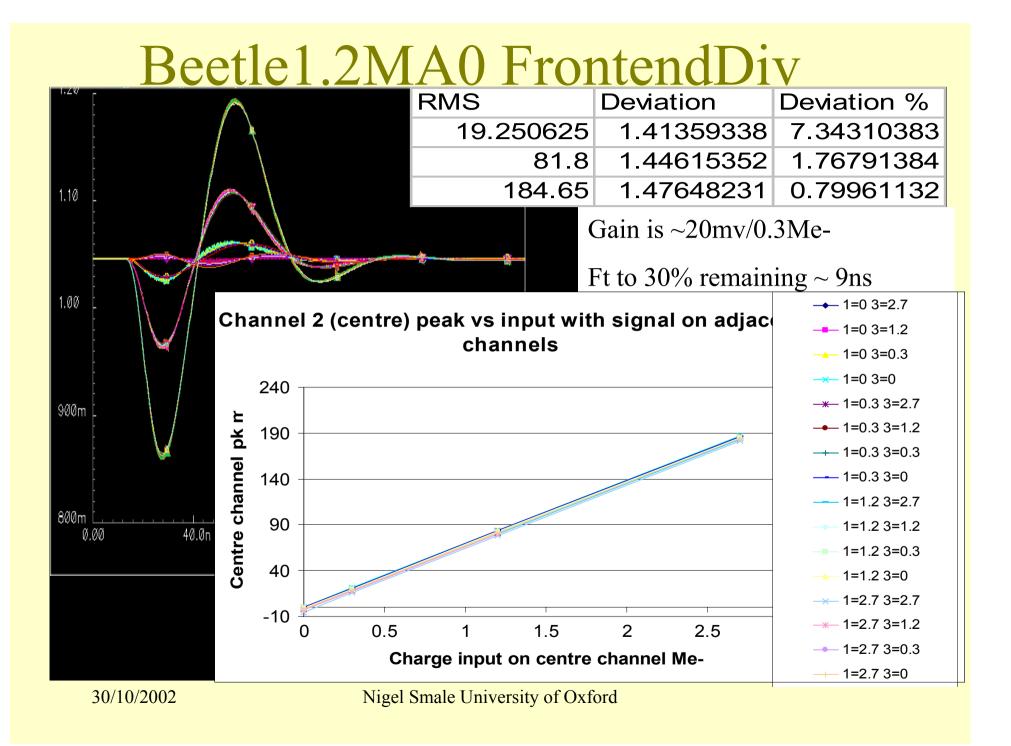

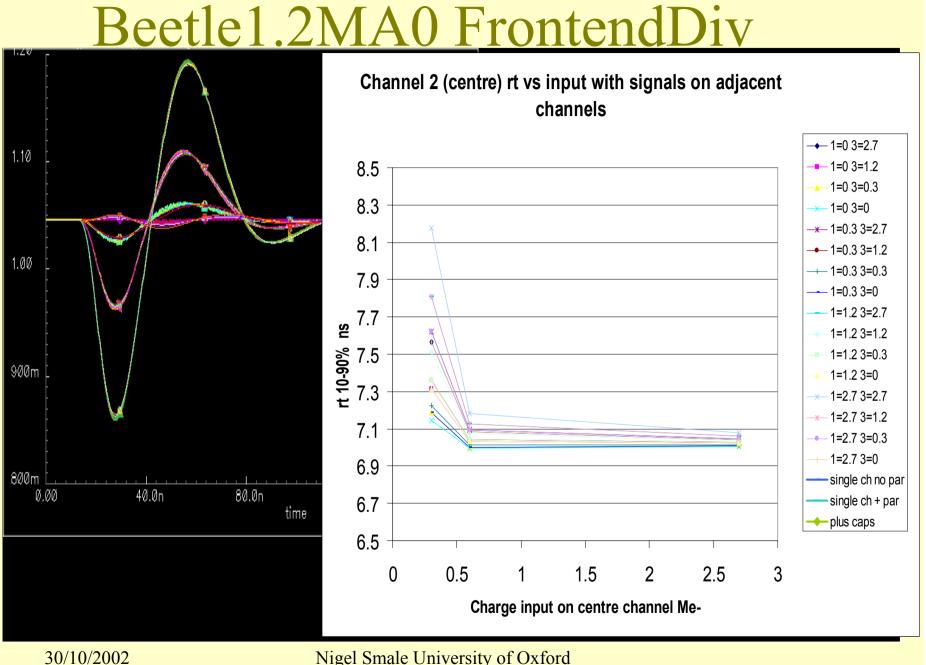


Beetle1.2MA0 layout checks

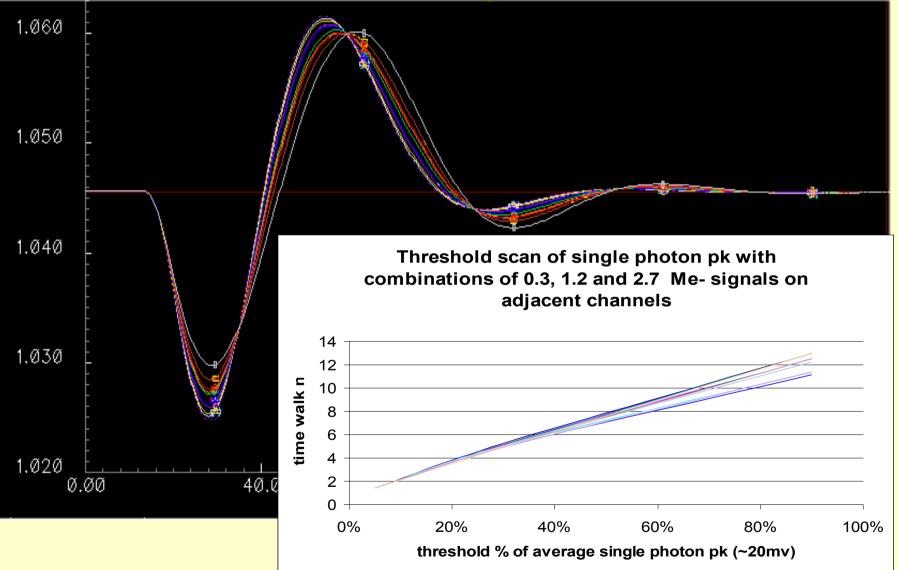


30/10/2002

Nigel Smale University of Oxford

Beetle1.2MA0 FrontendDiv

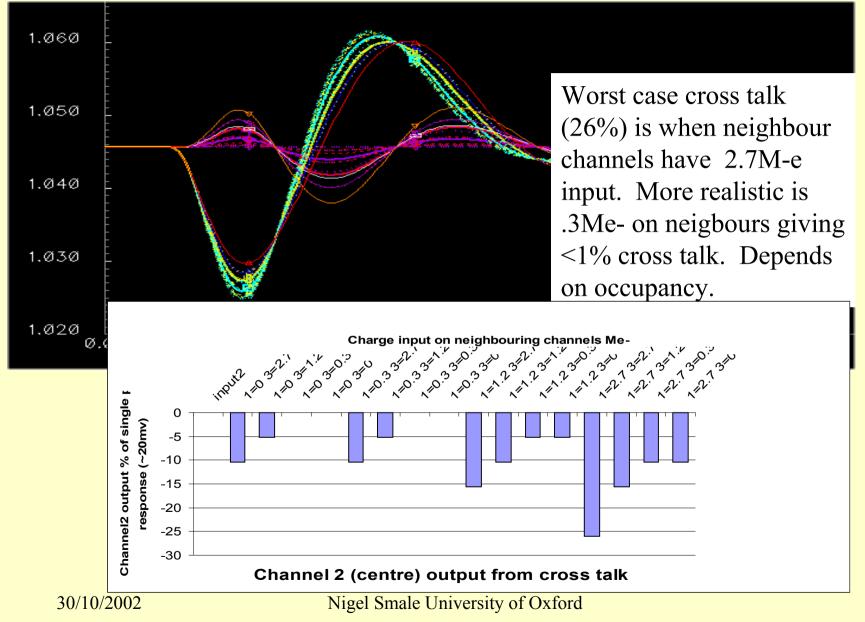


With and without Parasitic extraction

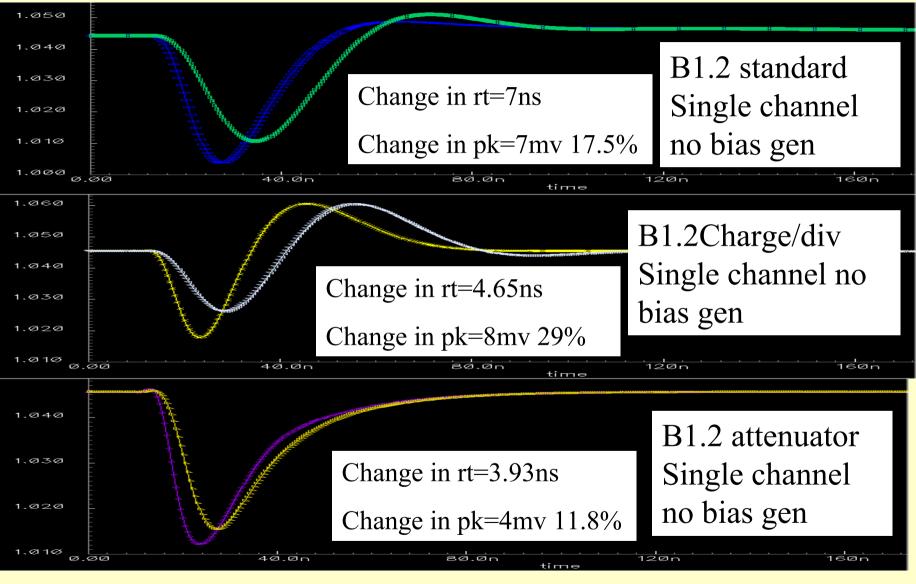

30/10/2002

The effect of changing pre-amp bias Vfs

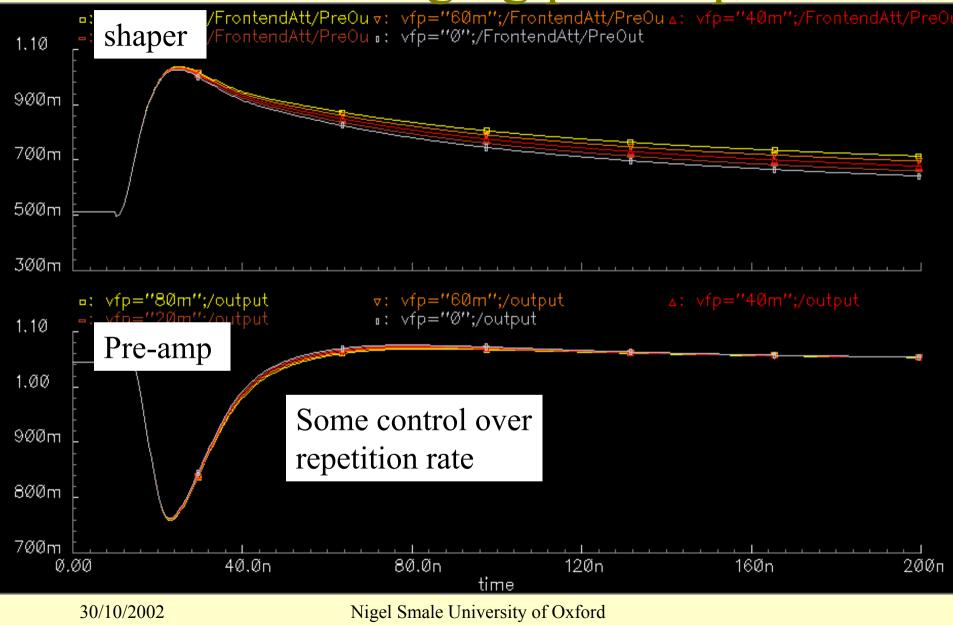

Beetle1.2MA0 layout checks

Three adjacent channels for both Div and Att have passed DRC, extraction and LVS.

Simulations look o.k for a first order for both, and are as expected.

Sven has incorporated these into a full chip structure, and completed extraction and LVS. Since this time the Div has had a modification made to the resistor block. The resistor has been surrounded by dummies.


Sven will do another full test when he is back and generate the gdsII file.

Consideration of changing a track width.


There was one warning in the DRC.

30/10/2002

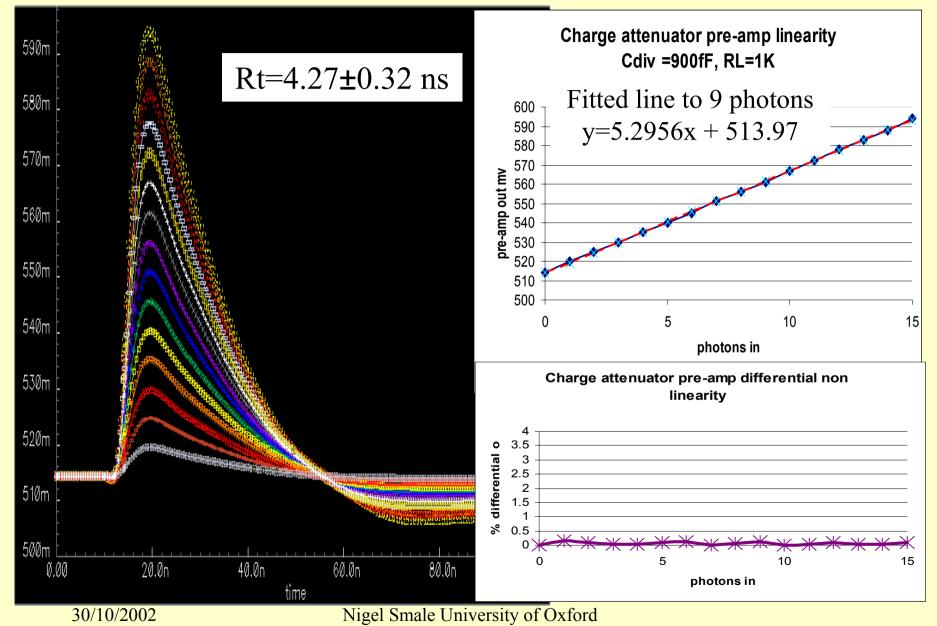
Charge attenuator Pre-amp, RL=1K,Cdiv=900fF,



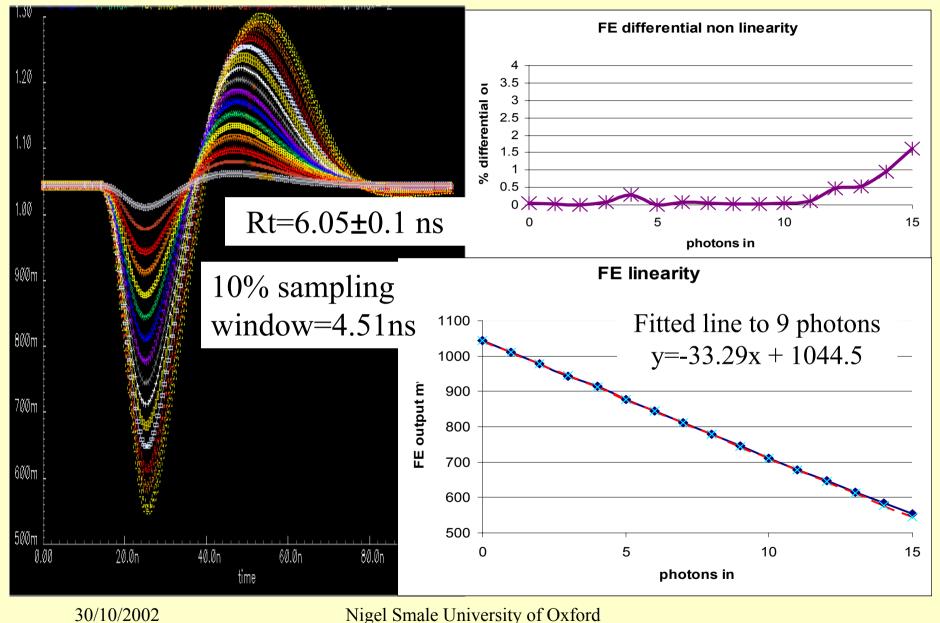
Charge attenuator FE-amp, RL=1K,Cdiv=900fF,




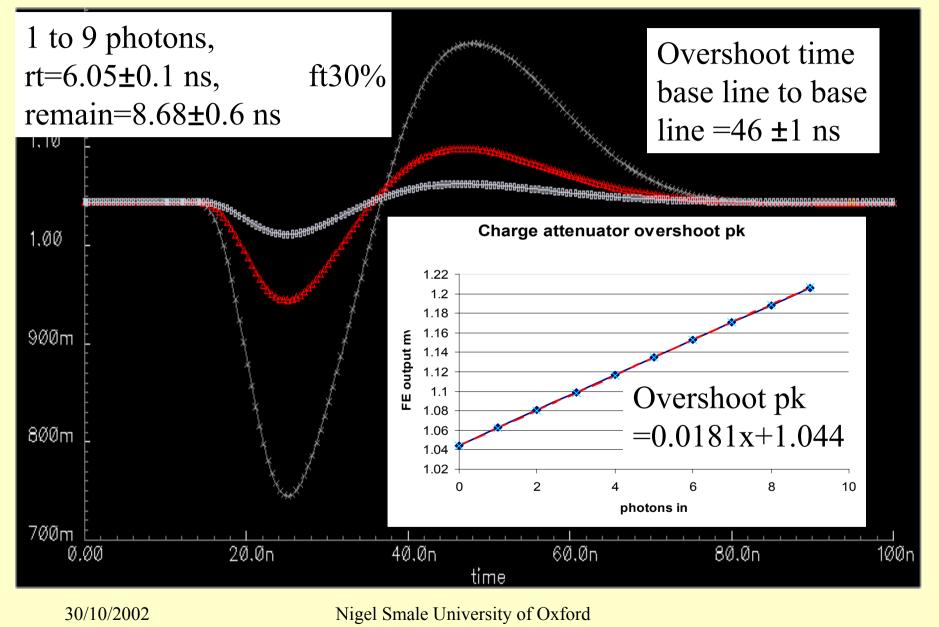Charge attenuator FE-amp, RL=1K,Cdiv=900fF,




The effect of load capacitance

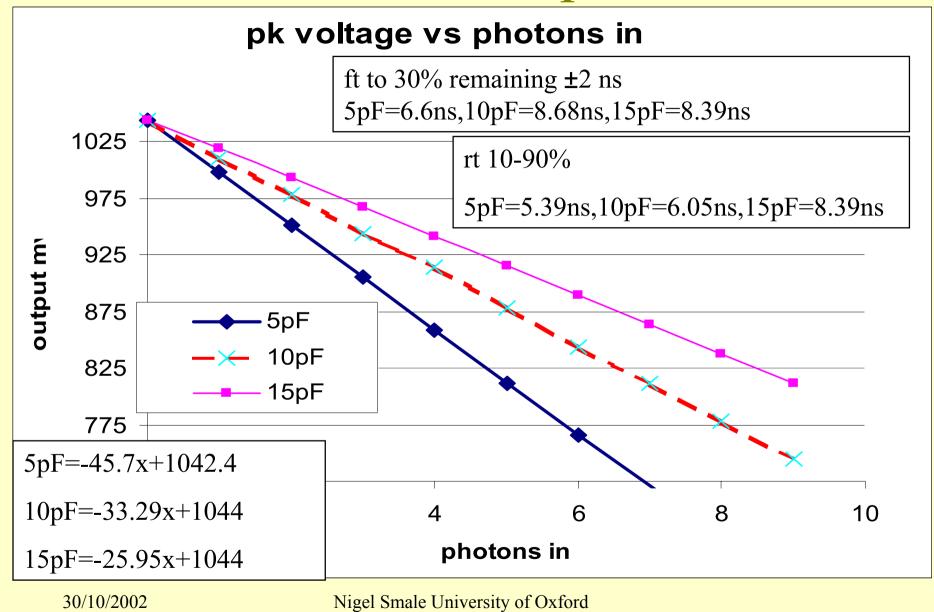

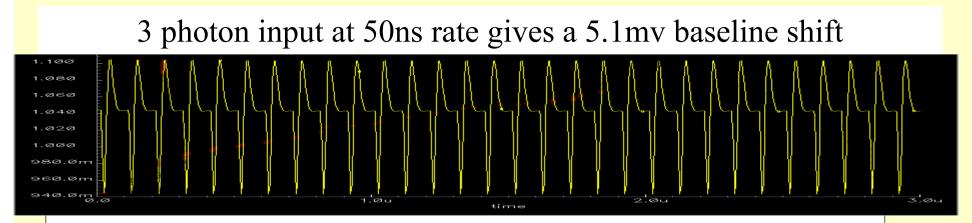


Rate capabilites measured at 2us 6 5 4 () baseline З 1 photon 2 photon 2 - 3 photon 1 Ο 100 200 300 400 M -1 Input rate ns

30/10/2002

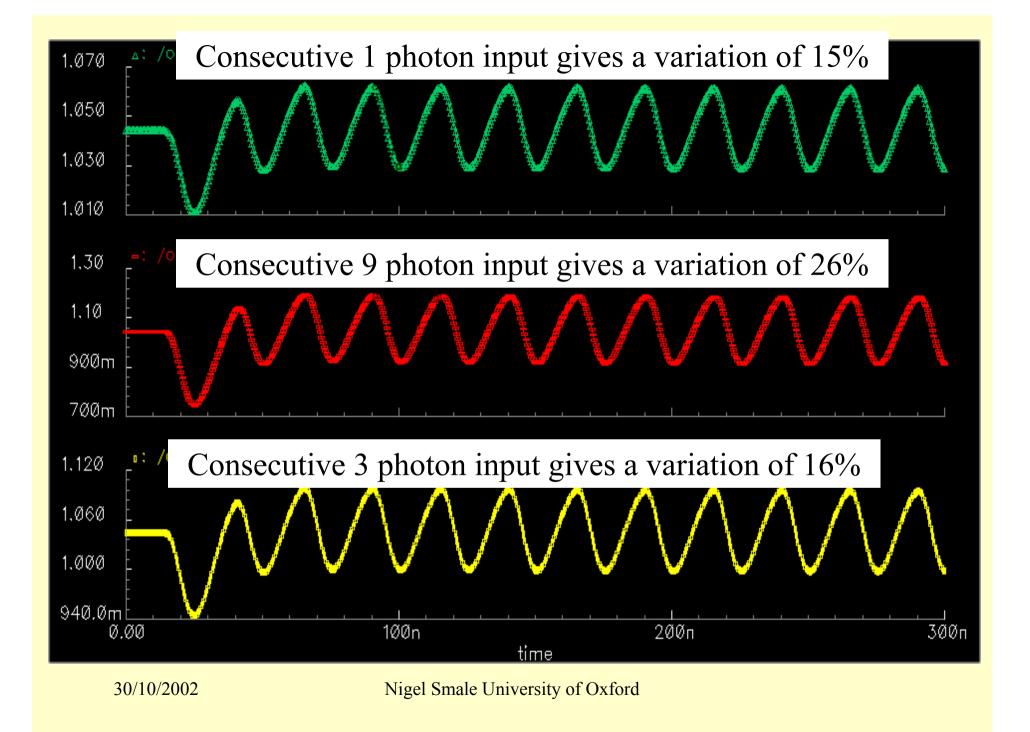


The Cpre,Cd and Cshap mod FE

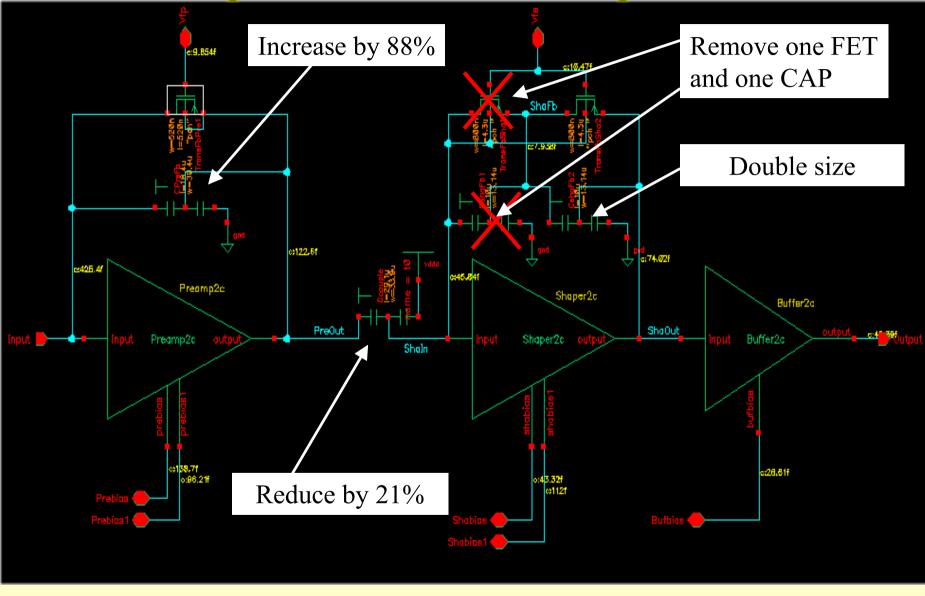


Nigel Smale University of Oxford

30/10/2002


In layout terms

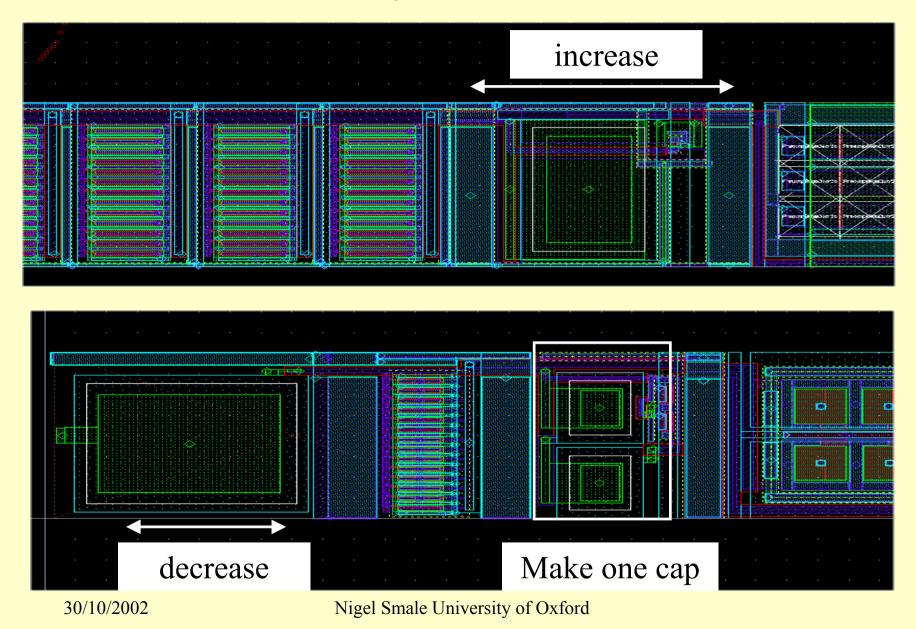

The pre-amp and shaper output

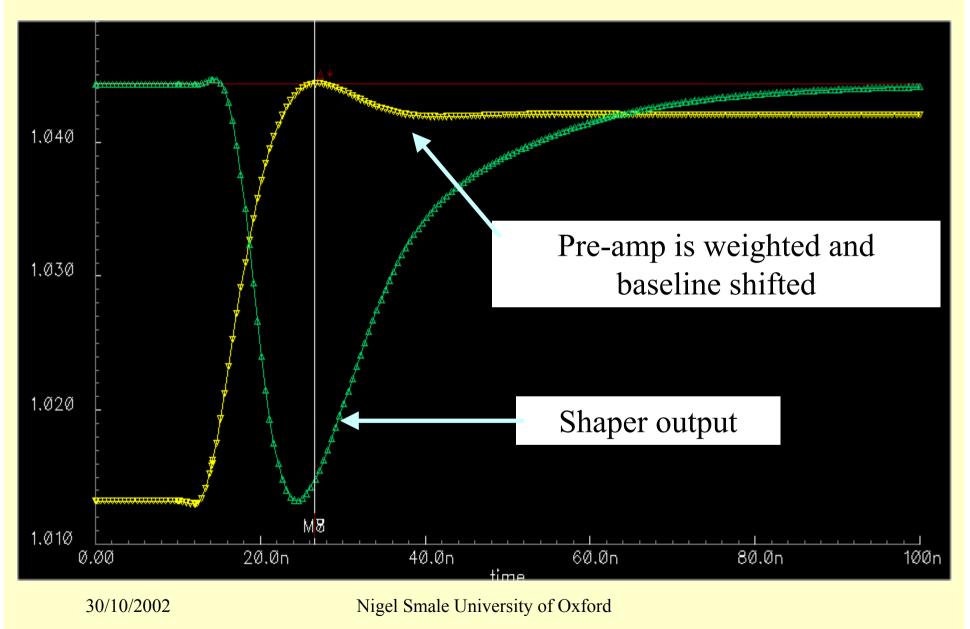

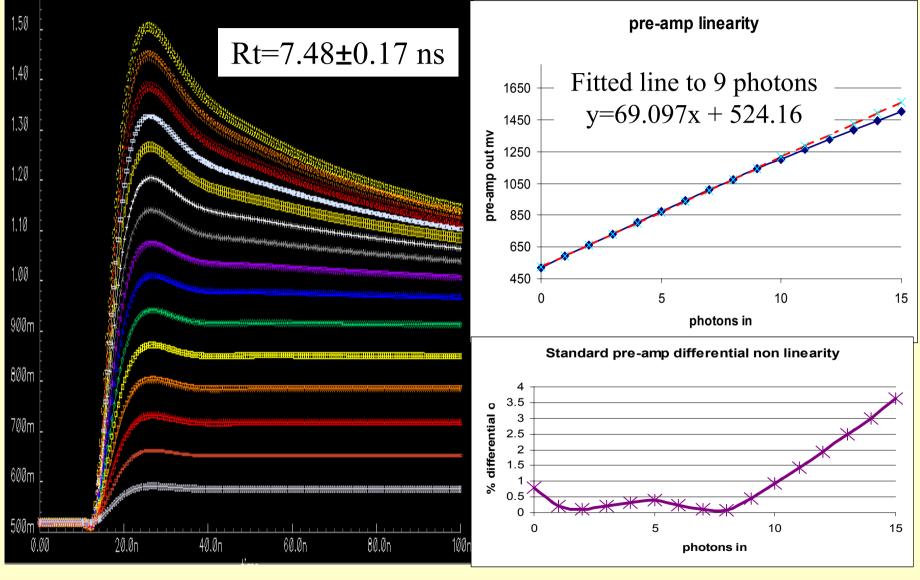
Pre-amp, vfp=400mv,Cfp=735fF,Cfs=192fF,Cd=147fF




30/10/2002

Nigel Smale University of Oxford

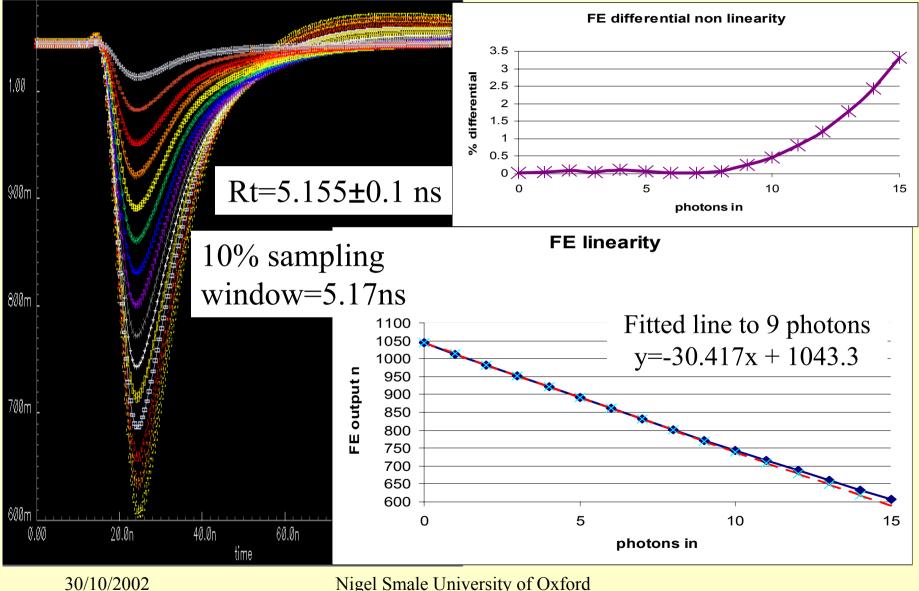FE-amp, vfp=400mv,Cfp=735fF,Cfs=192fF,Cd=147fF



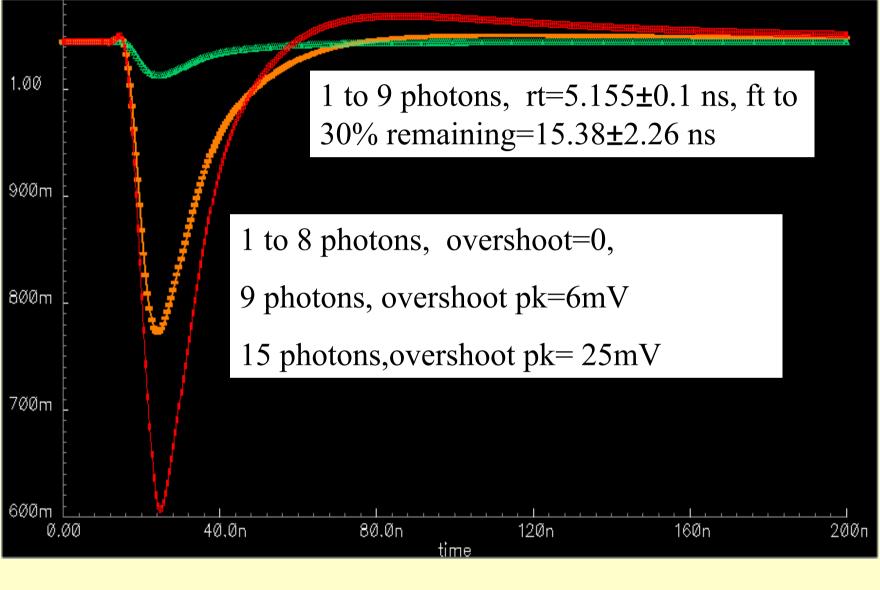FE-amp, vfp=400mv,Cfp=735fF,Cfs=192fF,Cd=147fF




Nigel Smale University of Oxford

30/10/2002


The effect of load capacitance

pk voltage vs photons in

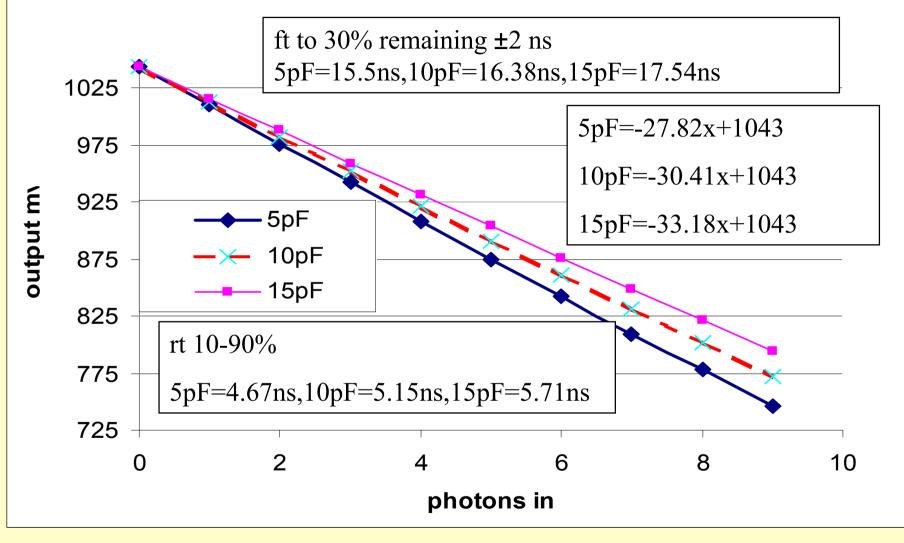



30/10/2002

The effect of changing shaper bias Vfs

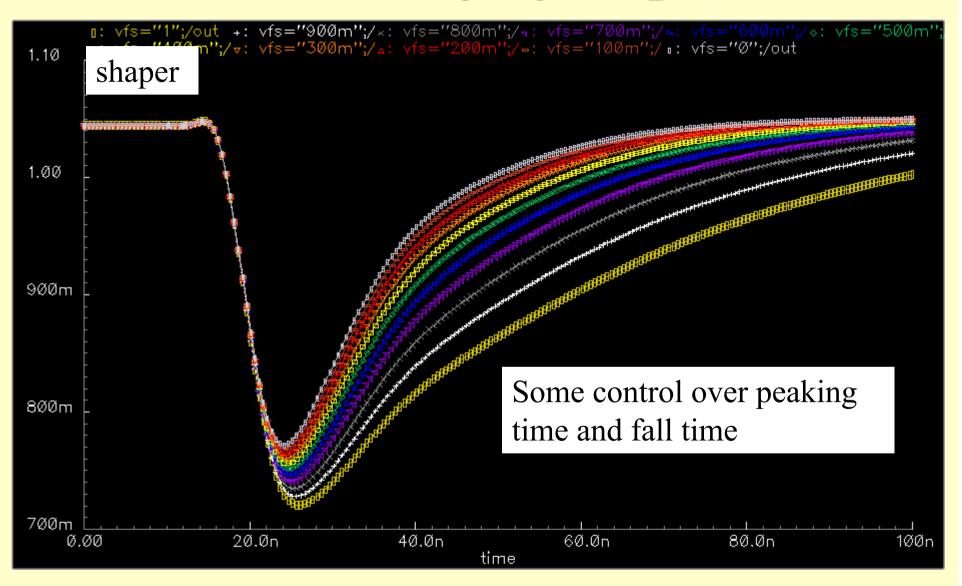

30/10/2002

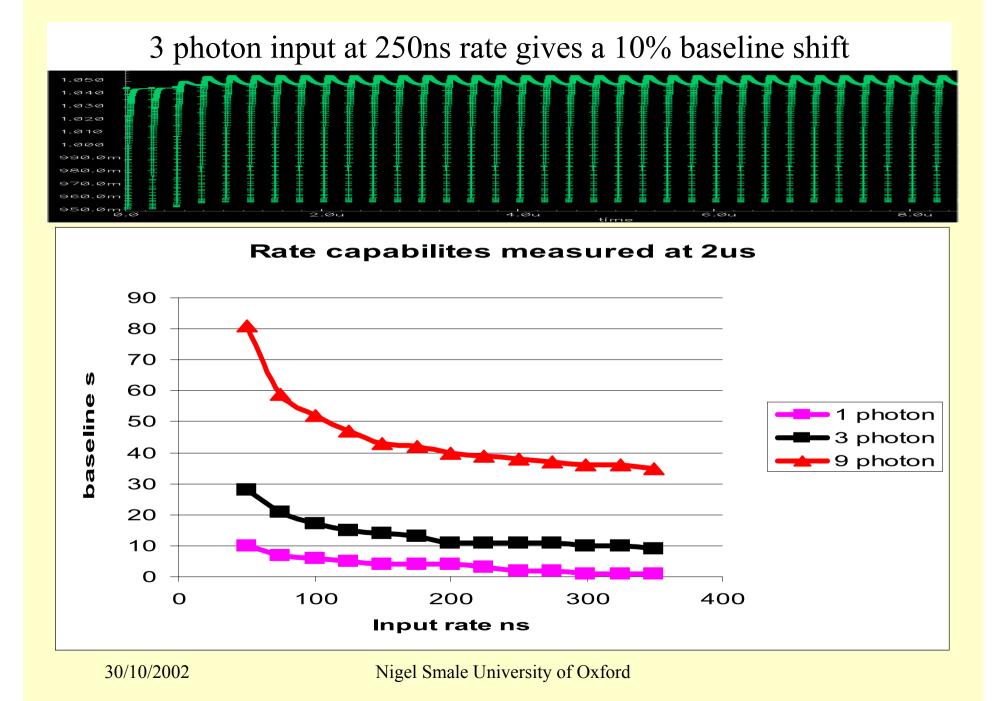

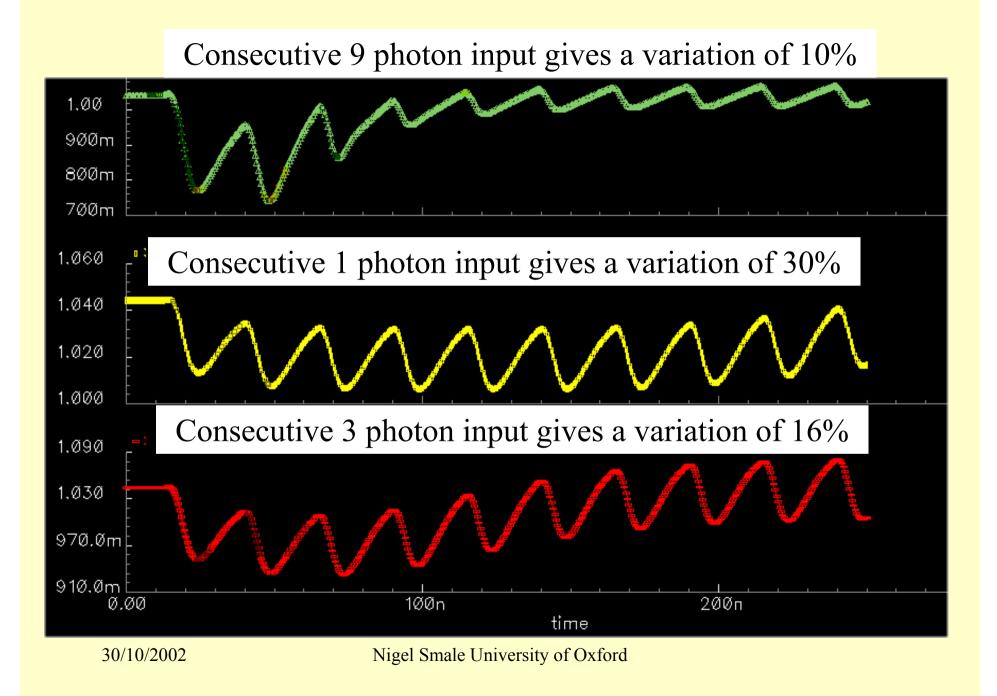

Conclusions and questions outstanding

•Beetle1.2 is in good condition, other than bug in control logic. Should we submit with new or old logic.

•Only three amplifiers are worth considering for the RICH option

The preferred is the C modified FE, the charge division is a definite contender if ac coupling is required, the op-amp needs consideration.

•Detailed study of how these amplifiers really fit into the rest of the Beetle1.2 architecture now needs to be studied. Real parasitic capacitance and inductance needs to be added to simulation when layout is complete.


•Detailed look at the binary comparator compatibility with the new amps needs to be studied.

30/10/2002




30/10/2002

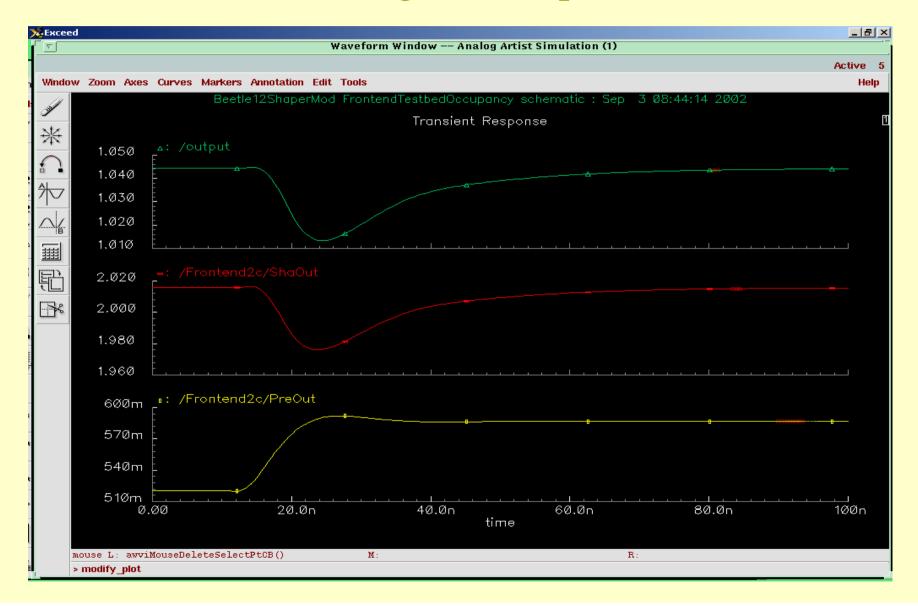For the shaper mod with vfb at 400mv etc, put here because interesting that shaper out is at 2v




Reference FE pre-amp

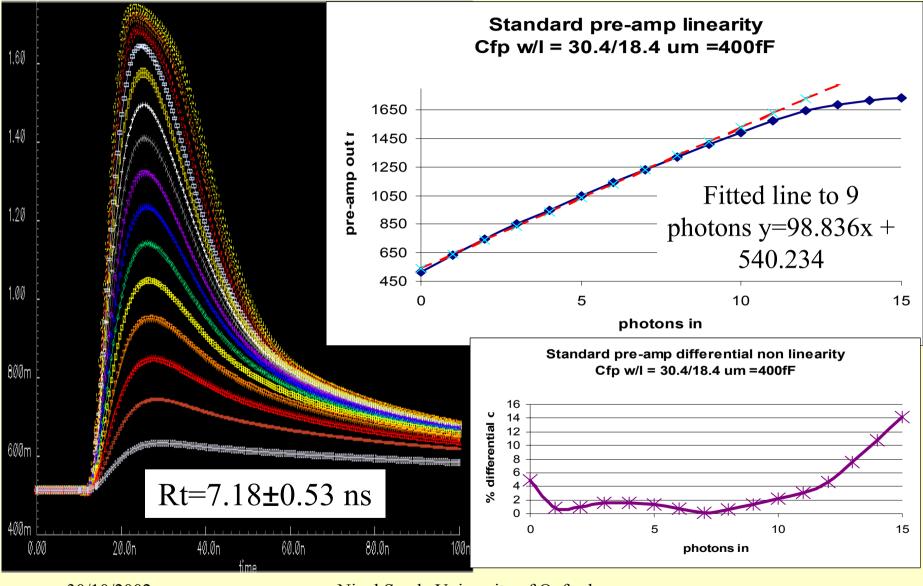


30/10/2002

Cfb made larger on Pre-amp

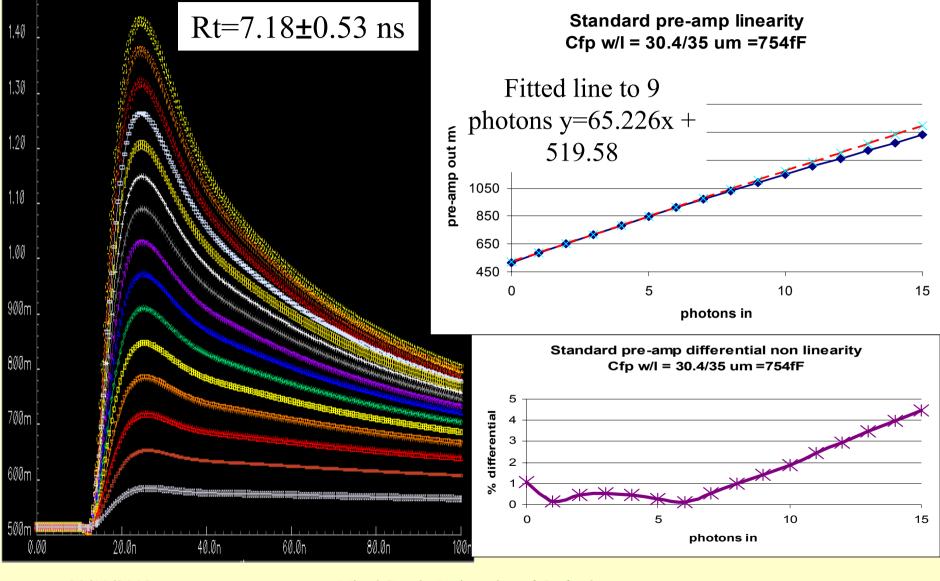


30/10/2002

Buf-amp with Cd & Cfs adjusted

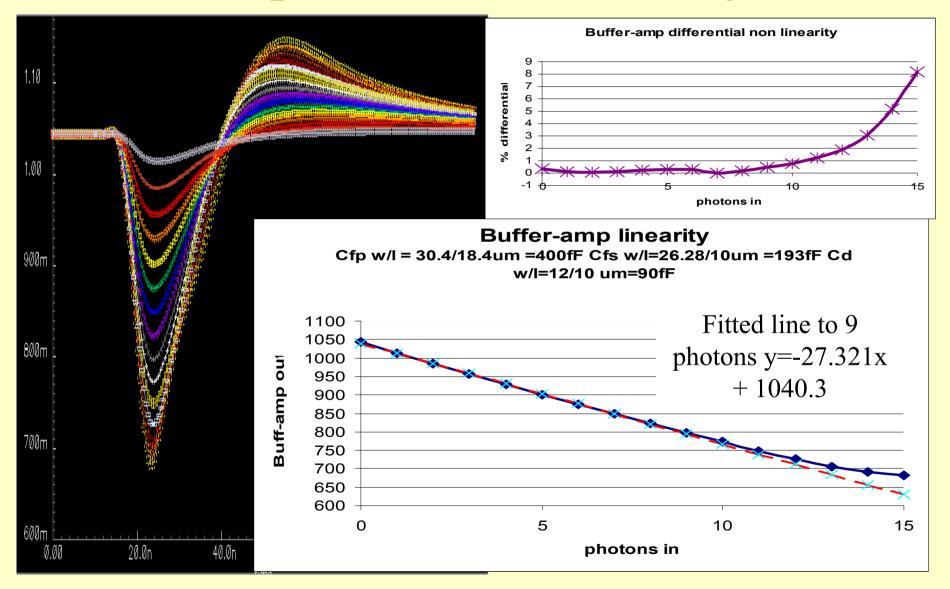

30/10/2002

Buf-amp with Cfp, Cd & Cfs adjusted

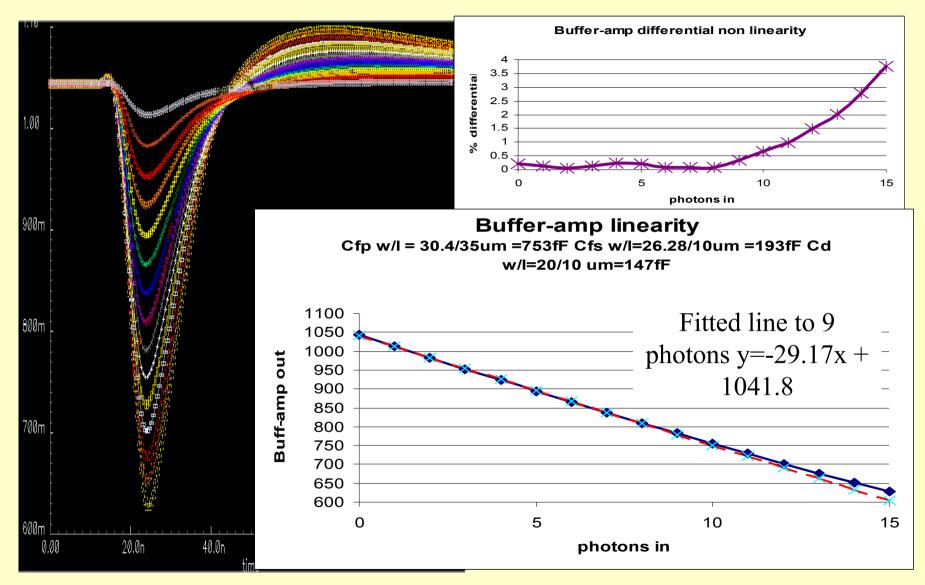

30/10/2002