

Advanced Analog Building Blocks

Differential amplifiers



Albert Comerma (PI)
(comerma@physi.uni-heidelberg.de)



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386



[Course web](#)

SoSe 2017

- **Next lectures after holidays:**

- 25.5 → lecture Friday 26th
- 15.6 → lecture Friday 16th
- Should we proceed as normal days (attendance)?
- Run some more cadence lab on one of those days?

Introduction: Miller Effect

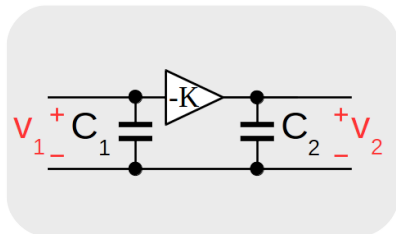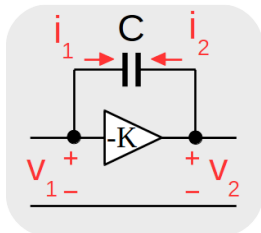

$$i_1 = \frac{v_1 - v_2}{Z} = \frac{v_1 + K v_1}{Z} = \frac{1+K}{Z} v_1$$

$$\frac{v_1}{i_1} = \frac{Z}{1+K} = \frac{1}{(1+K)C_s}$$

$$i_2 = \frac{v_2 - v_1}{Z} = \frac{v_2 + \frac{v_2}{K}}{Z} = \frac{1 + \frac{1}{K}}{Z} v_2$$

$$\frac{v_2}{i_2} = \frac{Z}{1 + \frac{1}{K}} = \frac{1}{(1 + \frac{1}{K})C_s}$$

$$C_1 = (1 + K) C$$

$$C_2 = (1 + \frac{1}{K}) C$$


for $K \gg 1 \rightarrow C_1 \gg C$, $C_2 \approx C$

Caution!

Miller effect is usually calculated for $K(\omega)$ at medium frequencies. Extrapolation to high frequencies produces error.



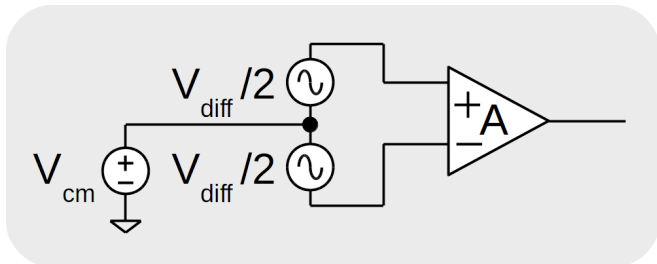Introduction: Differential amplifier key elements




- Two terminals input (differential).
- Flexibility in configuration / feedback options (OPamp).
- **Common mode**: DC voltage present at both inputs.
- **Differential input**: small signal present at input: $V_+ - V_-$
- **Common Mode Rejection Ratio, CMRR**: immunity to changes in common mode.
- **Power Supply Rejection Ratio, PSRR**: immunity to changes in power supply.



The Differential Pair: circuit basics

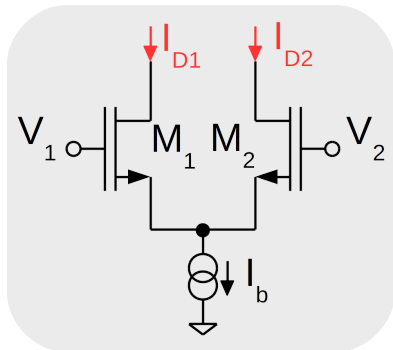- Usually a difference of voltages need to be amplified.




Differential voltage:

$$V_d = V_1 - V_2$$

Common-mode:

$$V_c = \frac{V_1 + V_2}{2}$$
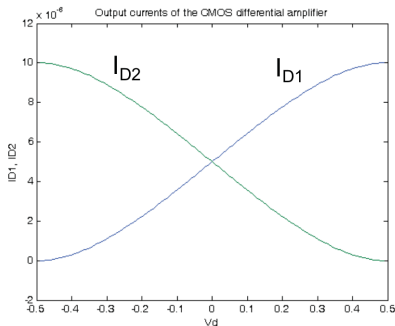
$$V_1 = V_c + \frac{V_d}{2}, \quad V_2 = V_c - \frac{V_d}{2}$$



Assuming both in saturation:


$$V_1 = V_2 \rightarrow I_{D1} = I_{D2} = \frac{I_b}{2}$$

$$V_1 \gg V_2 \rightarrow I_{D1} \approx I_b \rightarrow I_{D2} \approx 0$$



The Differential Pair: small signal analysis

- Intrinsic gain in differential mode.

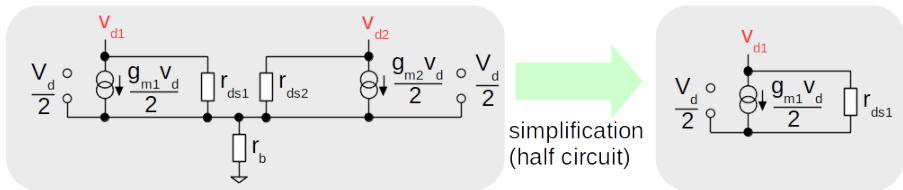

$$A_{V1} = \frac{v_{d1}}{v_d} = \frac{-g_{m1} r_{ds1}}{2}$$



Transconductance amplifier (voltage to current conversion);

$$g_1 = \frac{i_{d1}}{v_d} = \frac{g_{m1}}{2}$$

Caution!

Devices must be kept in saturation.

Amplifier configurations: active load

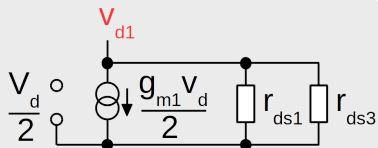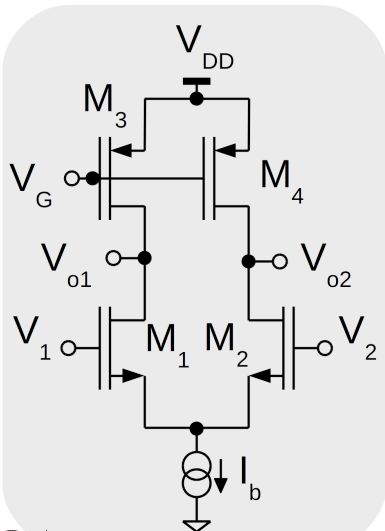

$$Av_1 = \frac{v_{o1}}{v_d} = \frac{-g_{m1}(r_{ds1} // r_{ds3})}{2} = \frac{-g_{m1}}{2(g_{o1} + g_{o3})}$$

Assuming $M_1 = M_2, M_3 = M_4$ then
 $g_{m1} = g_{m2}, g_{o1} = g_{o2}, g_{o3} = g_{o4}$ the
differential gain is;

$$Av_d = \frac{v_{o2} - v_{o1}}{v_d} = \frac{-g_{m1}}{g_{o1} + g_{o3}}$$


Caution!

V_G must guarantee that $I_{D3} + I_{D4} = I_b$



Amplifier configurations: common mode gain

- Intrinsic gain in differential mode.

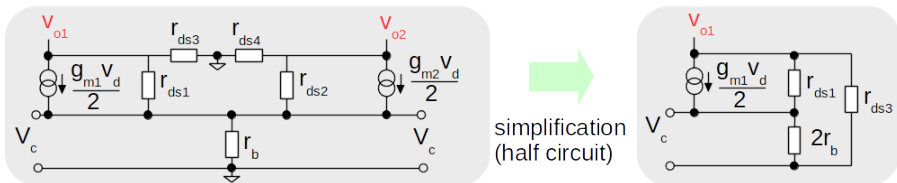

Neglecting the current flow in r_{ds1} ;

$$A_{V_{c1}} = \frac{V_{o1}}{V_c} \approx \frac{-g_{m1} r_{ds3}}{1 + 2g_{m1} r_b}$$

Amplifier configurations: CMRR

$$CMRR = \left| \frac{A_{v_d}}{A_{v_{c1}}} \right| = \frac{-g_{o3}(1+2g_{m1}r_b)}{2(g_{o1}g_{o3})}$$


$$\text{If } g_{o1} = g_{o3}, CMRR \approx \frac{g_{m1}r_b}{2}$$

CMRR

Increasing the differential pair transconductance or r_b , the CMRR raises!.




Amplifier configurations: asymmetric

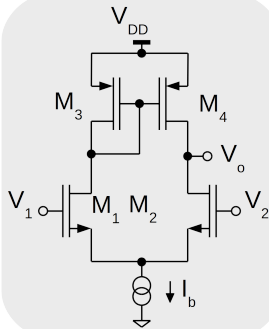


- Current mirror ensures currents are the same and half I_b
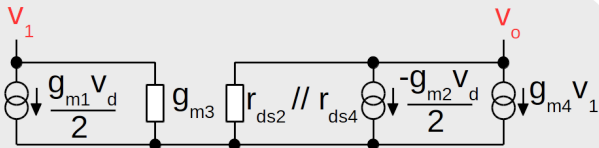
$$A_{v_d} \approx \frac{g_{m1}}{g_{o2} + g_{o4}}$$



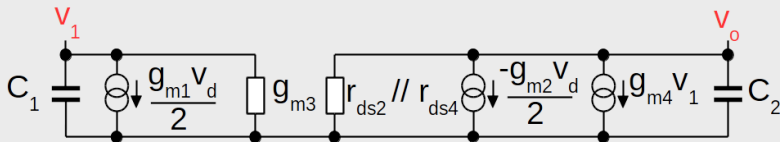Amplifier configurations: assymetric frequency response



$$C_1 = C_{GD1} + C_{BD1} + C_{GS3} + C_{GS4} + C_{BD3}$$

$$C_2 = C_{GD2} + C_{BD2} + C_{GD4} + C_{BD4} + C_L$$

$$R_1 = \frac{1}{g_{m3}}, R_2 = \frac{1}{g_{o2} + g_{o4}}$$

Then (with $g_{m1} \approx g_{m2}$):

$$A_v \approx \frac{g_{m1}}{2} \frac{R_2 \omega_2}{s + \omega_2} \left(1 + \frac{g_{m4} R_1 \omega_1}{s + \omega_1} \right) \text{ where } \omega_1 = \frac{1}{R_1 C_1}, \omega_2 = \frac{1}{R_2 C_2}$$

$$A_v = A_v(0) \frac{\left(\frac{s}{\omega_1} + 1 \right)}{\left(\frac{s}{\omega_1} + 1 \right) \left(\frac{s}{\omega_2} + 1 \right)}$$


$$A_v(0) = \frac{g_{m1} R_2}{2} (1 + g_{m4} R_1) \approx \frac{g_{m1}}{g_{o2} + g_{o4}}, \omega_1' = \omega_1 (1 + g_{m4} R_1) \approx 2\omega_1$$

A pole-zero pair is obtained, with the zero at double frequency of the pole.

The dominant pole is: $\omega_2 = \frac{g_{o2} + g_{o4}}{C_2}$



Telescopic cascode amplifier

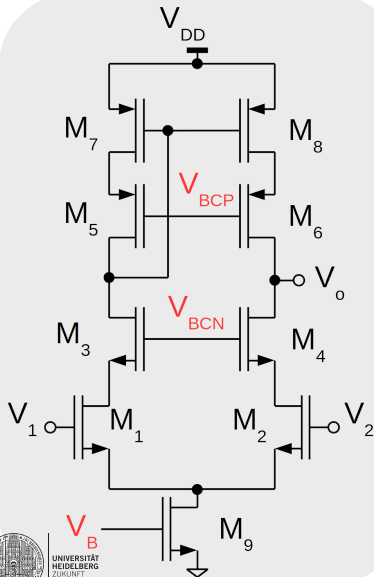


V_B, V_{BCN}, V_{BCP} are DC bias voltages generated externally to set saturation operation point.

- Gain: $A_d = \frac{(g_m r_{ds})^2}{2}$
- Cutoff frequency: $\omega_t = \frac{g_{m1}}{C_L}$ (other poles also)
- Output swing: $V_{DD} - 5V_{eff}$ ($V_{eff} = V_{GS} - V_{TH}$)

Low Gain, Low output swing but fast and low power.




Folded cascode N input

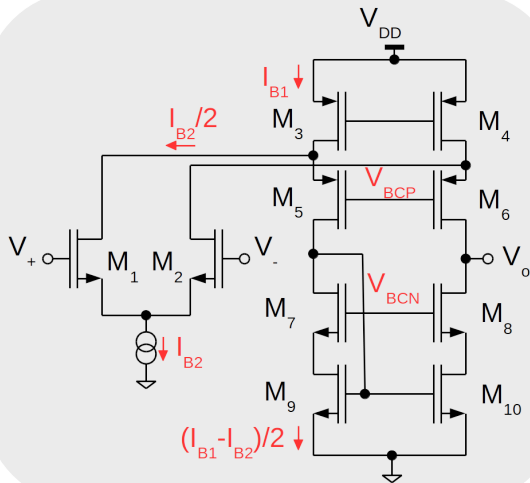

- Slower
- Wider output swing

Folded cascode N input

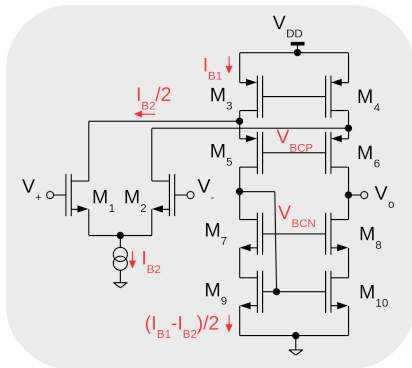- Gain: $A_d = \frac{(g_m r_{ds})^2}{2}$
- Cutoff frequency: $\omega_t = \frac{g_m}{C_L}$
(other poles also)
- Output swing $V_{DD} - 4V_{eff}$
- Wider output swing



Folded cascode P input

