



Noise

P. Fischer, Heidelberg University



Content

- Noise Description
- Noise of Components

- Noise treatment
 - Analytically
 - In Simulation
- Spectral Filtering and RMS noise
 - Noise of an RC Lowpass

- Noise in Current Mirrors
- Noise in an Amplifier

- Overall Noise of a Charge Amplifier





NOISE DESCRIPTION



What is Noise ?

- Noise is a random fluctuation of a voltage / current
- The average noise is zero: $\langle \text{noise} \rangle = 0$
 - A non-zero average is no noise, just a 'bias' or 'offset'
- The noise 'strength' can be defined as the variance:
 $\text{voltage noise}^2 = \langle v^2 \rangle$ or $\text{current noise}^2 = \langle i^2 \rangle$
where $\langle .. \rangle$ is over time
- The 'RMS Noise' is the square root of the variance
- The same RMS can be obtained by very different noise signals, as seen on an oscilloscope (time domain):

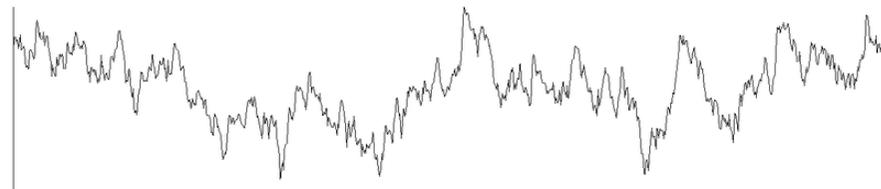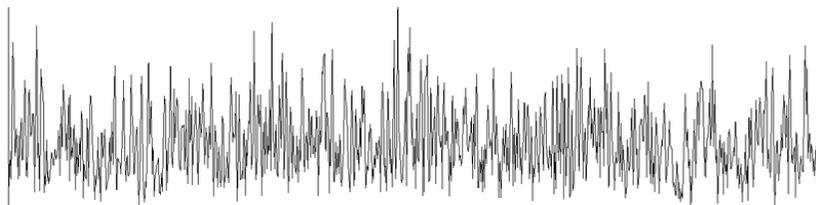

- Obviously, the left signal contains 'higher frequencies'...



Spectral Density

- The noisy signal can have different strength for various frequencies.
- We therefore describe noise by its *spectral density*, the (squared) noise voltage (density) as a function of frequency.
 - It has the unit V^2/Hz
 - Sometimes, we use the square root with the unusual unit V/\sqrt{Hz}



**30 V, 8 MHz, Low Bias Current,
Single-Supply, RRO, Precision Op Amps**

Data Sheet


ADA4622-1/ADA4622-2

NOISE PERFORMANCE				
Voltage Noise	e_N p-p	0.1 Hz to 10 Hz	0.75	μV p-p
Voltage Noise Density	e_N	f = 10 Hz	30	nV/ \sqrt{Hz}
		f = 100 Hz	15	nV/ \sqrt{Hz}
		f = 1 kHz	12.5	nV/ \sqrt{Hz}
		f = 10 kHz	12	nV/ \sqrt{Hz}
Current Noise Density	i_N	f = 1 kHz	0.8	fA/ \sqrt{Hz}



Noise Types / Spectra

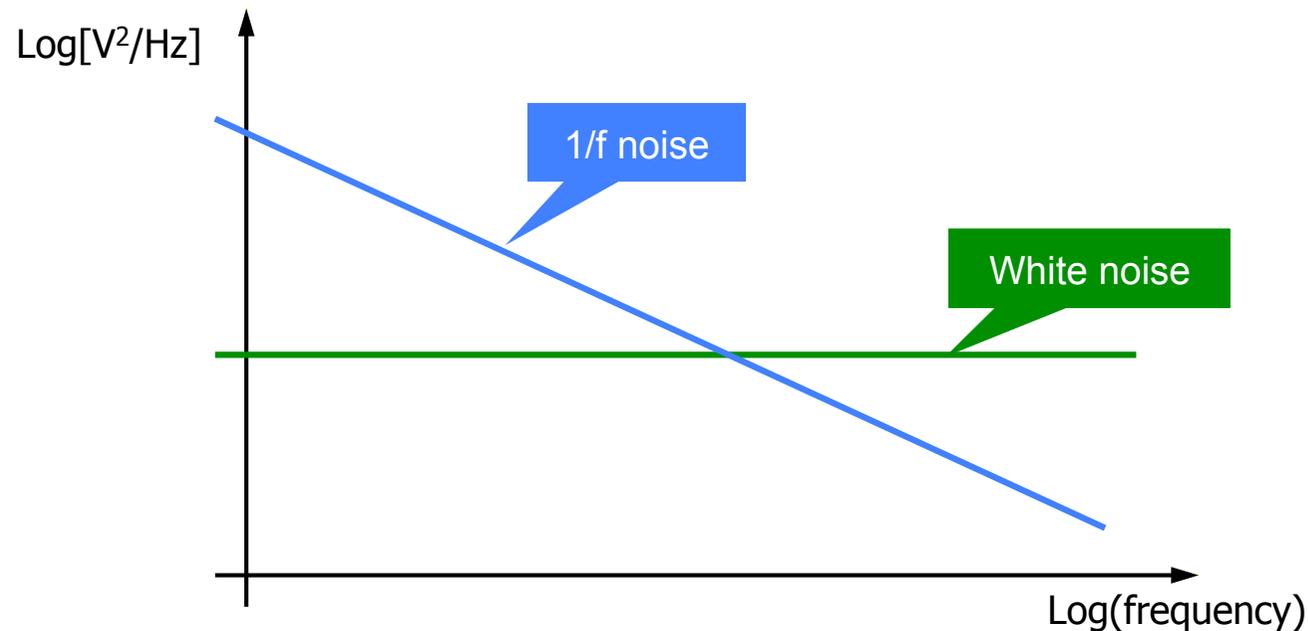- Most common types are
 - *White noise* has *constant* spectral density
 - *1/f noise* (*pink noise*) spectrum is $\sim 1/f$ (or $S(f) \propto 1/f^\alpha$)
- Be careful: one can use frequency ν , to angular freq. ω !



- The rms noise is the integral of the noise spectral density over all frequencies ($\nu = 0 \dots \infty$)



A Closer Look on Thermal Noise

- Problem: a constant spectral density up to infinite frequencies would be infinite noise power.
- Quantum mechanics gives the exact value for the spectral noise density as a function of frequency ν and temperature T :

$$S_{noise}(\nu, T) = \frac{h\nu}{e^{h\nu/kT} - 1} \xrightarrow{h\nu \ll kT} kT$$

- h = Planck's constant = 6.626×10^{-34} Js,
- k = Boltzmann's constant = 1.381×10^{-23} J/K
- For 'low' frequencies ($h\nu \ll kT$), this gives just kT
- The noise starts to drop at $\nu = kT/h \approx 21 \text{ GHz} \times T/K$
 - At room temperature, this is $\sim 5\text{THz}$. The approximation of $S_{noise} = kT$ is therefore valid for (our) practical circuit frequencies.
- (At very high frequencies, there is an additional 'quantum' noise which rises as $h\nu$)




NOISE IN COMPONENTS



Noise in Diodes

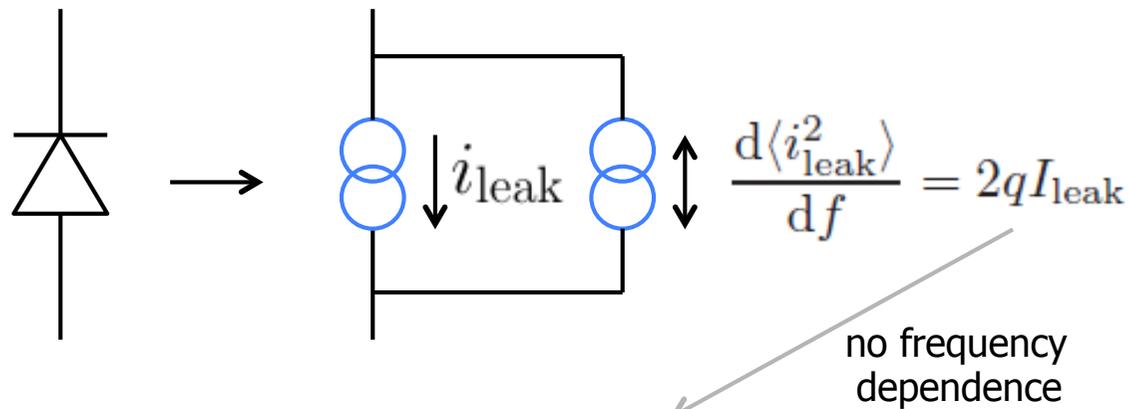- The reverse current ('leakage') of a diode is generated by charge carriers which statistically overcome a barrier.
- The statistical fluctuations lead to noise.
The fluctuations depend on the value of the leakage current.
- This is called shot noise.



- Spectrum is flat (white noise)


- Check Units: $[2 q I_{\text{Leak}}] = \text{As A} = \text{A}^2/\text{Hz}$



Noise in Resistors

- Resistors exhibit noise from thermal motion of charge carriers. This noise is *independent* on current flow!
- This *thermal noise* is *white* noise
- If can be modelled by a **serial voltage source**
OR
by the Thévenin equivalent **parallel current source**

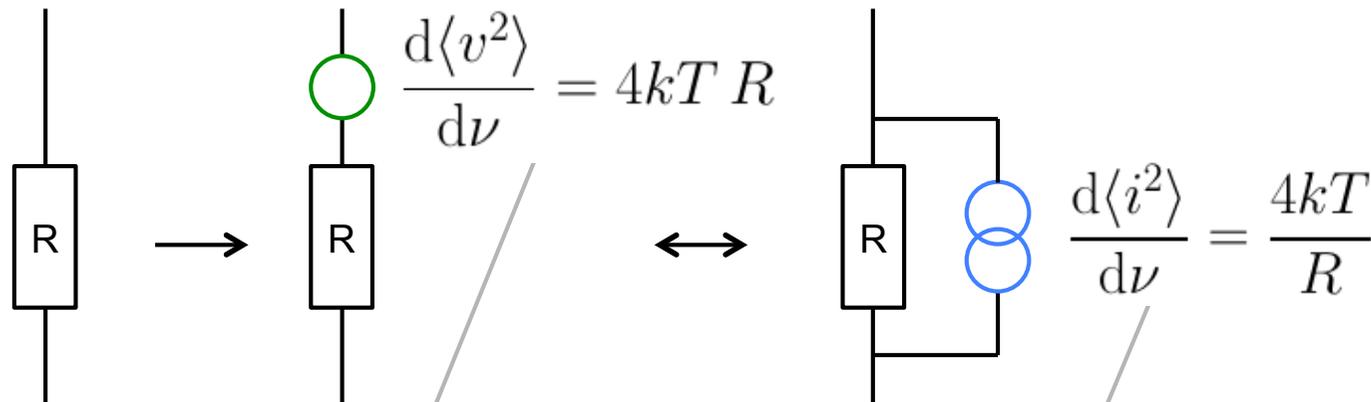Observe that (only!) these models give correct noise for serial / parallel connections of Rs




- Check Units: $[4kT R] = VA/Hz \times V/A = V^2/Hz$
 $[4kT/R] = VA/Hz / A/V = A^2/Hz$

$$4kT \approx 1.6 \times 10^{-20} VA_s = 16 \times zVA/Hz$$



White Noise in Transistors

- The MOS channel can be seen as a series of (position dependent) resistor (at least in linear operation). Their noise contributions can be integrated up.
- The white **current noise** in the channel is $\frac{d\langle i^2 \rangle}{d\nu} = 4kT \gamma g_m$
 - the factor γ from integration varies depending on operation regime: $\gamma = 2/3$ in strong inversion, less in w.i.
- This current noise at the drain can also be written as a **voltage noise** at the gate (by dividing by g_m^2)

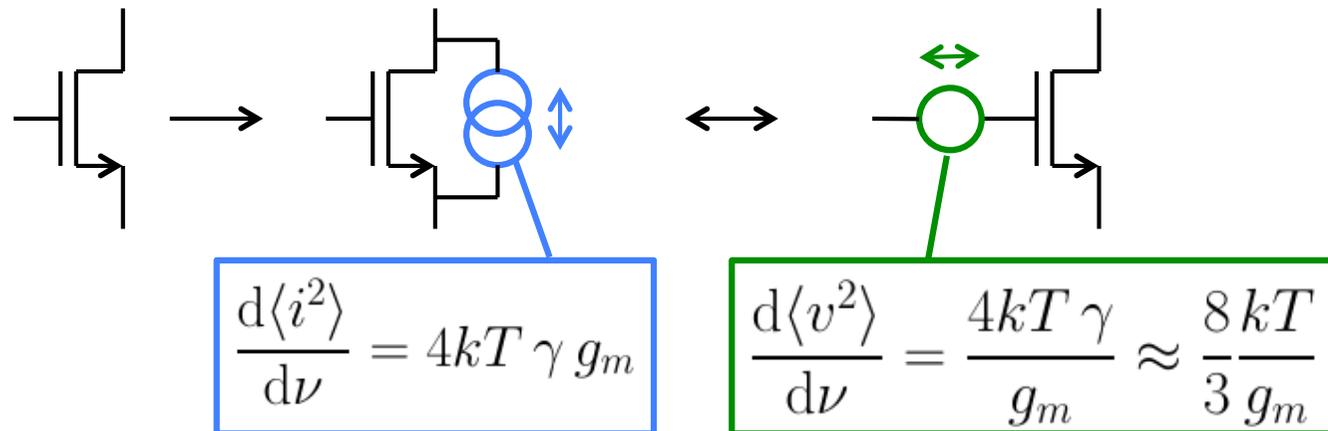

- Note: noise for very short devices can be increased



1/f Noise in Transistors

- Charge carriers in the channel can be captured ('trapped') at impurities and released later.
 - This happens mostly at the oxide interface
- This leads to an additional noise with *1/f spectrum*
- The importance of this contribution depends on
 - Fabrication process → Technology noise parameter K_f
 - MOS type (JFETs are *very much* (>10 x) better (no Interface))
 - MOS polarity (PMOS are *significantly* (10 x) better than NMOS)
- The effect averages out for larger devices (→WL in formula)

Independent of temperature
(as long as traps do not
freeze out)

$$\frac{d\langle v_{1/f}^2 \rangle}{df} = \frac{K_f}{C_{ox}WL} \frac{1}{f}$$

1/f noise

$$\frac{d\langle v^2 \rangle}{d\nu} = \frac{8kT}{3g_m}$$

Thermal noise (white)



NOISE CALCULATIONS



Recipes

- Noise contributions are independent → Each source is treated separately and noise contributions are added up (in quadrature) at the end
- For each source
 - calculate the transfer function $H(s)$ to the 'output'
 - multiply the noise spectrum of the source with $|H|^2(s)$ (because we treat squared voltages)
 - integrate the 'output' spectrum over all frequencies.
- Add the resulting variances
- Square root of the sum leads to the final noise (at the output)

- The noise rms (in V or A) value must be compared to the signal (which also depends on $H(s)$) to get a Signal-to-Noise ratio (SNR)




NOISE SIMULATION



Noise Simulation

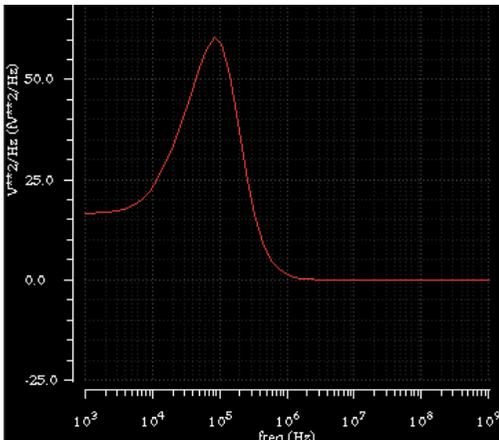- Simulation type 'noise' creates AC noise for all components
- Give a (generous) frequency range
- Noise is 'collected' for ONE node
This can be
 - a voltage (give terminals)
 - a current (give a voltage source)
- You need to select any node for plotting.
You will see the V^2/Hz spectrum



Output Noise

probe Output Probe Instance

Choosing Analyses -- Virtuoso® Analog Design Environ

Analysis tran dc ac noise sim

xf sens dcmatch pss

pz sp envlp pxf

pac pstb pnoise qpnoise

psp qpss qpac hb

qpxf qpdp hb hbac

hbnoise hbasp

Noise Analysis

Sweep Variable

Frequency Design Variable Temperature Component Parameter Model Parameter

Sweep Range

Start-Stop Center-Span

Start Stop

Sweep Type

Automatic

Add Specific Points

Output Noise

voltage Positive Output Node

Negative Output Node

Input Noise

none





Total Noise

- To integrate a noise spectrum over frequency use the **totalNoise("noise" nil nil nil)** command in ADE
 - Arguments are **start_freq stop_freq exlusions**. They can be set to **nil** for full range / all components
 - No need to specify a net / node (the one given on the simulation window is taken)
- This will give the *squared* noise voltage (in V^2 or A^2)
- To get RMS noise (in V or A), calculate the square root!



Noise Summary

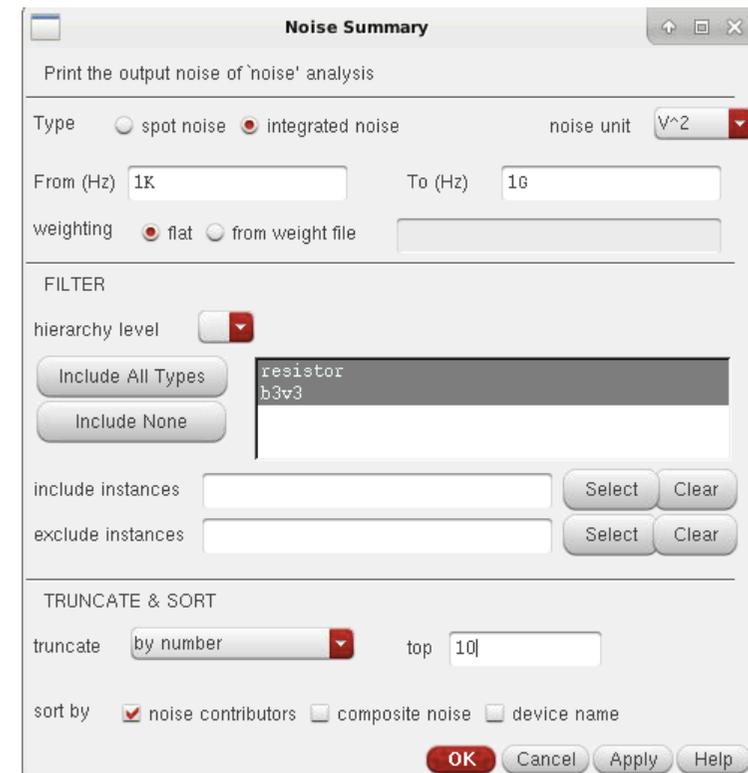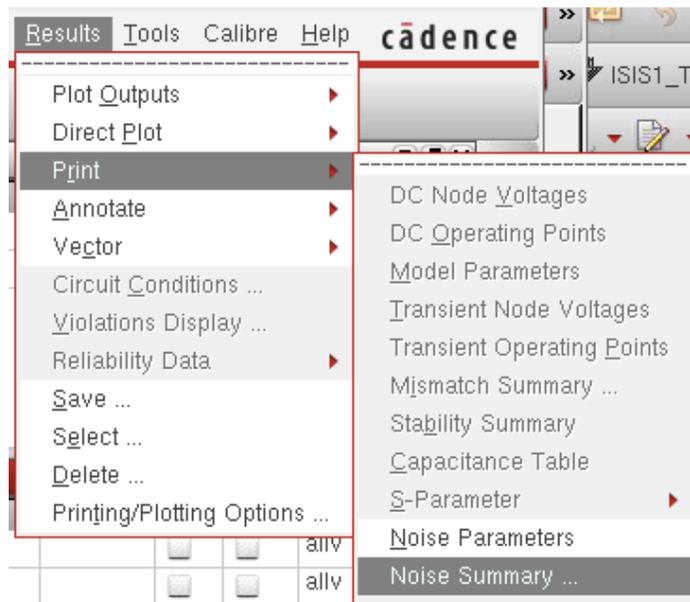- In more complex circuits, you can see which components contribute to the output noise:
 - Results → Print → Noise Summary
 - Usually select 'integrated noise'





Noise Summary Result

- Lists most important contributions
- Also gives the type of noise:
 - Resistor noise ('rn')
 - Channel noise ('id')
 - 1/f noise ('fn')
 - Source resistive noise ('rs') (depends on actual layout!)
 - Drain resistive noise ('rd') (depends on actual layout!)
 - Gate resistive noise (?) (depends on actual layout!)

Device	Param	Noise Contribution	% Of Total
/M1	fn	1.0337e-08	58.40
/R1	rn	4.17986e-09	23.62
/R0	rn	2.098e-09	11.85
/C2	rn	9.66773e-10	5.46
/M1	id	7.17454e-11	0.41
/MN	id	3.52872e-11	0.20
/MN	fn	1.07926e-11	0.06
/M1	rs	4.07753e-14	0.00
/MN	rs	3.16337e-15	0.00
/M1	rd	2.69697e-17	0.00




NOISE BANDWIDTH LIMITATION



Bandwidth Limitation

■ Brick-Wall Low Pass:

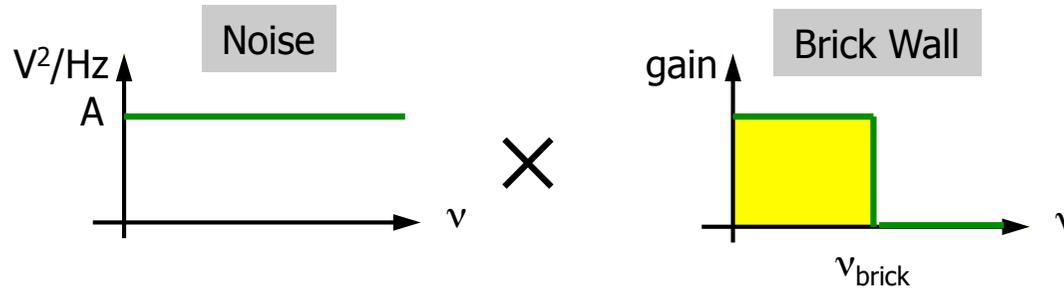
- Assume a Low Pass which passes all frequencies up to ν_{brick} and then stops perfectly



- When we filter white noise, the overall noise is just $\text{rms}^2 = A \nu_{\text{brick}}$

■ RC Low Pass:

- How is the integral now ?

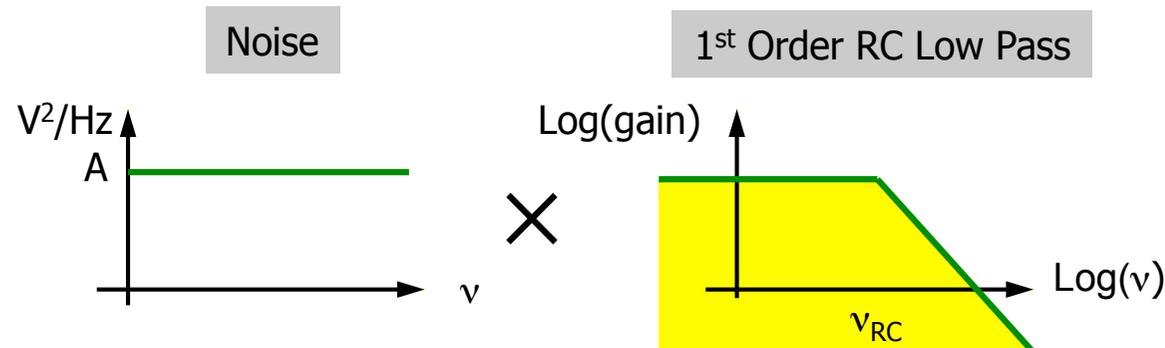



The Integral

- Transfer Function of RC Low Pass: $H(\omega) = \frac{1}{1 + i\omega\tau}$ ($\tau = RC$)

- Gain: $v^2(\omega) = |H(\omega)|^2 = H(\omega)H^*(\omega)$

$$= \frac{1}{(1 + i\omega\tau)(1 - i\omega\tau)} = \frac{1}{1 + (\omega\tau)^2}$$

- Integral: $rms^2 = \int_0^{\infty} \frac{A}{1 + (2\pi\nu\tau)^2} d\nu$

$$= \frac{A}{2\pi\tau} \int_0^{\infty} \frac{dx}{1 + x^2} = \frac{A}{2\pi\tau} \frac{\pi}{2} = \frac{A}{4\tau} = \frac{A\omega}{4} = \frac{A\pi\nu}{2}$$

(an integral of $H(\omega) \sim 1/\omega$ would not converge, but $H^2(\omega)$ does)

- To obtain the same noise with a 'brick wall' filter, we need

- $A v_{\text{brick}} = A \pi v_{\text{RC}} / 2 \rightarrow v_{\text{brick}} = v_{\text{RC}} \times \pi / 2$



Noise of RC Low Pass

- In the previous calculation, we have assumed R in the Low-Pass as noiseless. In reality, it is noisy
- If we have no *signal* at the input, the remaining input noise is just the *voltage noise* of the resistor, i.e. $A = 4kT R$
- The resulting output noise is

$$rms^2 = \frac{1}{4} A \omega = \frac{1}{4} 4kT R \frac{1}{RC} = \boxed{\frac{kT}{C}}$$

- This 'kT/C-Noise' does *not* depend on R, but on C
 - This is because the change in bandwidth (with R) just compensates the change in noise
 - This kTC noise is present whenever signals are sampled to Cs!



Small capacitors 'have' large noise



CURRENT SOURCES



MOS as Current Source

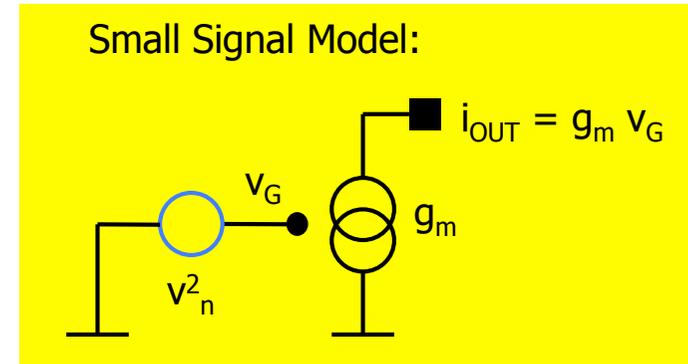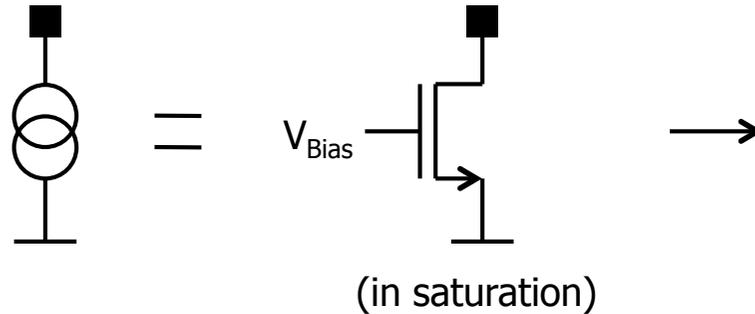

- Due to input voltage noise source, we get at the output

$$i_{OUT}^2 = g_m^2 v_G^2 = g_m^2 v_n^2 = g_m^2 \frac{4kT \gamma}{g_m} = 4kT \gamma g_m$$

as before.

For a *low noise current source* we need *small* g_m



MOS vs. Resistor

- For a current I_0 , what gives lower noise: MOS or resistor ?
 - Assume we operate the MOS in s.i. just at edge of saturation:



▪ **R:** $\langle i^2 \rangle_R = \frac{4kT}{R} = 4kT \frac{I_D}{V_{DSat}}$

▪ **MOS:** $I_D = \frac{\beta}{2}(V_{GS} - V_{th})^2(1 - \lambda V_{DS})$

$$V_{DSat} = V_{GS} - V_{th} = \sqrt{\frac{2I_D}{\beta}}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \sqrt{2I_D\beta} = \frac{2I_D}{V_{DSat}}$$

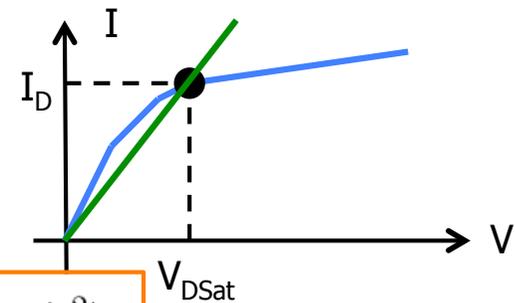
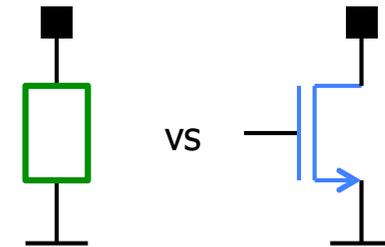
$$\langle i^2 \rangle_{MOS} = 4kT \eta g_m = 4kT \eta \frac{2I_D}{V_{DSat}} = 2\eta \times \langle i^2 \rangle_R$$



- MOS is slightly worse, but has *much* lower output resistance
 - Also, current cannot be varied with fixed R
 - At higher voltage, R is larger and its noise decreases.
 - R has *no* $1/f$ noise!
 - Consider this 'old style' approach for very low noise...



Noise in the Simple Current Mirror

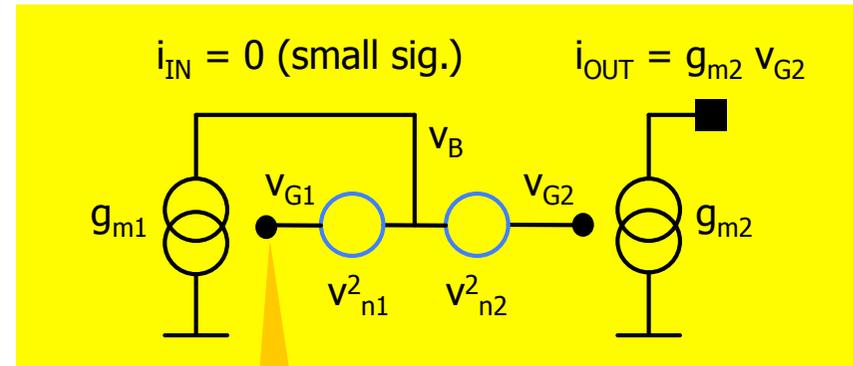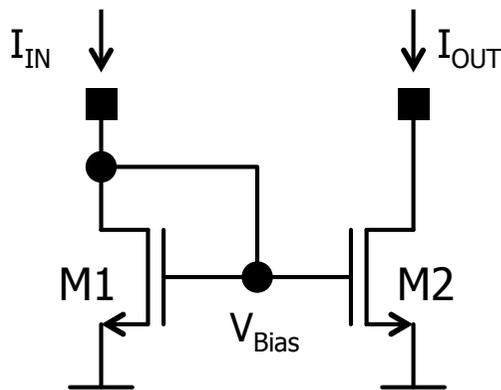



$V_{G1} = 0$ because small signal input current is 0

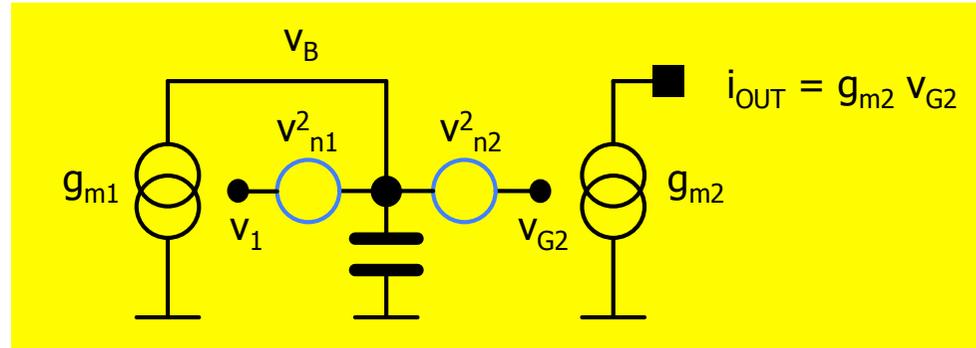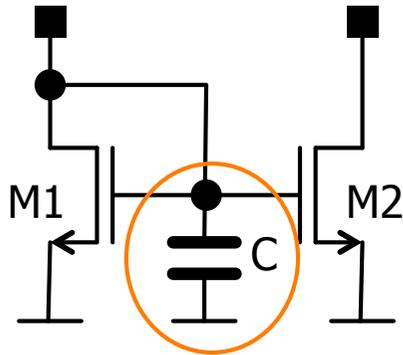1. Left noise source: $v_{G2}^2 = v_B^2 = v_{n1}^2 \rightarrow i_{OUT}^2 = g_{m2}^2 \frac{4kT \gamma}{g_{m1}}$
 2. Right noise source: $v_{G2}^2 = v_{n2}^2 \rightarrow i_{OUT}^2 = g_{m2}^2 \frac{4kT \gamma}{g_{m2}}$
- Sum:** $i_{OUT}^2 = g_{m2} 4kT \gamma \left(1 + \frac{g_{m2}}{g_{m1}} \right)$

- For $g_{m1} = g_{m2}$ (1:1 Mirror), noise $\sqrt{i_{OUT}^2}$ increases by $\sqrt{2}$
- For $g_{m1} \gg g_{m2}$ (N:1 Mirror), noise is small
- For $g_{m1} \ll g_{m2}$ (1:N Mirror), noise is large. **DO NOT USE**



Improving the Current Mirror with Decoupling



- The first component is multiplied by

$$\frac{1}{1 + \frac{C^2 \omega^2}{g_{m1}^2}} \text{ so that we get overall}$$

$$g_{m2} 4kT \gamma \left(1 + \frac{g_{m2}}{g_{m1}} \frac{1}{1 + \frac{C^2 \omega^2}{g_{m1}^2}} \right)$$

Noise of the input MOS is cut away above $\omega = g_{m1}/C$

```
In[41]:= EQ1 = gm1 v1 + vb s C == 0;
```

```
EQ2 = v1 - vb == vn;
```

```
In[43]:= Eliminate[{EQ1, EQ2}, v1]
```

```
Out[43]= gm1 vn == (-gm1 - C s) vb
```

```
In[44]:= Solve[%, vb] // First
```

```
Out[44]= {vb -> - gm1 vn / (gm1 + C s)}
```

```
In[45]:= VB[s_] = vb /. %
```

```
Out[45]= - gm1 vn / (gm1 + C s)
```


```
In[46]:= VB[i \omega] Conjugate[VB[i \omega]]
```

```
Out[46]= gm1^2 vn^2 / (gm1^2 + C^2 \omega^2)
```



(One Possible further Improvement)

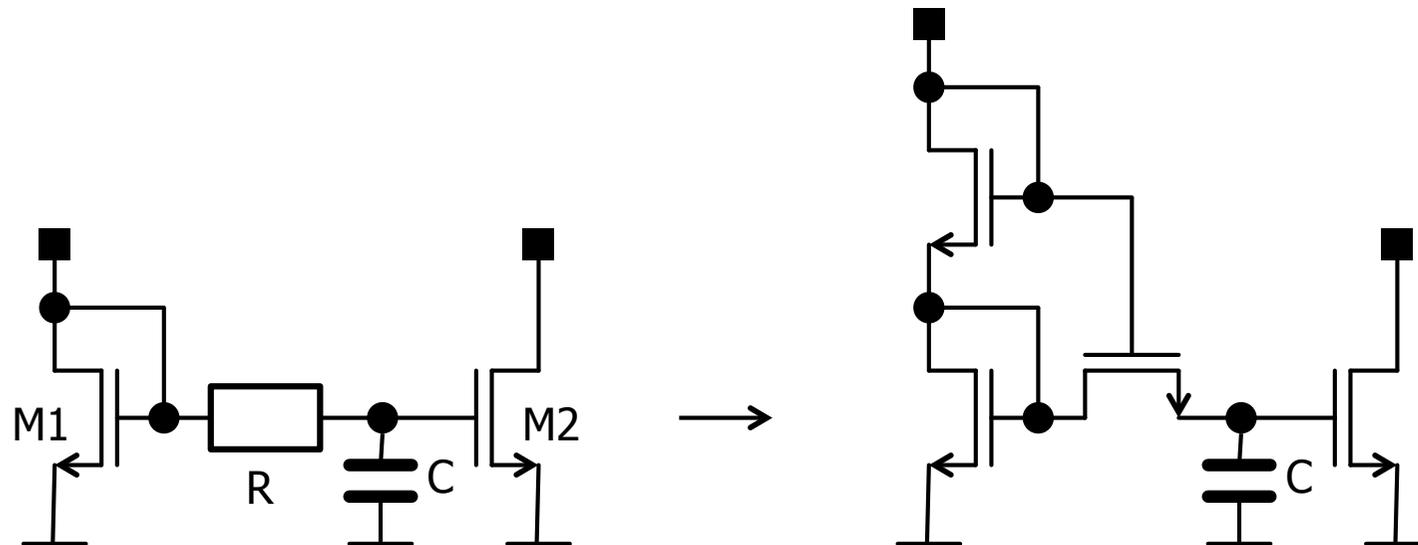- An additional resistor R can be used to lower the bandwidth of the filter from g_{m1}/C to $1/RC$
- Note that R also adds its own noise...
- R can be implemented as a MOS with proper bias...







AMPLIFIER



Gain Stage

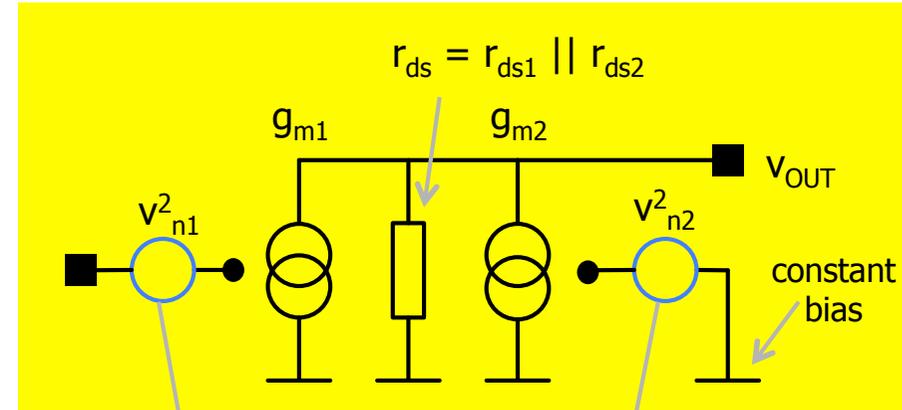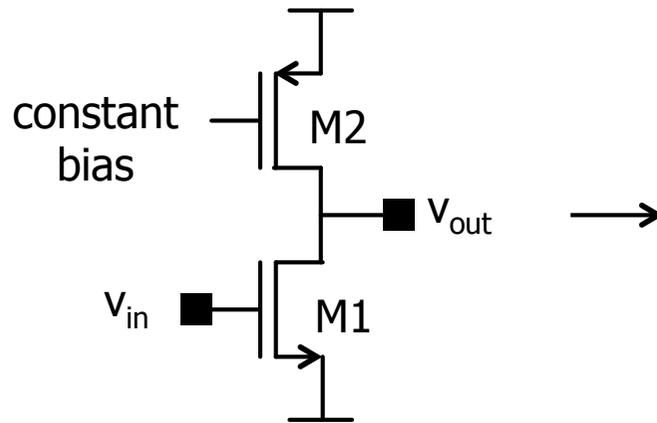

■ Output noise:

$$v_{out2} = v_{out2in} + v_{out2load} / .$$

$$\left\{ v_{n1}^2 \rightarrow \frac{4 k T \gamma}{g_{m1}}, v_{n2}^2 \rightarrow \frac{4 k T \gamma}{g_{m2}} \right\}$$

$$4 (g_{m1} + g_{m2}) k r_{ds}^2 T \gamma$$

■ Referred to input (divide by gain):

$$gain = g_{m1} r_{ds}; v_{in2} = \frac{v_{out2}}{gain^2}$$

$$\frac{4kT \gamma}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right)$$

$$EQ1 = g_{m1} v_{n1} + \frac{v_{out}}{r_{ds}} = 0 \quad EQ2 = \frac{v_{out}}{r_{ds}} + g_{m2} v_{n2} = 0$$

$$\text{Solve}[EQ1, v_{out}] // \text{First} \quad \text{Solve}[EQ2, v_{out}] // \text{First}$$

$$\{v_{out} \rightarrow -g_{m1} r_{ds} v_{n1}\} \quad \{v_{out} \rightarrow -g_{m2} r_{ds} v_{n2}\}$$

$$v_{out2in} = v_{out}^2 / . \% \quad v_{out2load} = v_{out}^2 / . \%$$

$$g_{m1}^2 r_{ds}^2 v_{n1}^2 \quad g_{m2}^2 r_{ds}^2 v_{n2}^2$$

Input MOS must have *high* g_{m1}
Bias Source must have *low* g_{m2}




CHARGE AMPLIFIER



The Charge Amplifier

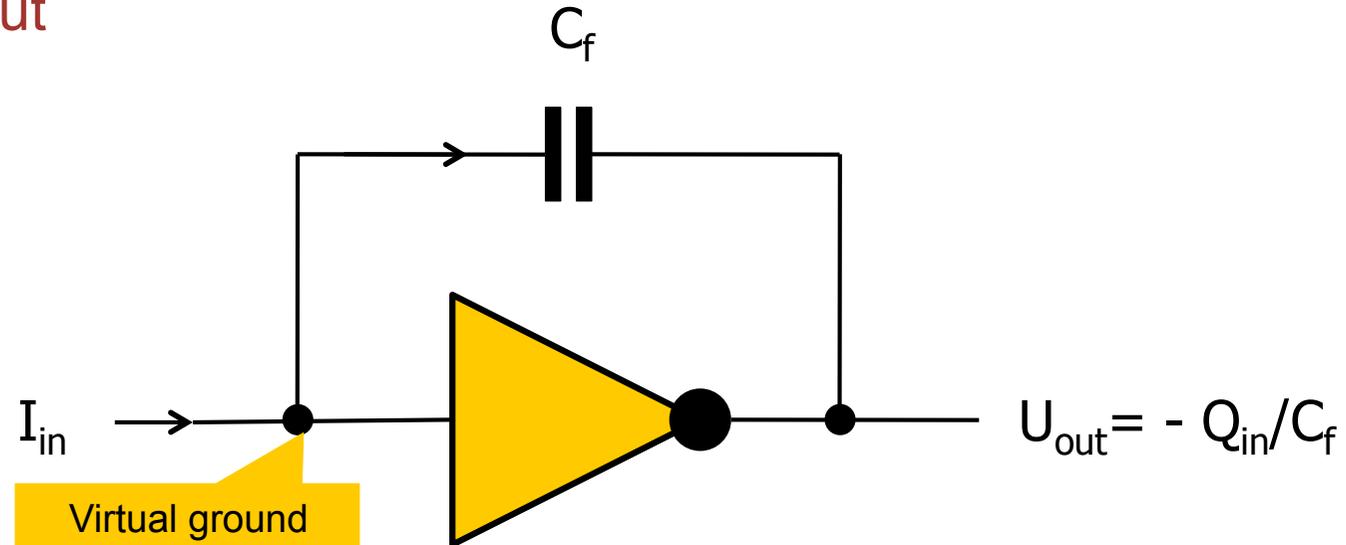- The amplifier with feedback generates a *virtual ground* at its input




- Current (flowing charge) cannot stay on the input node (because the voltage is fixed) and must flow onto C_f
- The total input charge is the integral over I_{in}
- Therefore $Q_{in} = \int I_{in} dt = Q_f = U_f C_f \rightarrow U_{out} = -U_f = -Q_{in}/C_f$



Classical System have a Filter = Shaper

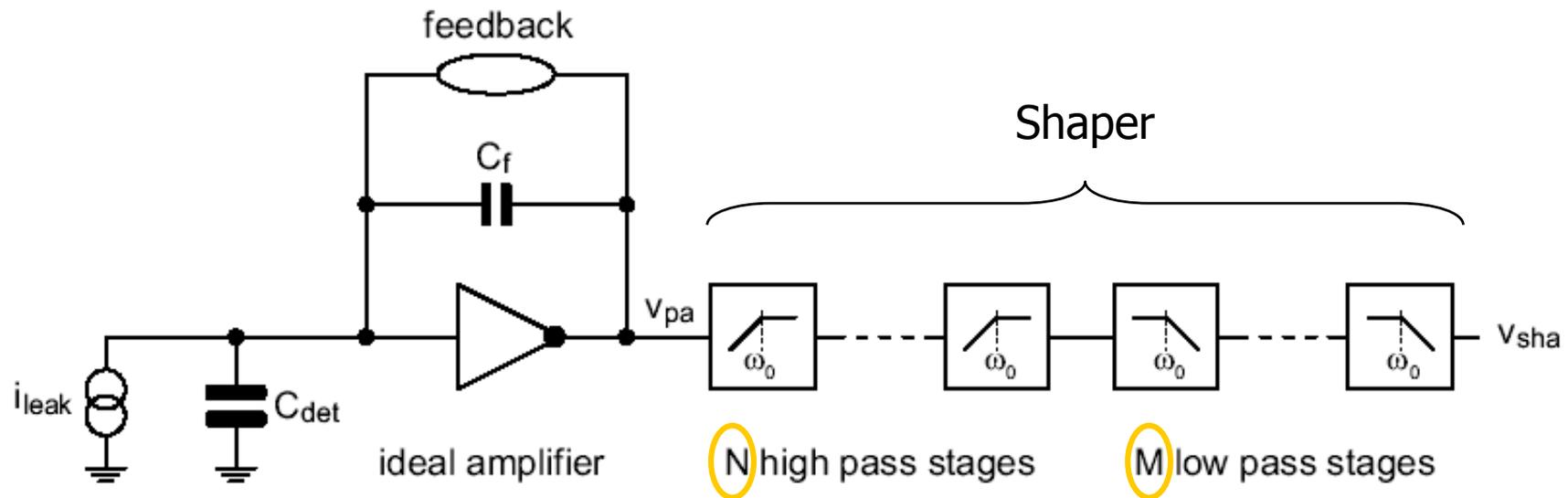- Filter are added for pulse shaping & noise reduction:
 - High pass stages* eliminate DC components & low freq. noise
 - Low pass stages* limit bandwidth & therefore high freq. noise




- Due to its output shape (see later), this topology is often called a ‘Semi Gaussian Shaper’
- Nearly always $N = 1$. Often $M = 1$, sometimes M up to 8




Frequency Behaviour of Shaper

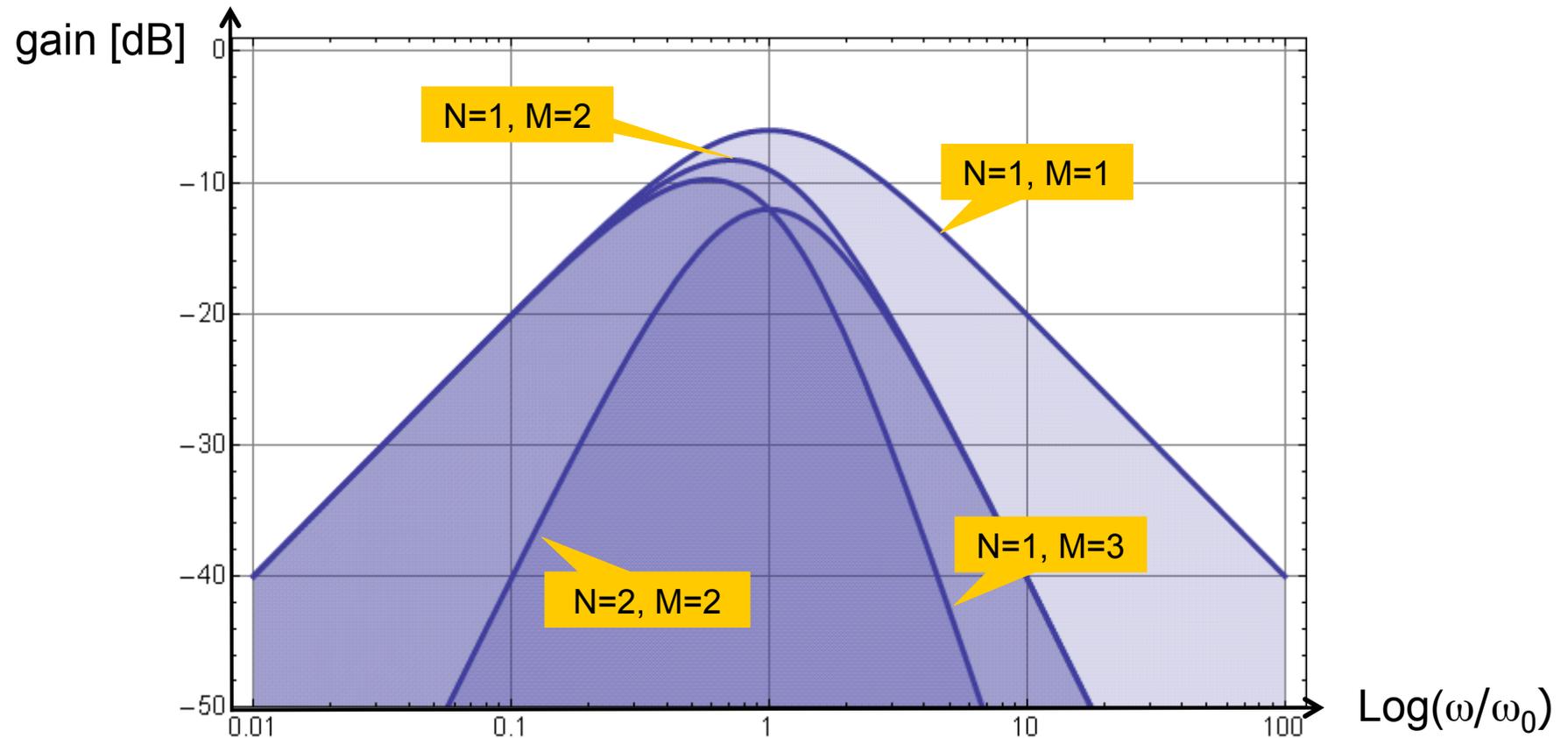- Low and High frequencies are attenuated
- Corner frequency (here: 1) is transmitted best
- Bode Plot (log/log) of transfer characteristic:





What is the output signal?

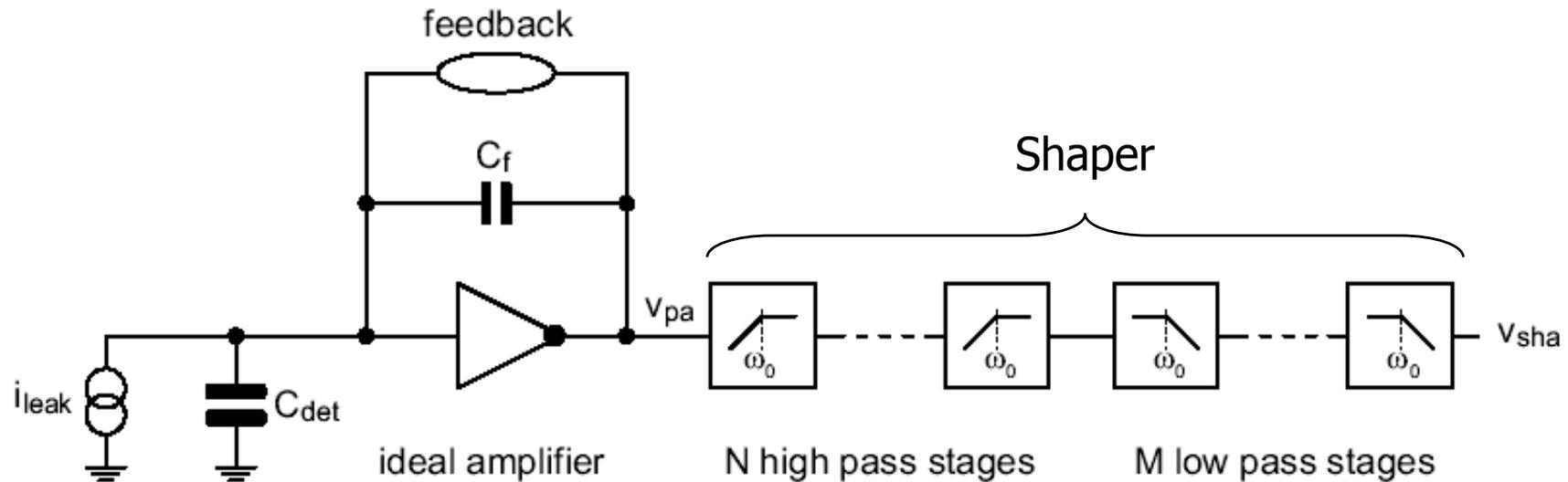

- For a delta current pulse, the output voltage v_{pa} is a step function
- This has a Laplace-Transform $\sim 1/s$
- The transfer functions of the high / low pass stages multiply to:

$$\mathcal{L}^{(N,M)}(s) = \frac{1}{s} \left(\frac{s\tau}{1 + s\tau} \right)^N \left(\frac{1}{1 + s\tau} \right)^M = \frac{\tau^N s^{N-1}}{(1 + s\tau)^{N+M}}$$



Pulse shape after shaper

- The time domain response is the inverse Laplace transform.
- The Laplace integral can be solved with residues:
There is an $(N+M)$ -fold pole at $-1/\tau$

$$\begin{aligned}
 f^{(N,M)}(t) &= \text{Res} \left. \frac{\tau^N s^{N-1} e^{st}}{(1+s\tau)^{N+M}} \right|_{s=-1/\tau} \\
 &= \frac{\tau^N}{(N+M-1)!} \lim_{s \rightarrow -\frac{1}{\tau}} \frac{d^{N+M-1}}{ds^{N+M-1}} \left[\frac{s^{N-1} e^{st}}{(1+s\tau)^{N+M}} \left(s + \frac{1}{\tau} \right)^{N+M} \right] \\
 &= \frac{1}{(N+M-1)!} \left(\frac{t}{\tau} \right)^M \sum_{i=0}^{\infty} \frac{\left(-\frac{t}{\tau}\right)^i}{i!} \frac{(M+i+N-1)!}{(M+i)!} \quad (1.42)
 \end{aligned}$$

- For only ONE high pass section ($N=1$), this simplifies to:



$$f^{(1,M)}(t) = \frac{1}{M!} \left(\frac{t}{\tau} \right)^M e^{-t/\tau} \quad t_{\text{peak}}^{(1,M)} = M\tau = \frac{M}{\omega_0} \quad f_{\text{max}}^{(1,M)} = \frac{1}{M!} \left(\frac{M}{e} \right)^M$$

$$f_{\text{max}}^{(1,1)} = 1/e$$



Pulse Shapes for N=1 (Only ONE High – Pass)

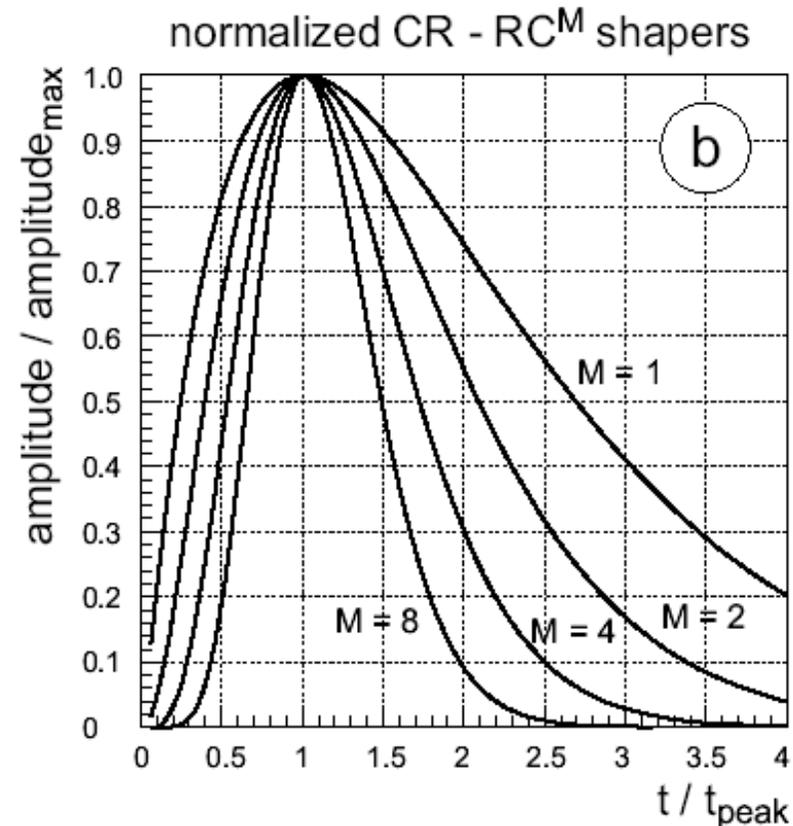
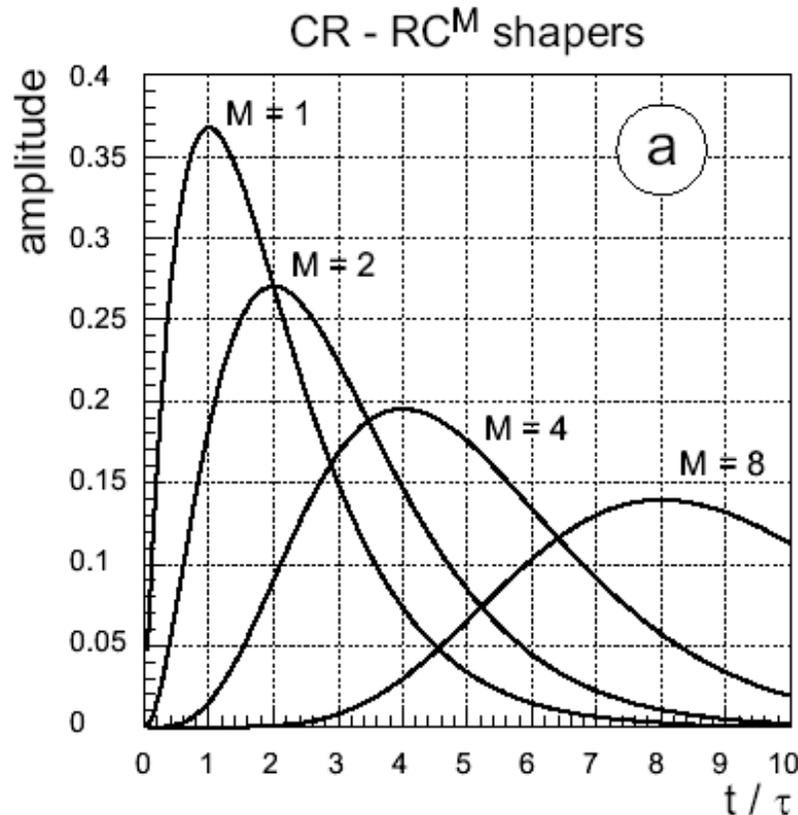
- Pulses from higher order are slower. To keep peaking time, τ of each stage must be decreased
- Right plots shows normalized pulses (same peak amp. & time)
- For high orders, pulses become narrow (width / peaking time), this is good for high pulse rates!





(Pulse Shapes for N=2)

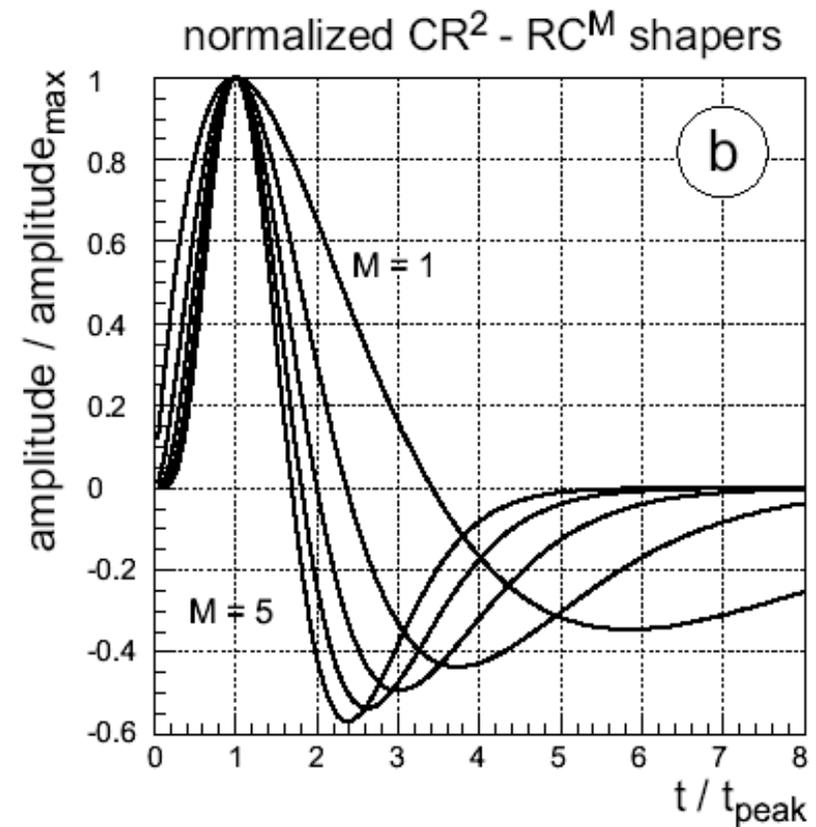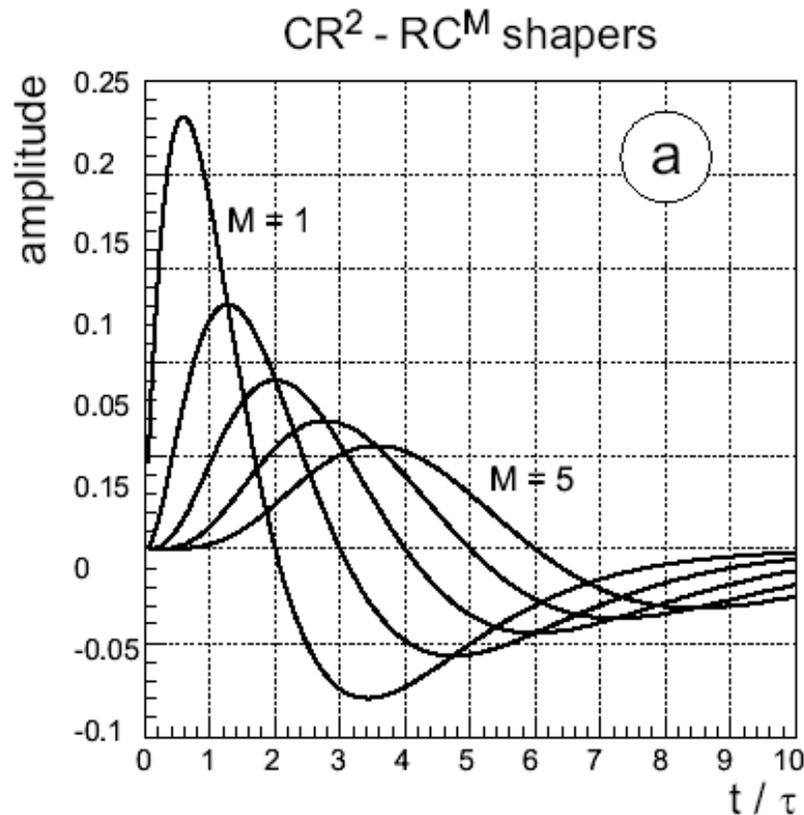
- This gives an undershoot which is often undesirable → N=1.
 - But: The zero crossing time is *independent* of amplitude.
It can be used to measure the pulse arrival time with no time walk





Noise calculation: Noise sources

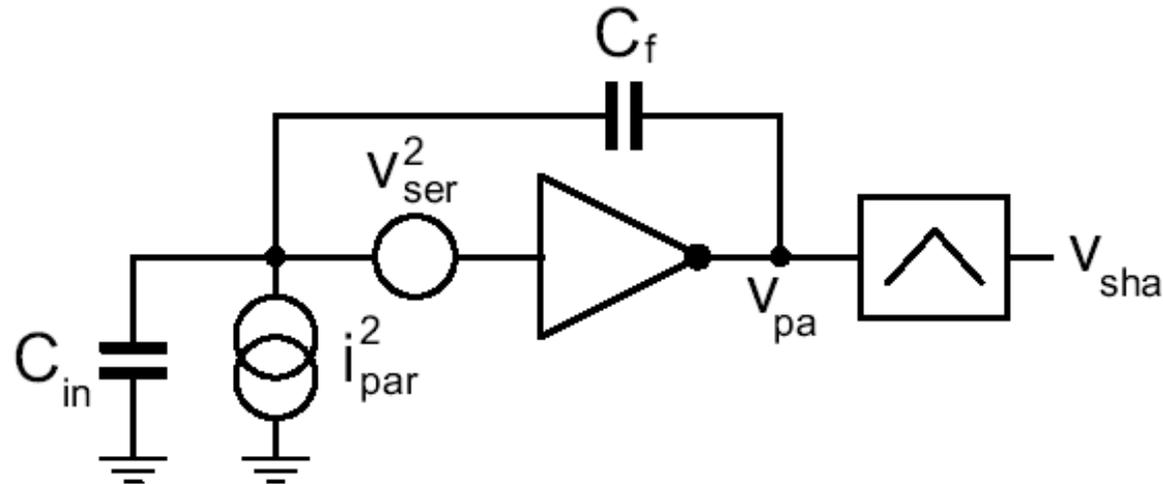- Equivalent circuit with (ideal) amplifier, input capacitance, feedback capacitance and (dominant) noise sources:



- Spectral densities of noise sources:

serial noise voltage : $\frac{d\langle v^2(f) \rangle}{df} = V_0 + V_{-1}f^{-1}$

parallel noise current : $\frac{d\langle i^2(f) \rangle}{df} = I_0$

white (channel)

1/f noise (MOS)

white (leakage)



What is the total noise at the output ?


- Recipe (again):
 1. Calculate what effect a voltage / current noise *of a frequency f* at the input has at the output
 2. For each noise source: Integrate over all frequencies (with the respective densities)
 3. Sum contributions of all noise sources

- This yields the total rms voltage noise at the output

- Then compare this to a ‘typical’ signal.
It is custom to use *one* electron at the input as reference.



Parallel Noise Current

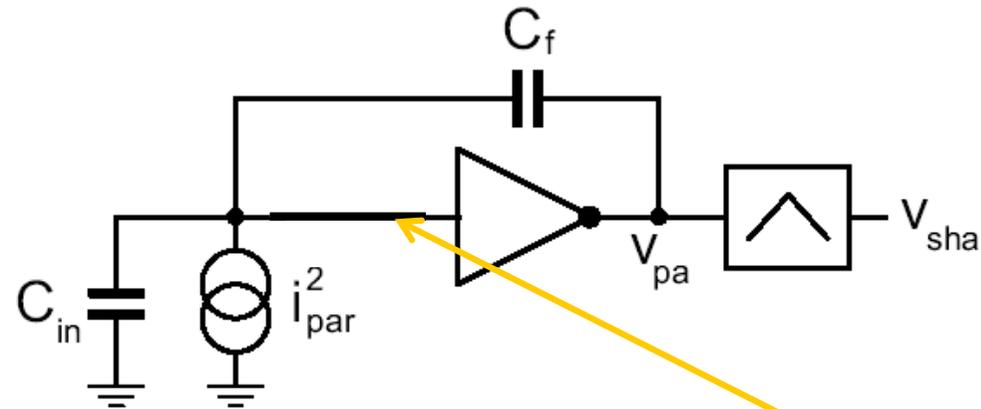


- We assume a perfect virtual ground at the amplifier input
 - No charge can go to C_{in} (voltages are fixed)
 - Noise current must flow through C_f : $v_{out} = i_{in} \times Z_{Cf}$

$$\text{parallel noise : } \frac{d\langle v_{pa}^2(\omega) \rangle}{d\omega} = \frac{d\langle i_{par}^2(\omega) \rangle}{d\omega} \frac{1}{(\omega C_f)^2} = \frac{I_0}{2\pi} \frac{1}{(\omega C_f)^2}$$

(note the change of the frequency variable from ν to ω)



Serial Noise Voltage

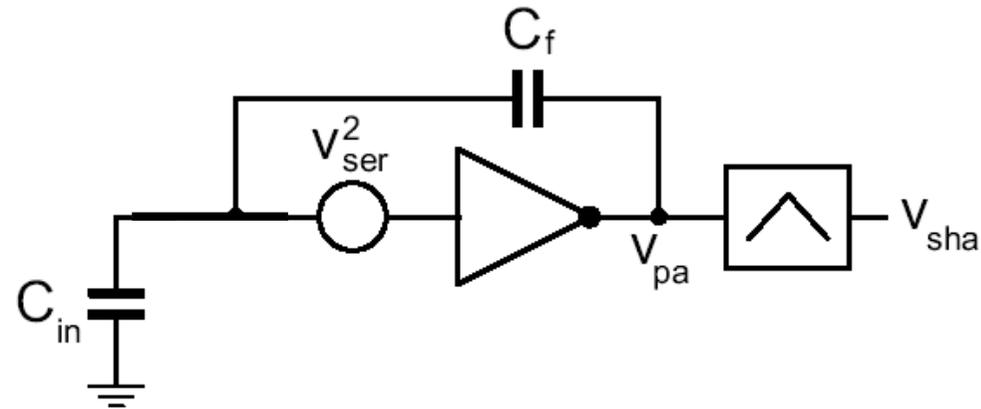

- Output noise is determined by the capacitive divider made from C_f and C_{in} : $v_{ser} = v_{pa} \times Z_{Cin} / (Z_{Cin} + Z_{Cf})$

or:

$$v_{pa}^2 = v_{ser}^2 \left(\frac{C_{in} + C_f}{C_f} \right)^2$$

Therefore: serial noise : $\frac{d\langle v_{pa}^2(\omega) \rangle}{d\omega} \approx \left(V_{-1}\omega^{-1} + \frac{V_0}{2\pi} \right) \left(\frac{C_{in}}{C_f} \right)^2$

$$(C_{in} = C_{det} + C_{preamp} + C_{parasitic})$$



Total *Output* Noise (after the amplifier)

- In total, the output noise can be written as a sum of contributions with different frequency dependence:

$$\frac{d\langle v_{pa}^2(\omega) \rangle}{d\omega} = \sum_{k=-2}^0 c_k \omega^k$$

frequency dependence is here

with

$$c_{-2} = \frac{I_0}{2\pi C_f^2}, \quad c_{-1} = V_{-1} \frac{C_{in}^2}{C_f^2} \quad \text{and} \quad c_0 = V_0 \frac{C_{in}^2}{2\pi C_f^2}.$$

leakage
(white)

MOS gate
(1/f)

MOS channel
(white)

from leakage current I_{leak} :

$$I_0 = 2qI_{leak}$$

from transistor channel noise:

$$V_0 = \frac{8}{3} \frac{kT}{g_m}$$

from 1/f noise:

$$V_{-1} = \frac{K_f}{C_{ox}WL}$$



Noise Transfer Function

- (N,M) - Shaper transfer function: $H_{N,M}^2(\omega) = A^2 \frac{\left(\frac{\omega}{\omega_0}\right)^{2N}}{\left(1 + \left(\frac{\omega}{\omega_0}\right)^2\right)^{N+M}}$.

- 'Filtered' noise at the output of the shaper:

$$\begin{aligned} \langle v_{\text{sha}}^2 \rangle &= \int_0^\infty H_{N,M}^2(\omega) d\langle v_{\text{pa}}^2(\omega) \rangle = \sum_{k=-2}^0 \int_0^\infty c_k \omega^k H_{N,M}^2(\omega) d\omega \\ &= \frac{A^2}{2} \frac{1}{\Gamma(N+M)} \sum_{k=-2}^0 c_k \omega_0^{k+1} \Gamma\left(N + \frac{k+1}{2}\right) \Gamma\left(M - \frac{k+1}{2}\right) \end{aligned}$$

$$\Gamma(z+1) = z \Gamma(z)$$

$$\Gamma\left(\frac{1}{2}\right) = \sqrt{\pi},$$

- For simplest shaper (N=M=1),
Squared rms noise voltage at the shaper output:

$$\langle v_{\text{sha}}^2 \rangle = A^2 \frac{\pi}{4} \left(\frac{c_{-2}}{\omega_0} + \frac{2}{\pi} c_{-1} + \omega_0 c_0 \right)$$



Calculation of ENC

- The **equivalent noise charge, ENC** is the (rms) noise at the output of the shaper expressed in Electrons input charge, i.e. divided by the ‘charge gain’
- The ‘charge gain’ is (see before): $V_{max} = q/C_f \times A \times 1/e$

charge of 1 electron
(1.6e-19C)

Shaper
dc gain

Peak amplitude
for N=M=1

leakage gives noise
for slow shaping

1/f – noise cannot be
reduced by charging
shaping time

$$ENC_{CR-RC}^2 = \frac{\langle v_{sha}^2 \rangle}{V_{max}^2} = \frac{e^2}{4q^2} \left(\frac{\tau}{2} I_0 + \frac{1}{2\tau} V_0 C_{in}^2 + 2 V_{-1} C_{in}^2 \right)$$

C_{in} is bad for **fast** shaping.
Reducing V_0 requires large g_m



Noise contributions

- Real noise contributions for the coefficients I_0 , V_0 , V_{-1} :

from leakage current I_{leak} : $I_0 = 2qI_{\text{leak}}$

from transistor channel noise: $V_0 = \frac{8 kT}{3 g_m}$

from 1/f noise: $V_{-1} = \frac{K_f}{C_{\text{ox}}WL}$

- For a $0.25\mu\text{m}$ technology ($C_{\text{ox}}=6.4 \text{ fF}/\mu\text{m}^2$, $K_f=33 \times 10^{-25} \text{ J}$, $L=0.5\mu\text{m}$, $W=20\mu\text{m}$) and $C_{\text{in}}=200\text{fF}$, $I_{\text{leak}}=1\text{nA}$ and $\tau=50\text{ns}$, $g_m=500\mu\text{S}$ (typical LHC pixel detector):

$$\left(\frac{\text{ENC}}{e^-}\right)^2 = 115 \cdot \frac{\tau}{10 \text{ ns}} \cdot \frac{I_{\text{leak}}}{1 \text{ nA}} \rightarrow 575$$

$$+ 388 \cdot \frac{10 \text{ ns}}{\tau} \cdot \frac{\text{mS}}{g_m} \cdot \left(\frac{C_{\text{in}}}{100 \text{ fF}}\right)^2 \rightarrow 621$$


$$+ 74 \cdot \left(\frac{C_{\text{in}}}{100 \text{ fF}}\right)^2 \rightarrow 296$$

$\left. \begin{array}{l} \rightarrow 575 \\ \rightarrow 621 \\ \rightarrow 296 \end{array} \right\} \text{ENC}=40 e^-$



Noise vs. Shaping Time

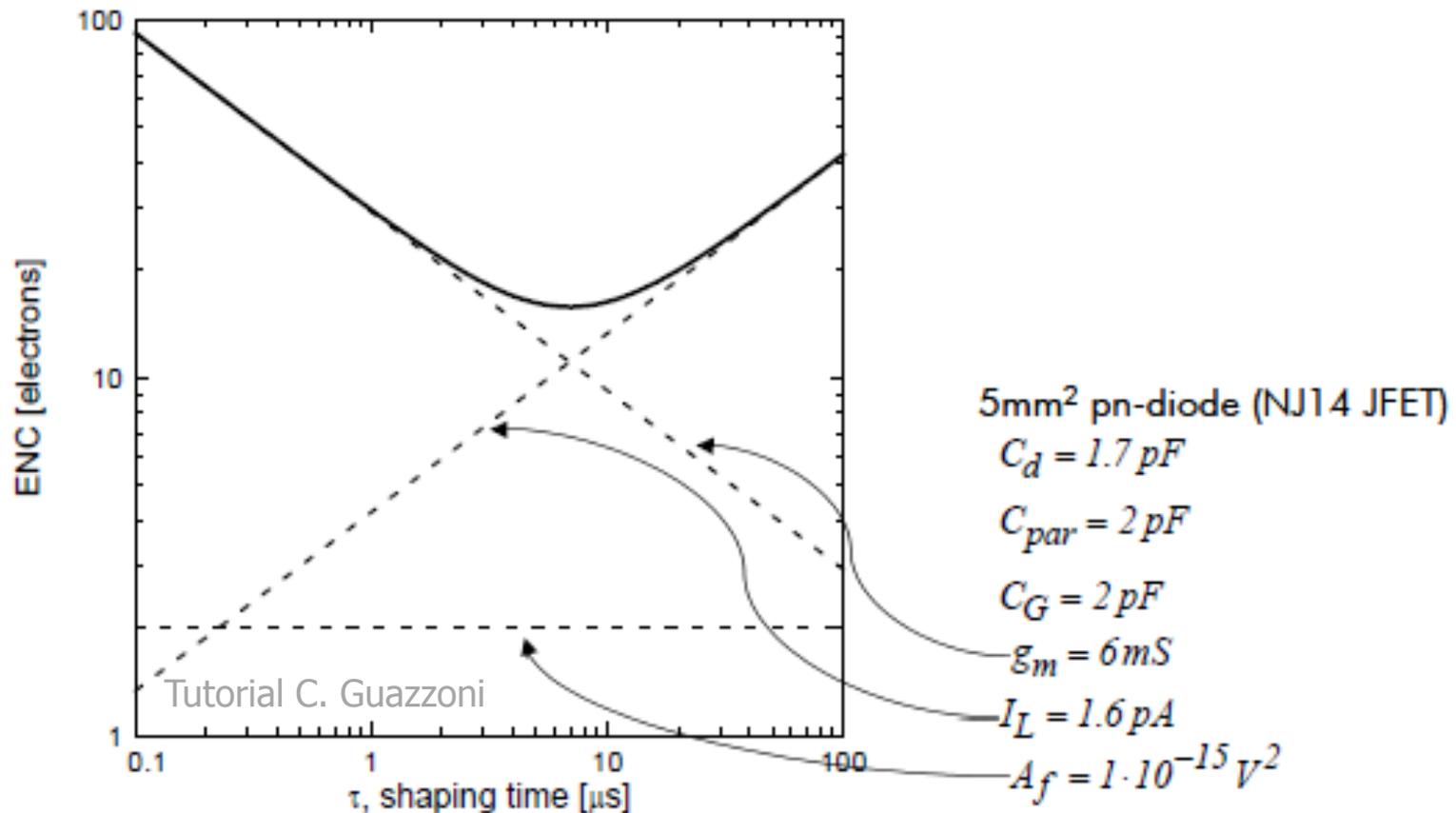- Long shaping: leakage noise contributes more
- Short shaping: Amplifier white noise, worsened by C_{Det}
- Always: Amplifier $1/f$ noise, worsened by C_{Det}





MISC

- For large MOS, the gate can have a significant resistance which can add thermal noise. Must use layout with multiple gate contacts.
- The noise coefficient γ can increase (quite) a lot for very short channel MOS. In general do NOT use shortest MOS if you need low noise.
- Noise models are often not very reliable. In particular 1/f noise can be run dependent. You may want to include noise test structures (i.e. large MOS arrays of the geometry you use)
- Noise can also be treated in transient simulation (enable 'transient noise' button). Good for nonlinear systems (comparator) and 'quick look'. Large simulation effort due to small time steps (high freq. noise components).
Provides less understanding where noise comes from...



Summary

- Resistor, MOS and Diodes (and BJTs) have noise
- Noise is described by its spectral density
- Noise contributions are propagated through the circuit with the respective frequency transfer function

- Total RMS noise is the integral over the spectra

- Current sources require MOS with low g_m .
 - This leads to larger saturation voltages...
- Amplifiers require MOS with large g_m

- Low bandwidth → Low Noise
- Filters limit bandwidth and thus reduce noise, but also decrease the signal...




Exercise 1: Noise in Resistors

- Connect a $1\text{k}\Omega$ resistor (from AnalogLib) on one side to gnd!
- Simulate the voltage noise spectrum on the other side
 - Is it flat?
 - Is the absolute value what you expect?
Note how the prefixes (e.g. 'a' for Atto) are used...
- Add an ideal low pass filter with corner frequency 10 MHz
 - Use a simple RC and set the 'Generate Noise?' flag of R to 'No'
 - Choose R much larger than $1\text{k}\Omega$ to not 'load' the 'source'
 - How does the spectrum look like?
 - How much has noise decreased at the corner?
 - Integrate over a large frequency range to get the rms noise
 - Is it what you expect?
- Determine the overall RMS noise (`totalNoise("noise" nil nil)`)
 - Is it what you calculate?



Exercise 1: Solution

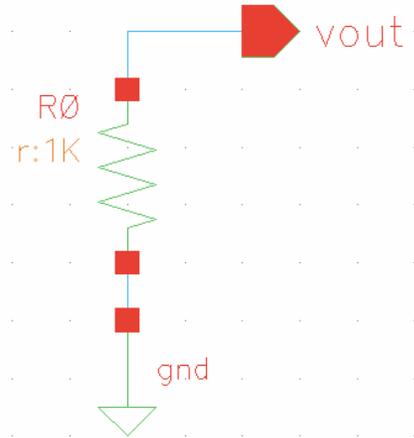

Sweep Range

- Start-Stop
- Center-Span

Start: 100 Stop: 1000

Sweep Type: Automatic

Add Specific Points:

Output Noise

voltage

Positive Output Node: /vout

Negative Output Node: gnd!

Input Noise: none



$$4kT \times 10k\Omega = 1.64 \times 10^{-17} V^2/Hz = 16.4 aV^2/Hz - OK$$


$$aV^2 = a \times V^2$$

NOT: (aV)²




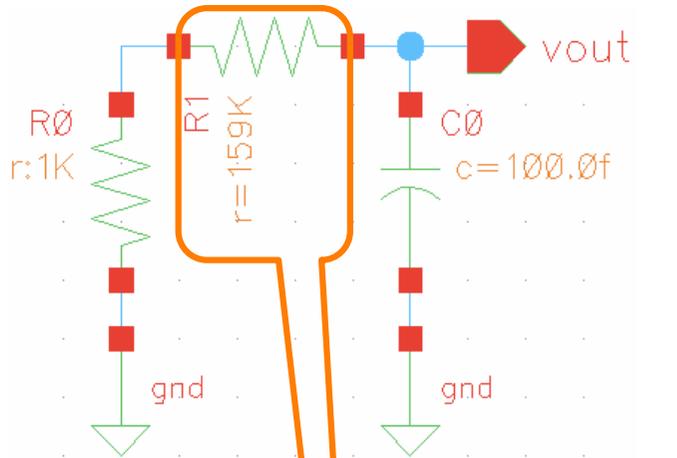Exercise 1: Solution

▪ $\omega = 2 \pi \nu = 1/(RC) \rightarrow R = 1/(2 \pi \nu C) = 159k\Omega$ (for $C = 0.1pF$)



Model name	
Resistance	159K Ohms
Length	
Width	
Multiplier	
Scale factor	
Temp rise from ambient	
Temperature coefficient 1	
Temperature coefficient 2	
Resistance Form	
Generate noise?	no

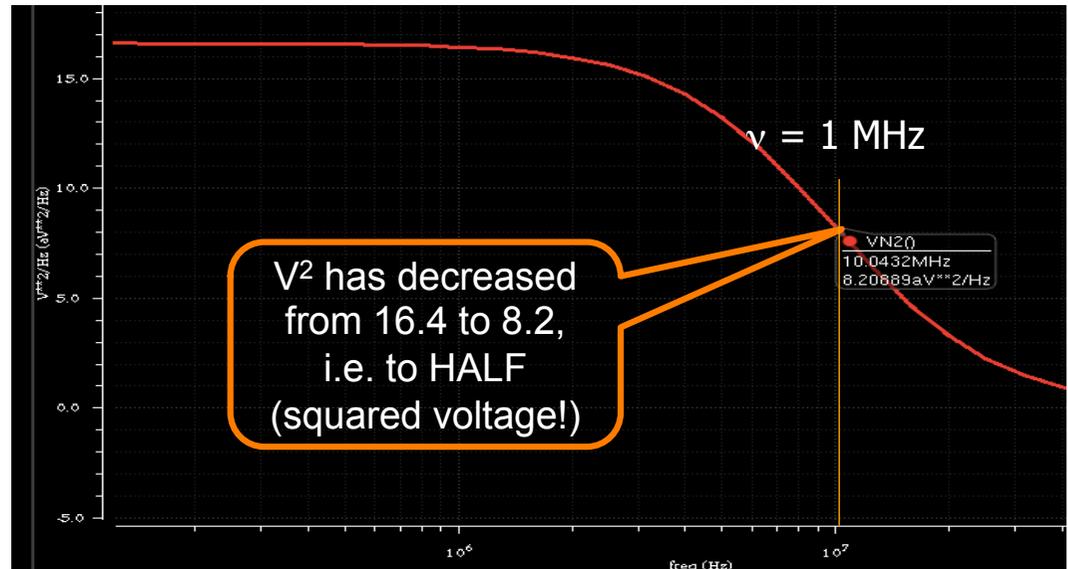

▪ $v_{RMS}^2 = 16.4 \text{ aV}^2 \times \nu_{Brick}$
 $= 16.4 \text{ aV}^2 \times \pi/2 \times 10 \text{ MHz}$
 $= 257 \text{ pV}^2$

Outputs			
	Name/Signal/Expr	Value	Plot
1	vout		<input checked="" type="checkbox"/>
2	totalNoise("noise" nil nil nil)	259.4p	<input checked="" type="checkbox"/>



Exercise 2: Noise in MOS Transistors




- Instantiate an NMOS and a PMOS of $W/L = 30\mu\text{m}/0.3\mu\text{m}$
- Apply a fixed drain voltage of, say, 1V
- Find the gate voltages required for drain currents of $100\mu\text{A}$
 - Use a DC sweep
- Determine the transconductance for this operation point
 - Use an AC analysis
 - What g_m values do you get? Compare NMOS and PMOS.
- Observe the noise current spectra at the drains
 - Set the drain voltage source as *probe instance* to see *currents*
 - You have to run NMOS and PMOS separately
- What are the white noise magnitudes?
 - Do the values roughly match with what you expect from g_m ?
- Where are the $1/f$ corners? (Use Log Plot!)
- For one device, increase the current and observe the spectrum





Exercise 2: Solution

- For my technology (UMC180nm):
 - V_{gate} : NMOS = 511 mV, PMOS = 649 mV (PMOS needs more because geometry and current are the same, but not so much, because we are close to w.i. given the 'wide' devices)
 - g_m : NMOS: 1.7mS, PMOS: 1.1mS

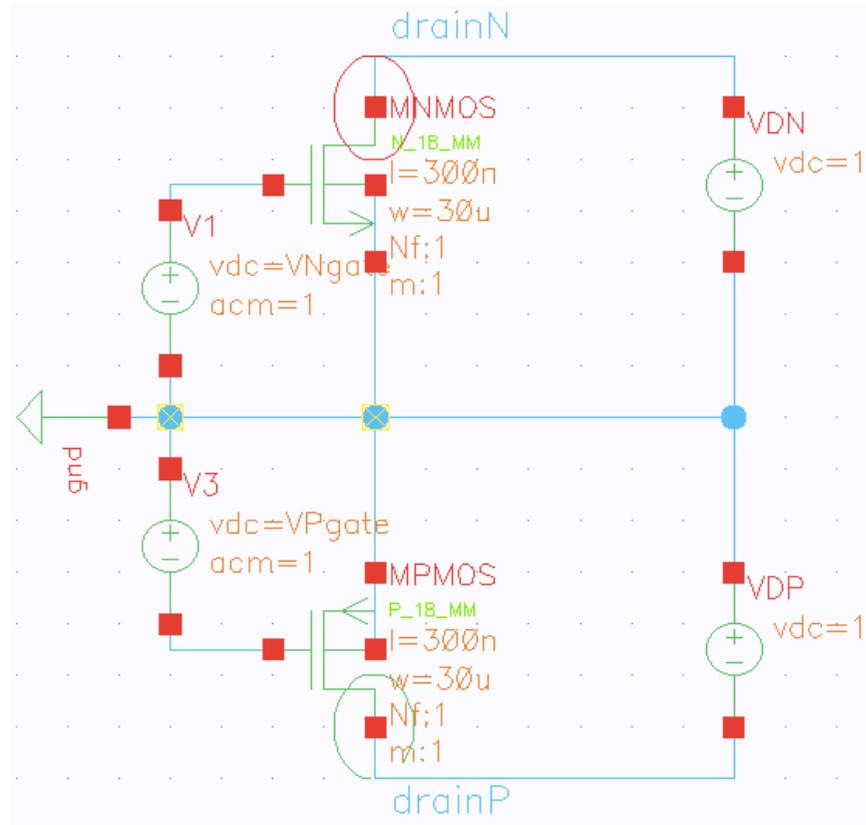



Exercise 2: Solution

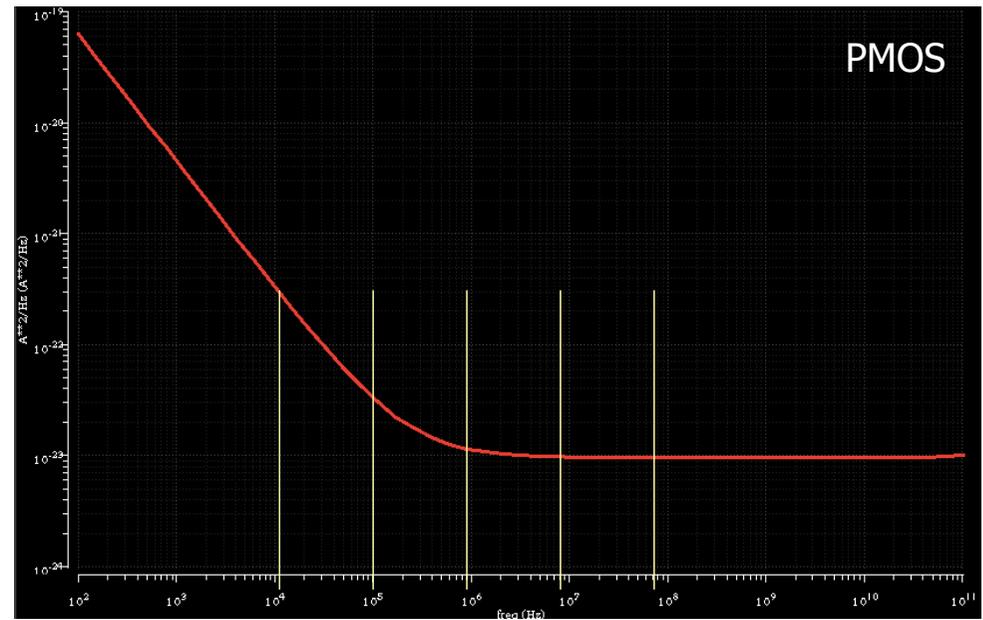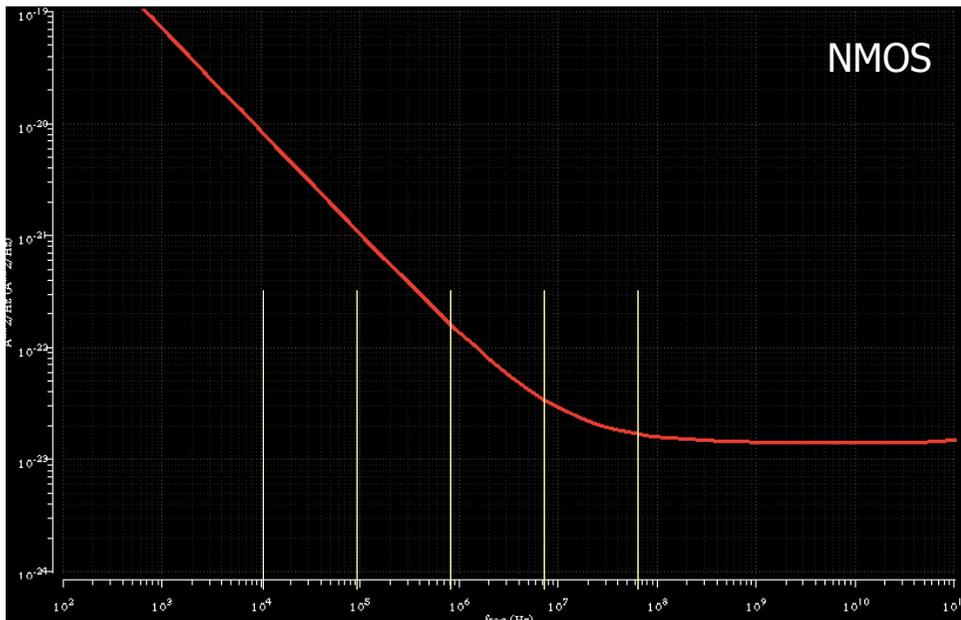


- Expect noise currents (NMOS/PMOS):
 - $2/3 \times 16.4 \text{ aVA/Hz} \times 1.7/1.1\text{mS} = 19/11.9 \text{ yA}^2/\text{Hz}$
- Simulated:
 - NMOS: $14.3/9.7 \text{ yA}^2/\text{Hz}$ - OK
- Corners: $\sim 50 / 1 \text{ MHz}$.
PMOS is much better @ comparable thermal noise



Exercise 2: Solution

- With higher gate voltage (higher current, higher g_m (1.5- >4mS)) output current noise increases (left), but input voltage noise decreases (right)
- 1/f noise at input is 'fairly' constant

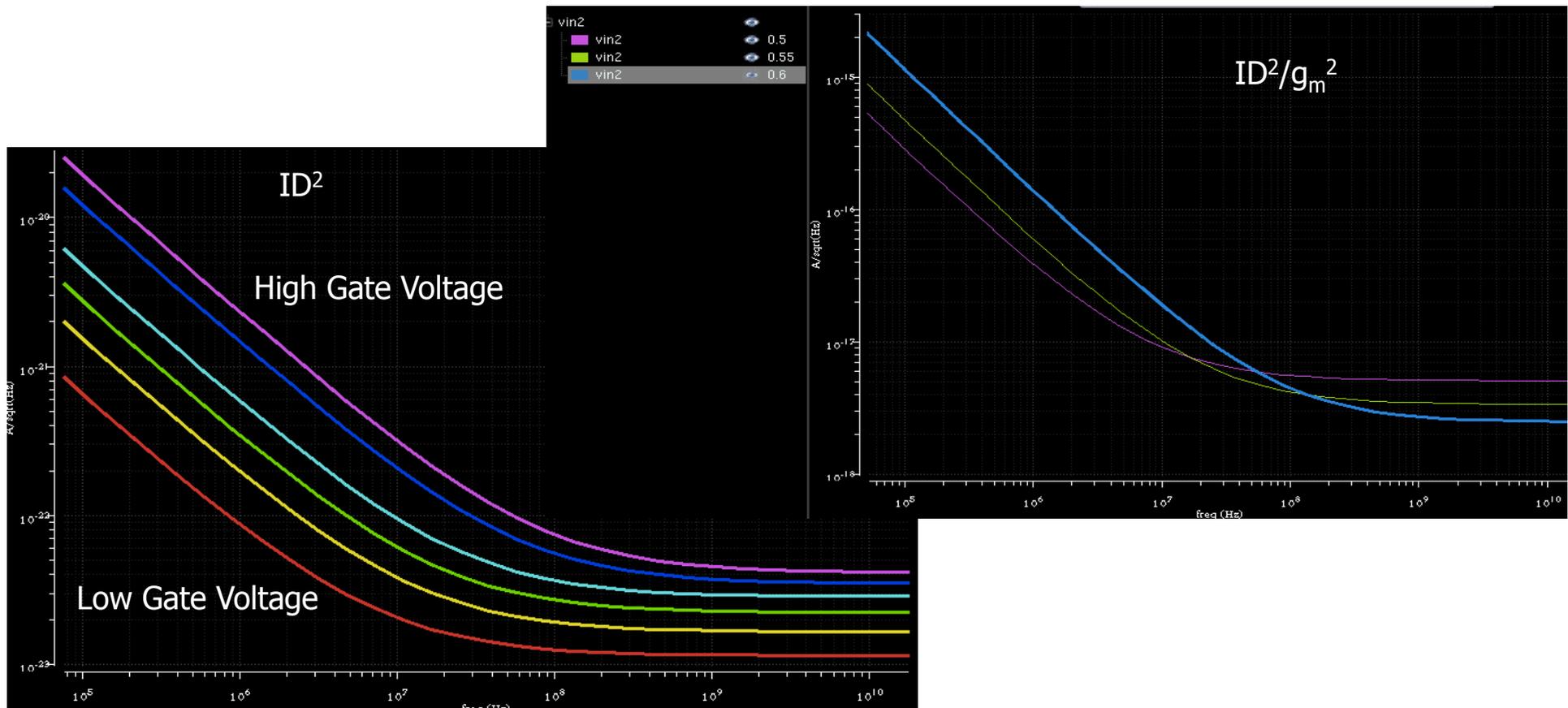




Exercise 3: Noise in Current Mirror

- Make an 1:1 PMOS current mirror, using the same PMOS as in the previous exercise.
 - (PMOS is better for lower $1/f$ noise here)
- Load the output with 1V. Inject a current at the input and verify that you get the current at the output
- Plot the noise at the output.
- Now add a decoupling capacitor (to gnd!) to the bias node.
- Plot the noise spectrum for $C_{\text{dec}} = 1/10/100/\dots$ fF
 - Observe how larger decoupling cuts down the noise at lower frequencies
 - Why is there no added noise at very high frequency ?
 - Check that the 'corner' frequencies for various caps are where you expect them !



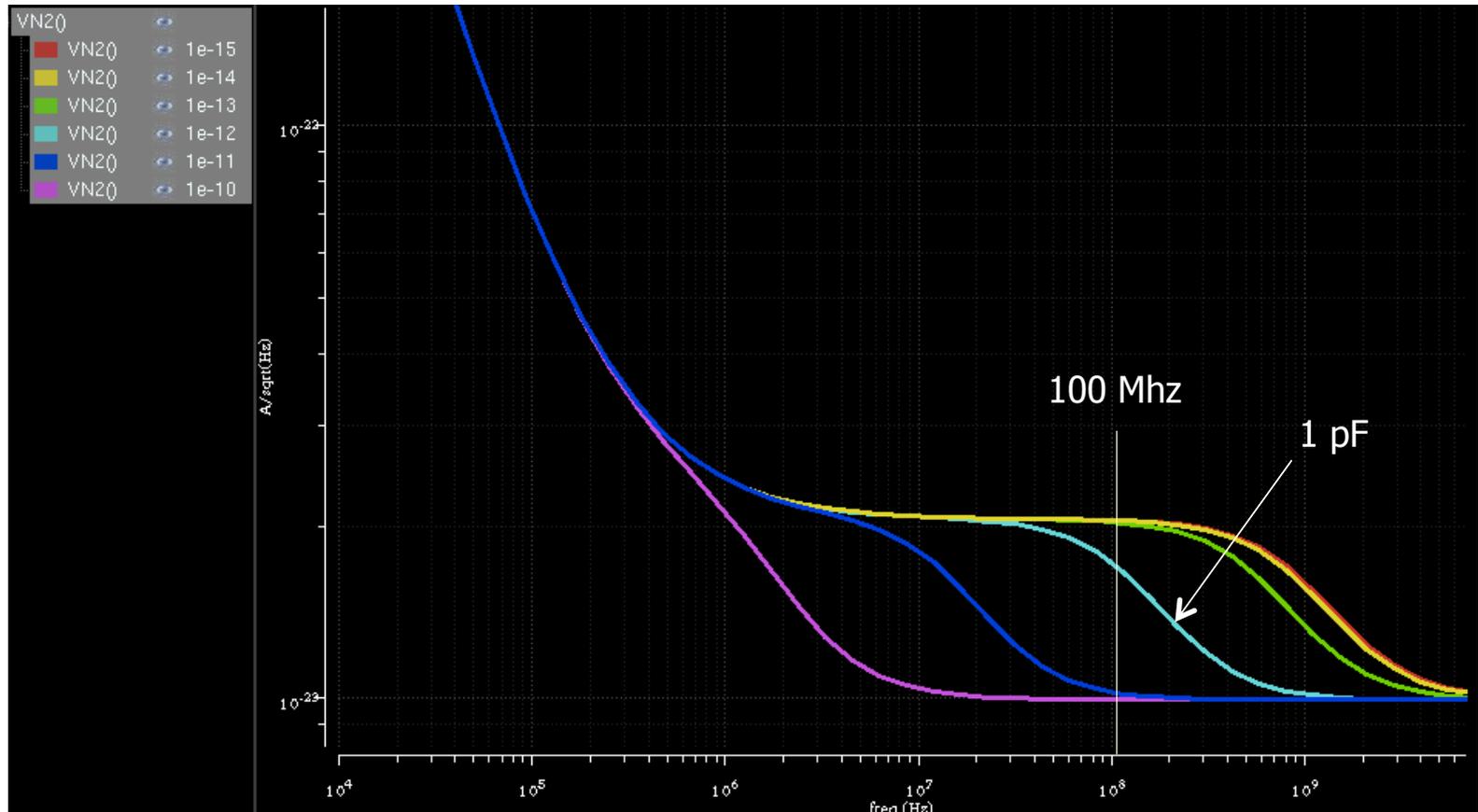Exercise 3: Solution

- Simulation for $C=1\text{fF}$ (red), 10fF , ... 100pF (pink)



- The corner is at $\omega = g_m / C$ with $g_m \sim 1\text{mS}$.
For 1pF this gives $\omega \sim 1\text{GHz}$, i.e. $\nu \sim 130\text{ MHz}$




Exercise 4: Charge Amplifier

- Design a charge amplifier followed by a (passive) CR-RC filter with corner frequency $\tau \sim 1\mu\text{s}$ with input cap of 1 pF.
 - For the amplifier, use a simple NMOS ($W/L \sim 10\mu/0.3\mu$) gain stage with a PMOS current mirror load ($30\mu/0.3\mu$). Decouple the bias node.
 - Bias at $\sim 100\mu\text{A}$.
 - Use a feedback capacitor of 100 fF. Put a $100\text{M}\Omega$ resistor in parallel to set the dc operation point.
 - Implement the filter as passive RCs, with parameterized τ . Use vcvs buffering between the stages. You may want to switch off noise in the resistors...
- In a transient simulation, inject a 1fC charge (1V step across a 1fF injection capacitor)
 - Observe the output of preamp / shaper, and the preamp input
 - Is the virtual ground at the input 'ok'?
 - Is the shaper signal as expected (amplitude, peaking)? Vary τ !



Exercise 4: Transient Simulation

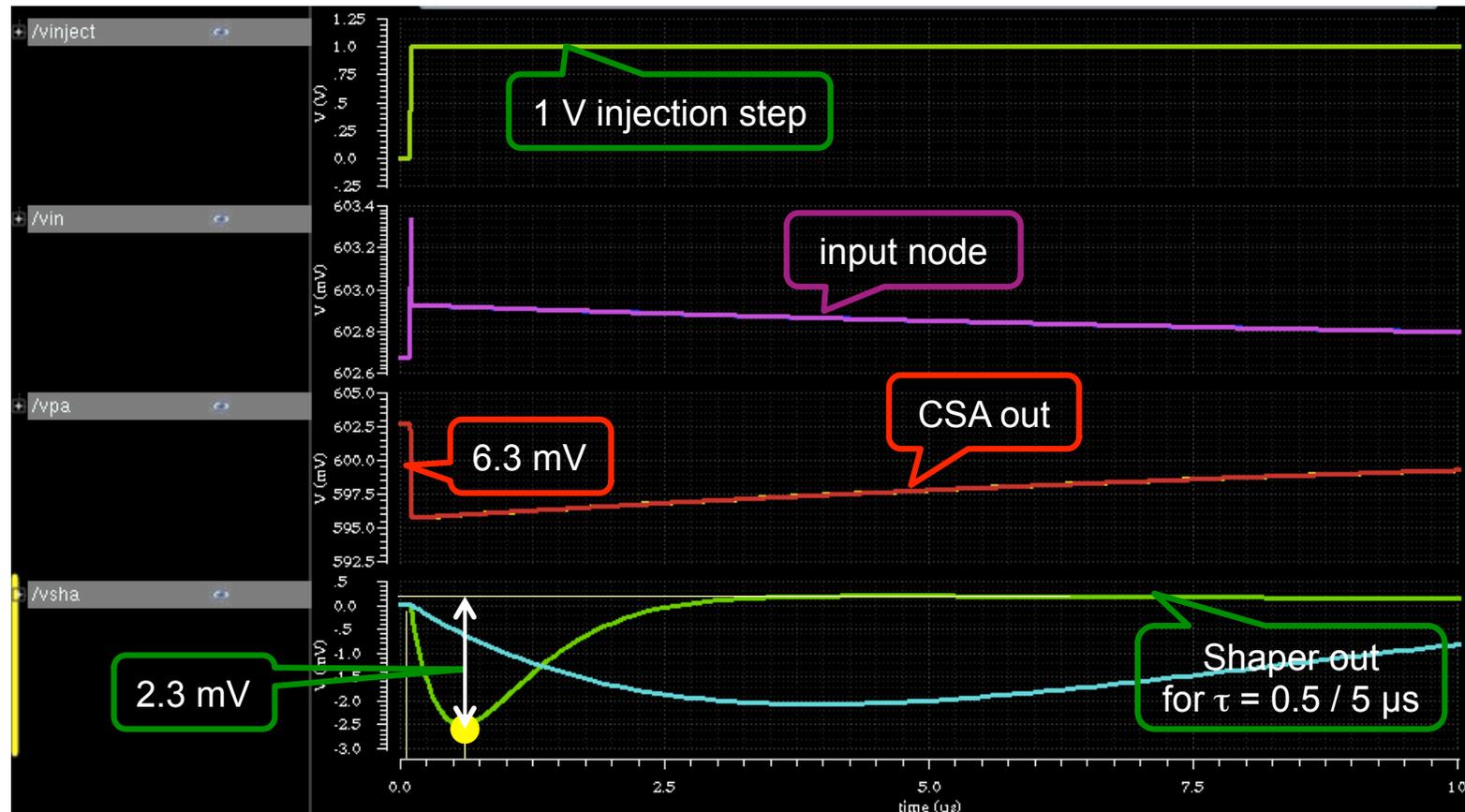

$$\Delta V_{CSA} = Q_{in}/C_f = V_{in} \times C_{in}/C_f = 1V \times 1fF/100fF = 10 \text{ mV (see 6.3 mV)}$$

$$\Delta V_{SHA} = \Delta V_{CSA} / e \text{ (p.43)} = 3.7 \text{ mV (see 2.3 mV)}$$

-> Gain x C_f is not much larger than C_{in} so that input moves

-> Shapes for long shaping are degraded by preamp discharge



Exercise 4: Charge Amplifier

- Perform a noise simulation for $\tau = 0.5 \mu\text{s}$ and $5 \mu\text{s}$

- For $\tau = 1 \mu\text{s}$:
 - Determine the total noise at the shaper output by integration
 - Take the square root to get the RMS (voltage) noise
 - Divide by the signal for one electron to get the ENC
 - What do you get ?

- Double C_{in} to 2 pF
 - What is the ENC now?

- Find out which noise type / contribution dominates your circuit by using Noise Analysis



Exercise 4: Solution


- Noise sim:

- For $\tau = 1 \mu\text{s}$, $C_{\text{in}} = 1 \text{ pF}$:

- Noise Integral: $17 \times 10^{-9} \text{ V}^2$ ($30 \times 10^{-9} \text{ V}^2$ for 2 pF)
- RMS noise (square root): $130 \times 10^{-6} \text{ V}$ (173)
- We get 2.3/2.0 mV for 1fC ($\sim 6250 \text{ e}$) $\rightarrow 3.7/3.2 \times 10^{-7} \text{ V/e-}$
- For 1pF: $\text{ENC} = 130 \times 10^{-6} \text{ V} / 3.7 \times 10^{-7} \text{ V/e} = 350 \text{ e-}$
- For 2pF: $\text{ENC} = 173 \times 10^{-6} \text{ V} / 3.2 \times 10^{-7} \text{ V/e} = 540 \text{ e-}$

- Notes:

- Gain of amplifier is very low
- More noise components than just input....

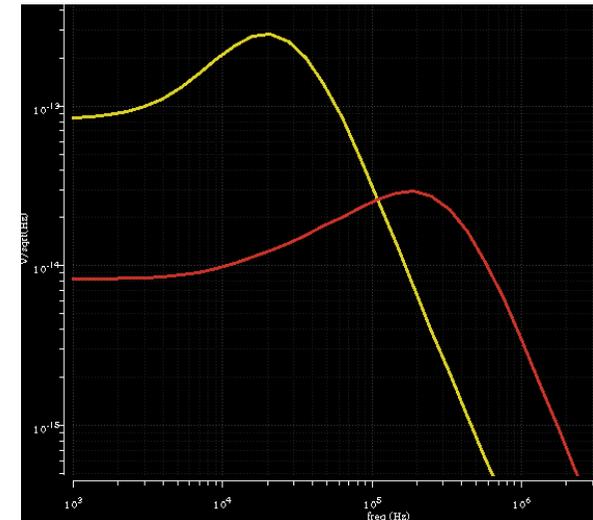



Exercise 4: Solution

■ Noise Summary:

Device	Param	Noise Contribution	% Of Total
/M1	fn	9.72616e-09	57.09
/R1	rn	4.17986e-09	24.53
/R0	rn	2.098e-09	12.31
/Rf	rn	8.74026e-10	5.13
/M1	id	6.28512e-11	0.37
/MN	fn	4.92349e-11	0.29
/MN	id	4.7543e-11	0.28
/M1	rs	3.66483e-14	0.00
/MN	rs	1.25303e-14	0.00
/M1	rd	2.44555e-17	0.00

Integrated Noise Summary (in V²) Sorted By Noise Contributors
Total Summarized Noise = 1.70377e-08

1/f noise input MOS

Oups: Noise in the Rs of the filter...

Noise in Feedback Resistor

Channel Noise in input MOS

- We are totally 1/f noise limited.... (slow shaping)
→ larger area MOS, PMOS,...
- I forgot to switch off the resistive noise in the shaper...