

AdvancedAnalog Building Blocks

Two Stage amplifiers

Fully Differential amplifiers



Albert Comerma (PI)
(comerma@physi.uni-heidelberg.de)



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386


[Course web](#)

SoSe 2017


OTA and OPamp

- **OTA:** *Operational Transconductance Amplifier*
Voltage input \rightarrow Current output
- **OPamp:** *Operational Amplifier*
Voltage input \rightarrow Voltage output (buffered)


OTA

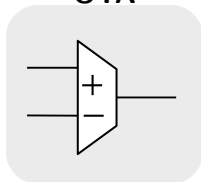

OTA+buffer

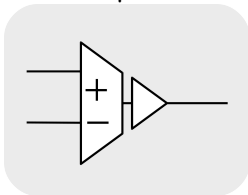

OPamp

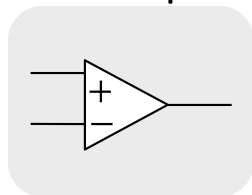


Key parameters;

- Gain Bandwidth Product
- DC Gain
- Stability (Phase margin)
- Biasing (symmetry and matching)



General OPamp model

General model

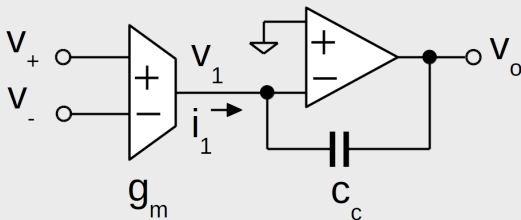


- First stage OTA; $i_1 = (v_+ - v_-) \times g_m = v_{diff} \times g_m$
- Virtual short circuit in v_1 ; $\rightarrow \frac{v_o}{i_1} = -\frac{1}{sC_c}$
- Thus; $|A_v(f)| = \frac{g_m}{2\pi \times f \times C_c}$
- $GBW = A_v(f)_{f_T=1} = \frac{g_m}{2\pi \times C_c}$



Miller OTA - Circuit


Two stage amplifier;

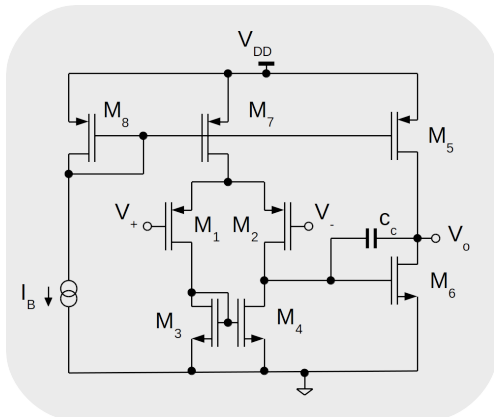- First stage: OTA
- Second stage: Inverter
- Miller capacitance between first and second stage



Miller OTA - Circuit nodes

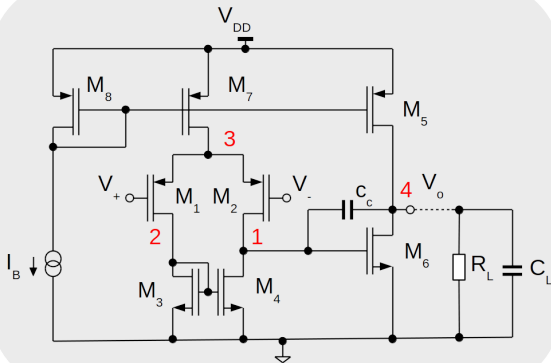- 3-node for analysis (3 virtually grounded in ac)
- Load affects stability!




$$\begin{aligned} \left(\frac{W}{L}\right)_8 &= \left(\frac{W}{L}\right)_7 \\ \left(\frac{W}{L}\right)_5 &\gg \left(\frac{W}{L}\right)_7 \\ &\text{(Typically } \times 10) \end{aligned}$$



Miller OTA - Circuit DC gain

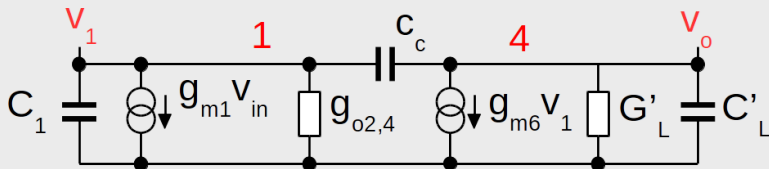- Small-signal model (node 2 is low-resistance node).



$$g_{o2,4} = g_{o2} + g_{o4}$$




$$G'_L = G_L + g_{o5} + g_{o6}$$

$$C'_L = C_L + C_4$$

$$A_v = \frac{v_o}{v_{in}} = \frac{v_i}{v_{in}} \frac{v_o}{v_i} = \left(\frac{g_{m1}}{g_{o2,4}} \right) \left(\frac{g_{m6}}{G'_L} \right) = A_{v1} A_{v2}$$



Miller OTA - Pole splitting effect

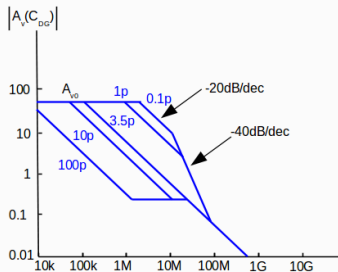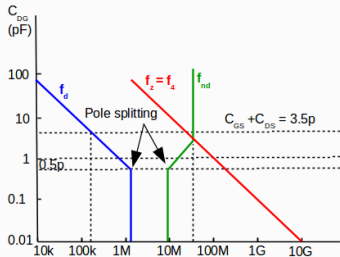
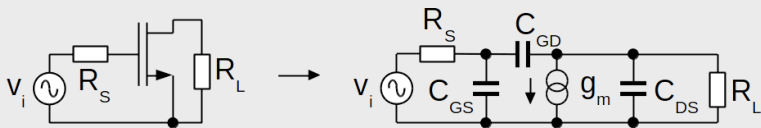


Miller OTA - Circuit poles

- Circuit poles without C_c
 - $f_{p1} = \frac{g_{o2,4}}{2\pi C_1} \rightarrow C_1 = C_{GD2} + C_{DB2} + C_{GD4} + C_{DB4} + C_{GS6}$
 - $f_{p4} = \frac{G'_L}{2\pi(C_L + C_4)} \rightarrow C_4 = C_{GD5} + C_{DB5} + C_{DB6}$
 - $f_{p2} = \frac{g_{m3}}{2\pi C_2} \rightarrow C_2 = C_{GS3} + C_{DB3} + C_{GS4} + C_{GD4} + C_{GD1} + C_{DB1}$
- f_{p2} goes to high frequency forming a pole-zero pair, so can be neglected.
- **Adding C_c the dominant pole becomes more dominant;**
 $BW \approx f_d = \frac{g_{o2,4}}{2\pi A v_2 C_c}$ (applying Miller effect)
 $GBW \approx \frac{g_{m1}}{2\pi C_c}$
- Non-dominant pole, assuming $C_1 \ll C_c, C'_L$ and $g_{m6} \gg G'_L$;
 $f_{nd} \approx \frac{g_{m6}}{2\pi C'_L}$
- $PM \approx 90^\circ - \arctg \frac{GBW}{f_{nd}} \rightarrow f_{nd} = 3GBW$ ($PM \approx 70^\circ$)



Miller OPamp - C_c and GBW, PM

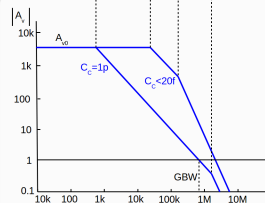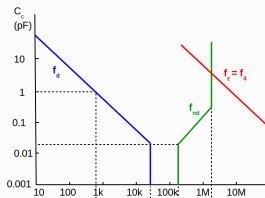

- Variation of poles and zeros with C_c
- C_c value is fundamental to achieve enough GBW and PM
- $GBW \approx \frac{g_{m1}}{2\pi C_c}$
- $PM \approx 90^\circ - \arctg \frac{GBW}{f_{nd}}$
- $f_{nd} \approx \frac{g_{m6}}{2\pi C_L'} , g_m = \frac{2I_D}{(V_{GS} - V_T)}$
- $f_{nd} = 3GBW$ ($PM \approx 70^\circ$)



Miller OTA - Steps for design

- Take a value for $I_{D6} = I_{D5}$
- For M_6 ;
 1. Choose the overdrive voltage (ex. $V_{GS} - V_T = 0.2$).
 2. Obtain $g_{m6} = \frac{2 \cdot I_{D6}}{V_{GS6} - V_T}$ and $\left(\frac{W}{L}\right)_6 = \frac{g_{m6}}{K'(V_{GS5} - V_T)}$
 3. Use minimum L_6 to get W_6
- Repeat for M_5 (now use $V_{GS} - V_T = 0.5$ for better matching, reduced swing)
- Calculate C_c for desired A_v .
- Use around a factor 10 between M_5 and first stage bias.
- Iterate on simulation to fine tune values.




Miller OTA - characteristics

- Common mode input:


$$V_{CMinMAX} = V_{DD} - V_{GS1} - V_{DS7}$$
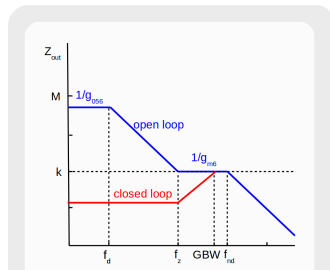
$$V_{CMinMIN} = V_{SS} + V_{GS3} - V_{DS1} - V_{GS1}$$
- Output voltage range, with no R_L rail-to-rail with some distortion due to MOS linear operation close to rails.
- Slew rate, non linear effect. Maximum rate output voltage variation. $SR = \frac{I_{bias1^{st} stage}}{C_C}$
- Output impedance: (will limit output voltage when R_L)



Fully Differential - schematic

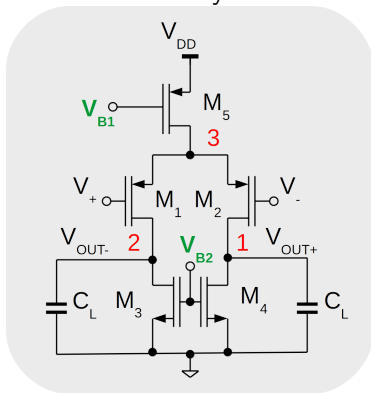Fully differential amplifiers show excellent CMRR and PSRR which make them very useful for mixed-signal design.




- No current mirror as load, just current sources.
- Nodes 1 and 2 become symmetric.
- $GBW \approx \frac{g_{m1}}{2\pi C_L}$

Problem


Keep all transistors saturated, regulation of $V_{B1,2}$

Fully Differential - CMFB

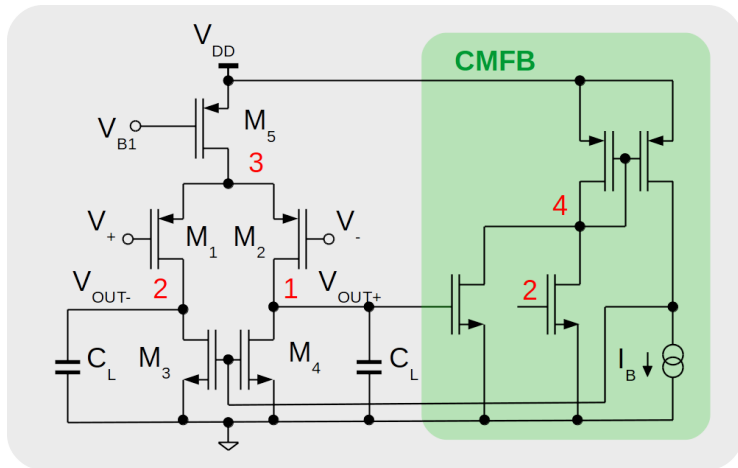

- The common-mode output voltage is sensed and fed back to load sources (CMFB: Common-Mode FeedBack).

Fully Differential - CMFB

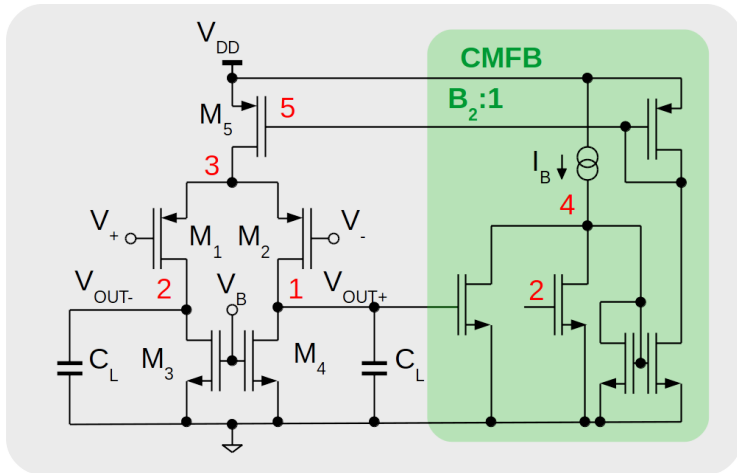

- More usual implementation



Exercise 1: Miller OTA

Design a Miller OTA with the following specifications:

- $A_{vDC} = 100$
- $BW = 100MHz$
- $PM > 70^\circ$
- Try to minimize power consumption.

Use $R_L = 1M$, $C_L = 1pF$.

Exercise 2: Fully differential amplifier

Design a Fully differential amplifier with CMFB with the following specifications:

- $A_{vDC} = 100$
- $BW = 100MHz$
- $PM > 70^\circ$
- Try to minimize power consumption.

Use $R_L = 1M$, $C_L = 1pF$.