


Improving the ADC board

Liliane Dias
Fernandes
June 2013

Outline



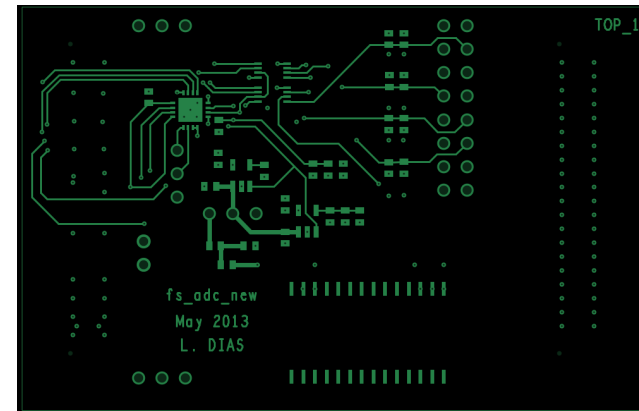- Context and needs
- First problem
- Second problem
- New board
- Results



Context and needs







- Two boards
- Multiplexers, termination, operational amplifier
- Distortion
- Too noisy

First problem




Distortion of the signal

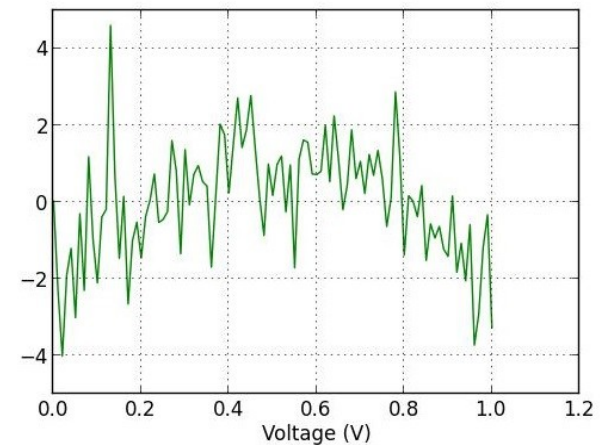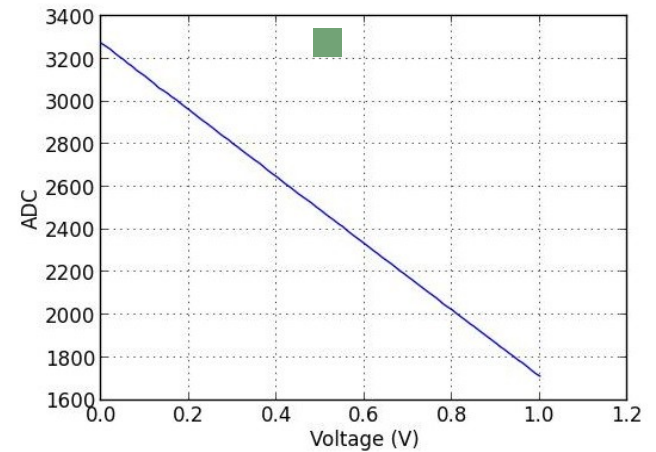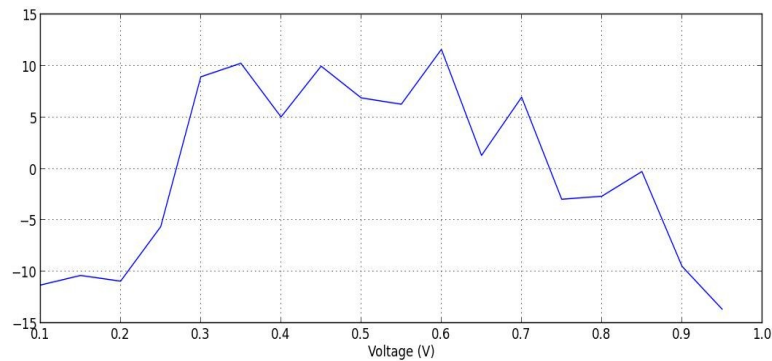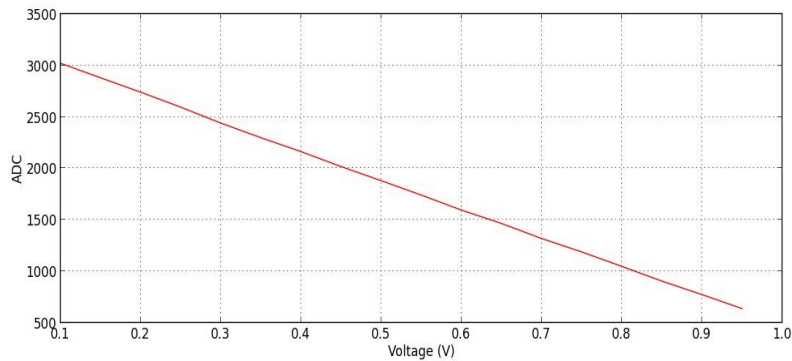


First problem



Simulation of the operational amplifier

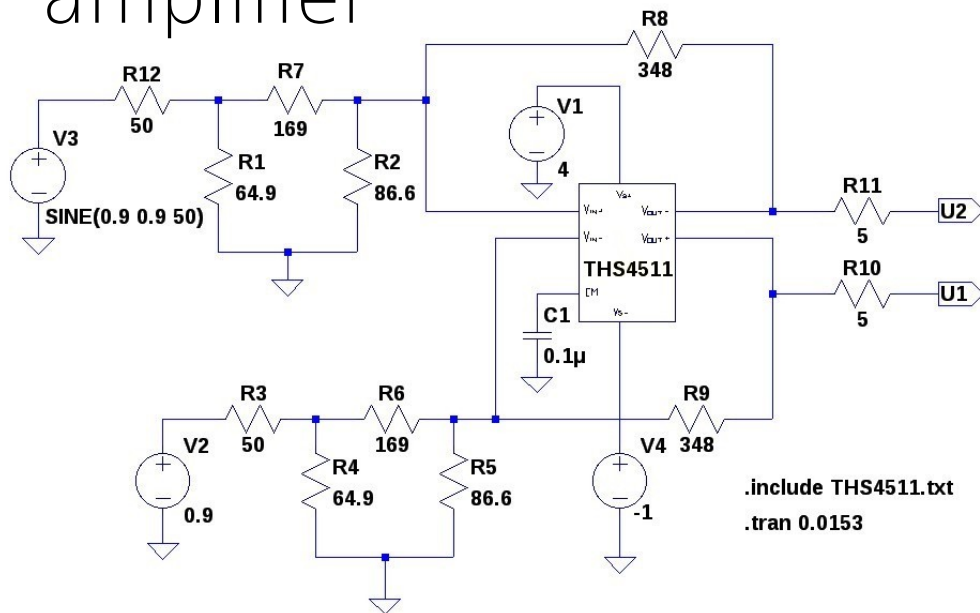


No distortion shown

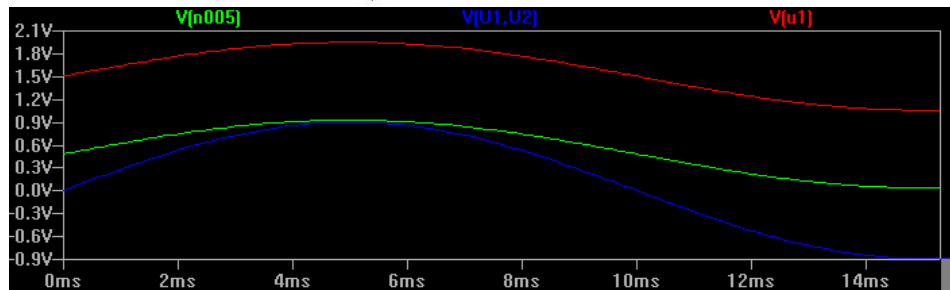

First problem




With and without the multiplexer

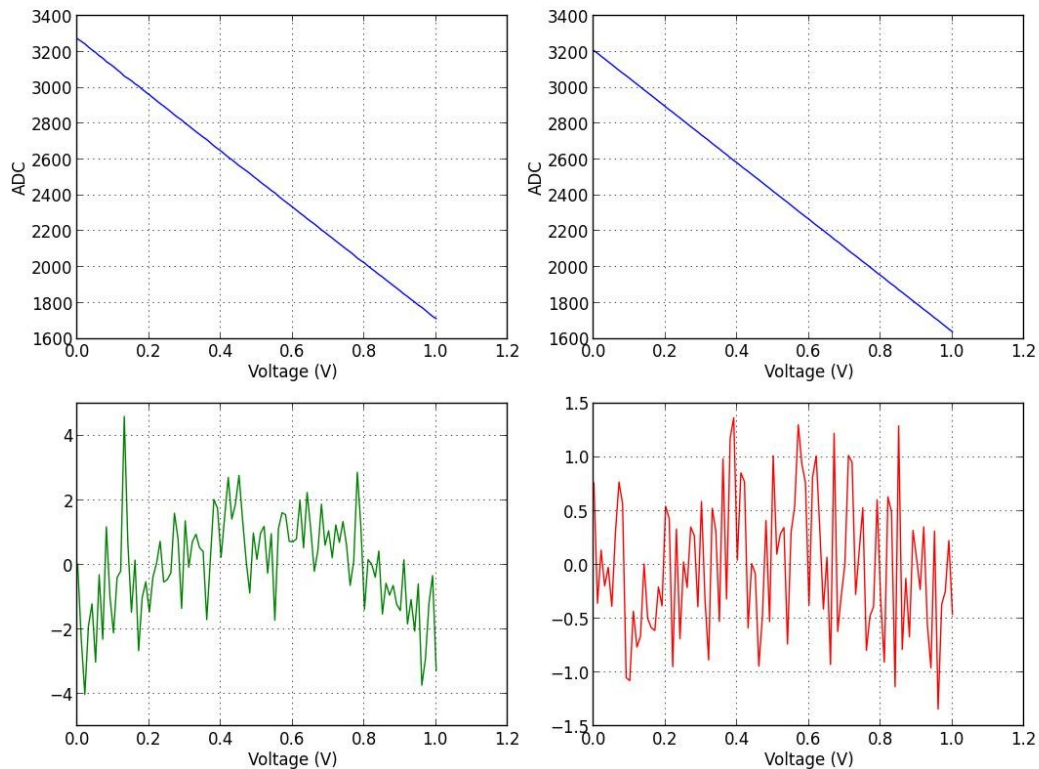

Residual resistor of the multiplexer


Current in the termination

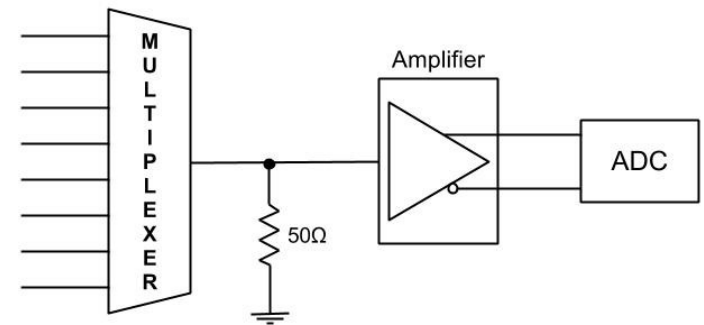

First problem



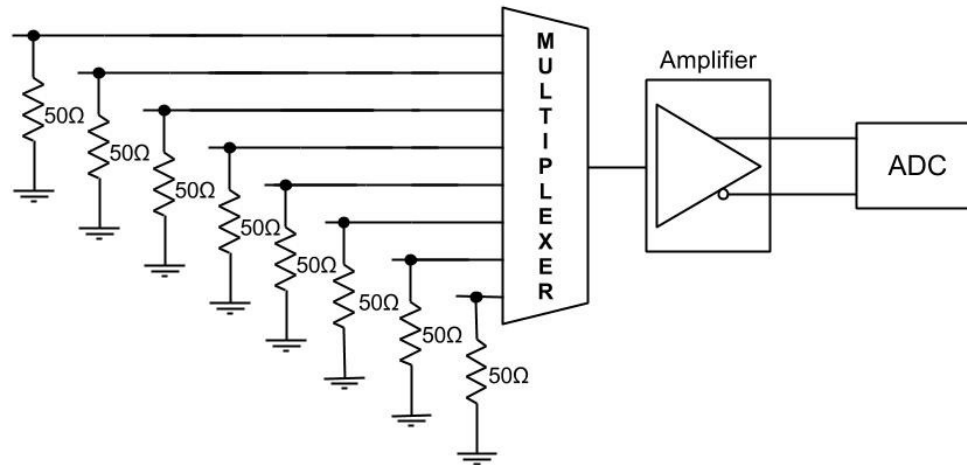Fix the multiplexer problem move terminations




First problem



New amplifier : LMH6518

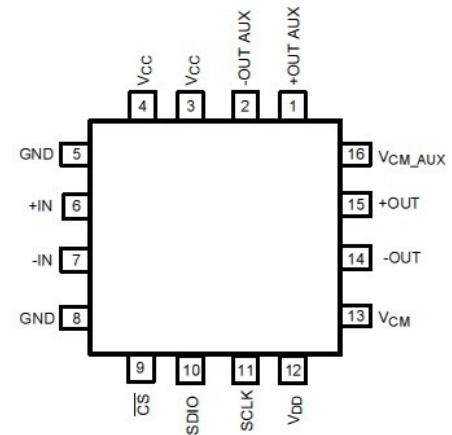
- High impedance input
- Programmable low pass filter
- Programmable gain



Second problem




Supplied directly

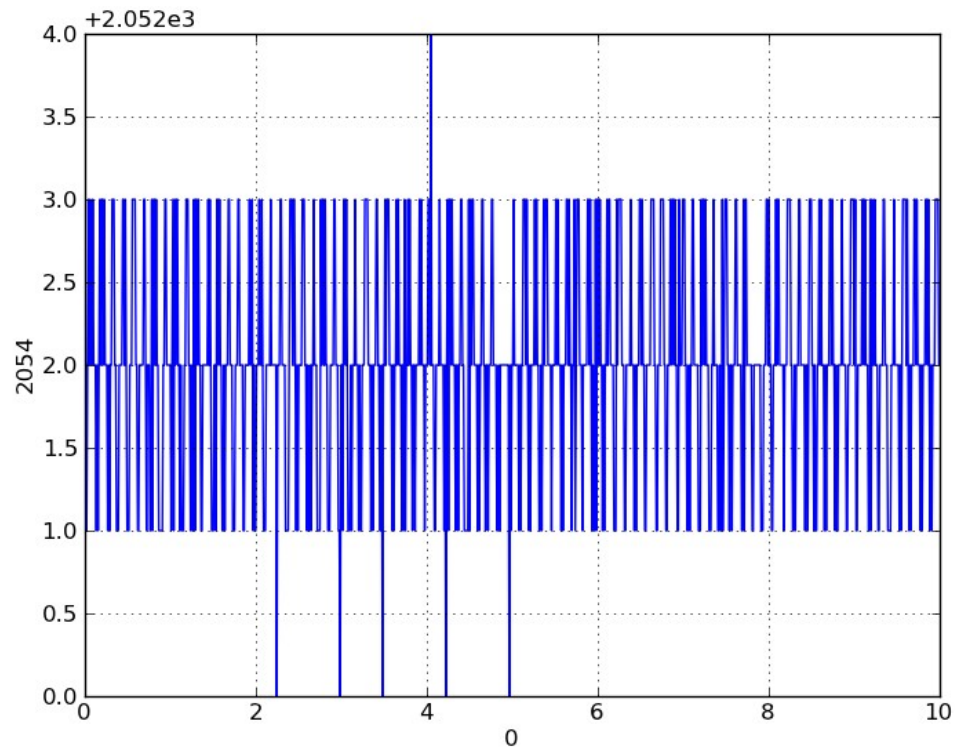

Second problem




With the second board

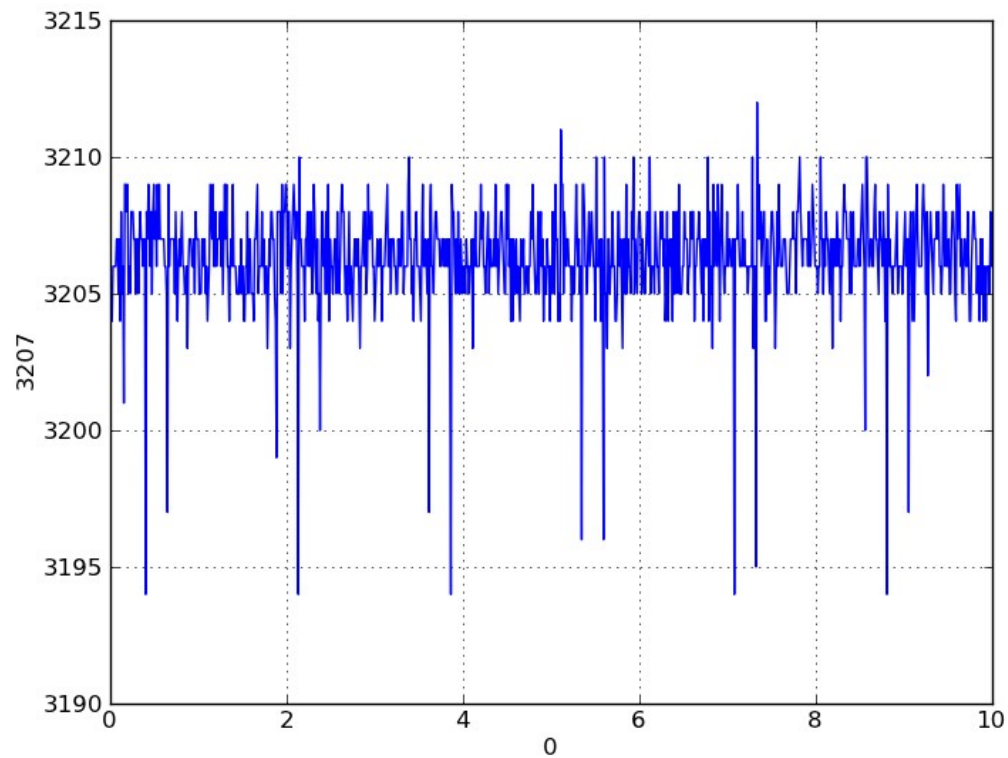

Second problem



To fix the problem

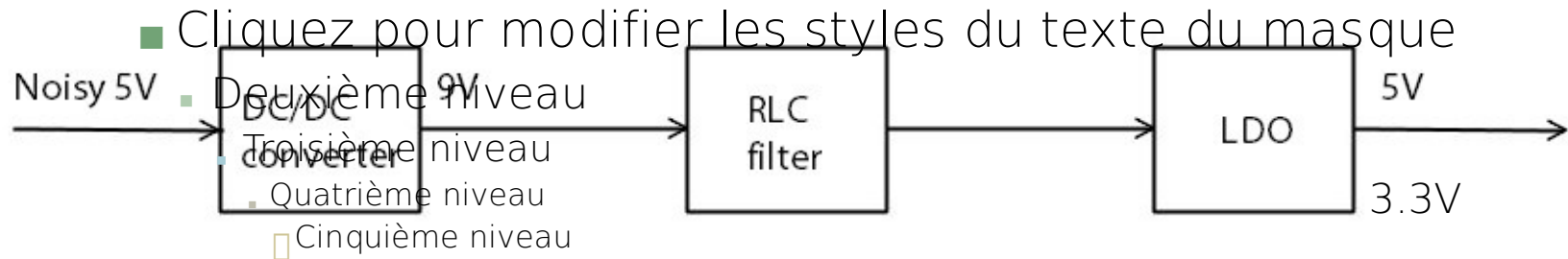


New board



- Multilayered circuit board
- Two types of ground
- Mechanical connector


New board

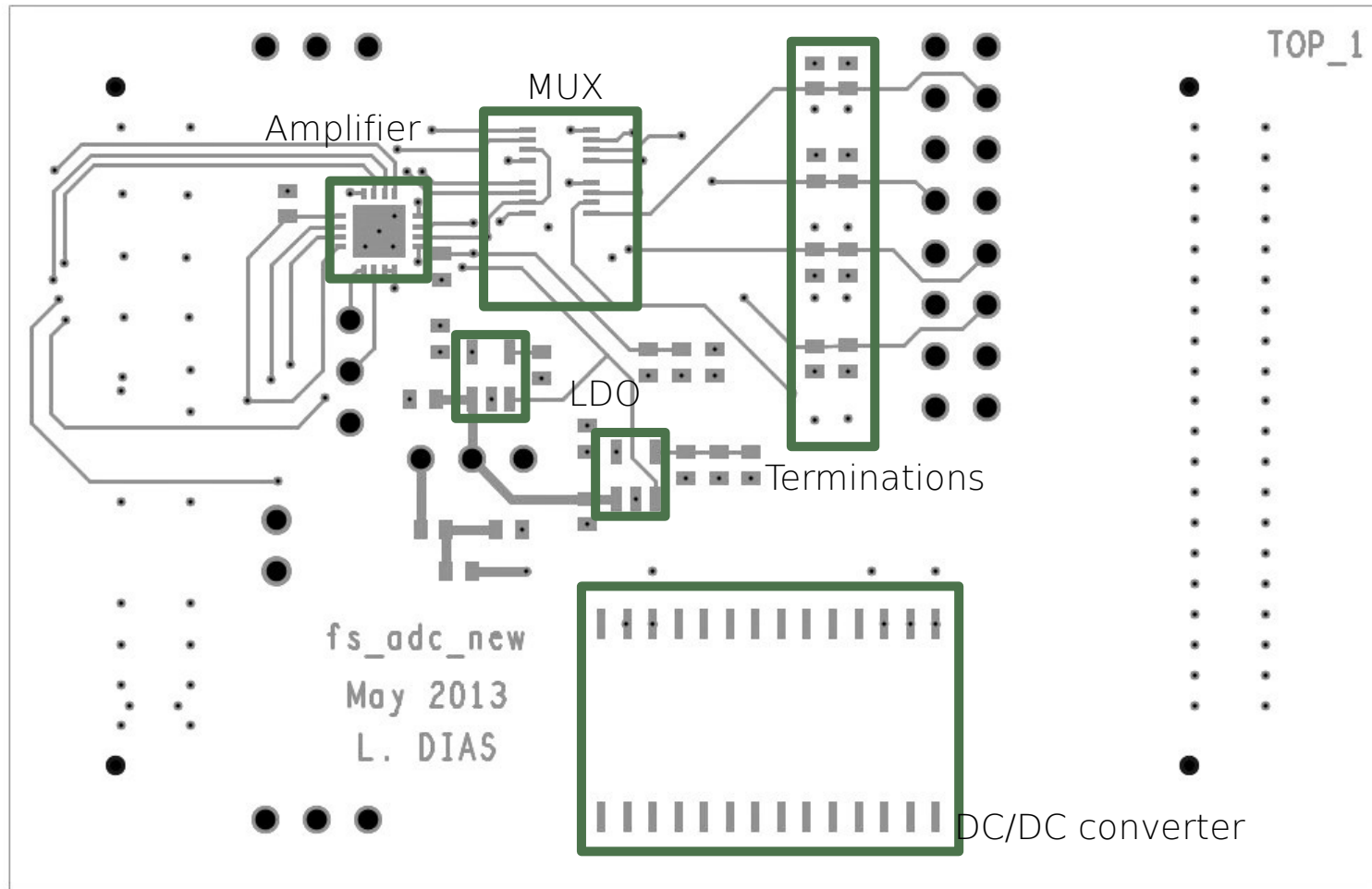

Results



- Debugging
- Tests

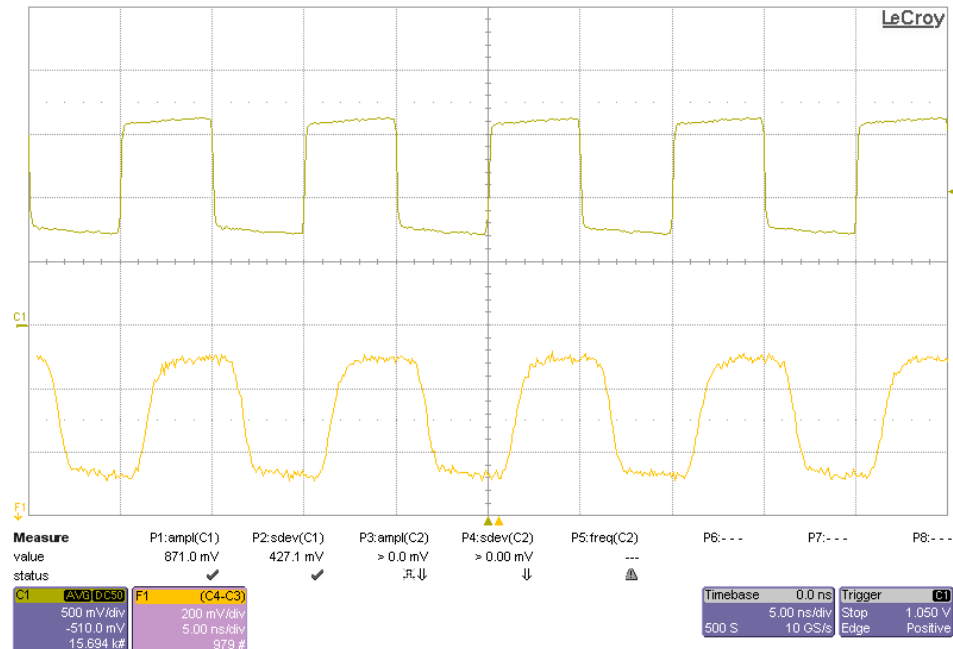



Thank you for your attention.